

- Electric Circuit: The closed path followed by an electric current.

$$I = \frac{d\phi}{dt} \text{ Clos or Amp}$$

$$P = \frac{dw}{dt}$$

- Electromotive Force: Voltage of an energy source.

$$V = \frac{dw}{d\phi}$$

$$P = \frac{dw}{d\phi} \cdot \frac{d\phi}{dt} = VI$$

$$W = \int_{-\infty}^t P dt J$$

⇒ Current entering +ve terminal → Absorbing  
 " leaving " " " → Delivering

- Absorbing Power Delivering Power

When the current is entering the +ve terminal then the element is absorbing power.

When the current is leaving the +ve terminal then the element is ~~delivering~~ delivering power.

1. Active Elements:

(i) When an element is capable of delivering power independently for infinite time is active element.

2. Passive L

(ii) When an element is having property of internal amplification, it is an active element.

2. Passive Elements:

(i) When an element is not capable of delivering energy independently then the element is called passive element.  
Eg:- Resistor, Inductor, Capacitor, etc.

a. Resistor: Current is directly proportional to applied voltage.

$$\text{b. Capacitor : } i = C \frac{dV}{dt}$$

$$\text{c. Inductor : } I = L \frac{dV}{dt}$$

2. Resistor :

$$J = \sigma E \rightarrow \text{Ohm's law 1st form}$$

$J \rightarrow$  current density in amperes per square meter

$\sigma \Rightarrow$  conductivity of the substance which is constant for each particular substance.

$E \rightarrow$  Electric field along the conducting substance in volts per meter.

$$J = \frac{I}{A}$$

$$\frac{I}{A} = \frac{1}{\rho} \cdot \frac{V}{l}$$

$$\frac{I}{A} = \frac{V \cdot l}{R \cdot A \cdot l}$$

$$I = \frac{V}{R}$$

$V = IR$  - Ohm's law 2<sup>nd</sup> form

$I = G V \rightarrow$  Ohm's Law 3<sup>rd</sup> form

$$G = \frac{1}{R}$$

$V = R d \varphi \rightarrow$  Ohm's law 4<sup>th</sup> form

## 2. Capacitor:

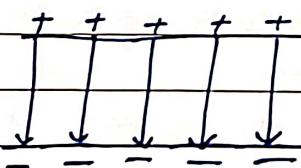


Fig: Electric field lines or lines of force  
b/w two charged conductor.

$$E = \frac{F}{Q}$$

Area of the plates as  $A$  and charge on the top plate  
be  $Q$

$$\text{Charge Density} = \frac{Q}{A}$$

$$J = \frac{I}{A}$$

$$\frac{I}{A} = \rho \cdot \frac{V}{l}$$

$$\frac{I}{A} = \frac{V \cdot l}{R A d}$$

$$I = \frac{V}{R}$$

$V = IR$  - Ohm's law 2nd form

$I = GV$  → Ohm's Law 3rd form

$$G = \frac{1}{R}$$

$V = R \frac{d\phi}{dt}$  → Ohm's law 4th form

## 2. Capacitor:

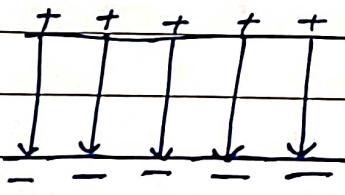


Fig: Electric field lines or lines of force b/w two charged conductors.

$$E = \frac{F}{Q}$$

Area of the plates are  $A$  and charge on the top plate be  $Q$ .

$$\text{Charge Density} = \frac{Q}{A}$$

Acc. to Gauss's Law

$$Q = \oint D \cos \theta dS$$

→ Increment of surface  
Angle b/w  $D$  and  $dS$ .

Flux Density

$$\Phi = DA$$

$$D = \epsilon E$$

$$E = \frac{Q}{EA}$$

$$V = Ed$$

$$V = \frac{Qd}{EA}$$

$$V = DQ$$

↳ elastance → reciprocal of Capacitance

~~elastance~~

$$V = \frac{Q}{C} \Rightarrow D = CV$$

$$C = \frac{EA}{d}$$

$$\frac{dq}{dt} = C \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_{-\infty}^t i dt$$

$$P = V_i$$

$$P = V_i C \frac{dv}{dt}$$

$$W = \int P dt = \int V_i C \frac{dv}{dt} dt$$

$$W = \frac{1}{2} C V^2$$

### \* Linear & Non-Linear Resistors:

When the resistor follows ohm's law it is linear resistor & when the resistor does not follow ohm's law it is non-linear resistors.

⇒ Bidirectional → Independent of direction of current.

$$\frac{dv}{dt} = \frac{cdt}{dt}$$

$$i = C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_{-\infty}^t i dt$$

$$P = Vi$$

$$P = VC \frac{dv}{dt}$$

$$W = \int P dt = \int VC \frac{dv}{dt} dt$$

$$W = \frac{1}{2} CV^2$$

\* Linear & Non-Linear Resistors:

When the resistor follows ohm's law it is linear resistor & when the resistor does not follow ohm's law it is non-linear resistors.

⇒ Bidirectional  $\rightarrow$  Independent of direction of current.

$\Rightarrow$  When  $C = \infty$ ,  $\frac{dV}{dt} = 0$   
 $\therefore i = 0$  ] Steady state  $\rightarrow$  open circuit

$\Rightarrow$  Capacitor doesn't allow sudden change in voltage.

$$i = C \frac{dV}{dt}$$

$dt \rightarrow 0$  for sudden change

$i \rightarrow \infty$  so it doesn't allow to change voltage suddenly

#### • Linear Capacitor:

When capacitance on the capacitor is independent on voltage magnitude then capacitor is called as linear capacitor.

#### • Non-Linear Capacitor:

When capacitance on the capacitor is dependent on voltage magnitude then capacitor is called as non-linear capacitor.

#### 3) Inductor:

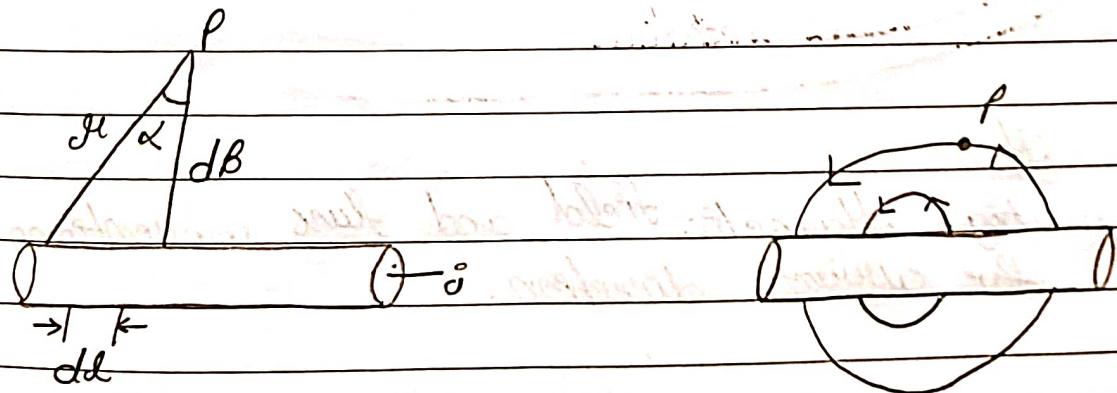


Fig: Identifying Quantities which determine the magnetic field at point P.

Force per unit magnetic pole:

$$\frac{dB}{4\pi\mu_0} = \frac{\mu_0 i \cos\theta d\phi}{r^2} \quad \text{(i)}$$

$\mu_0$  = magnetic permeability

$i$  = current


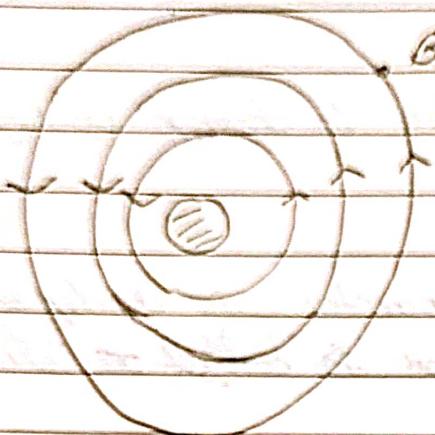


Fig: Cross-section of a current carrying conductor.

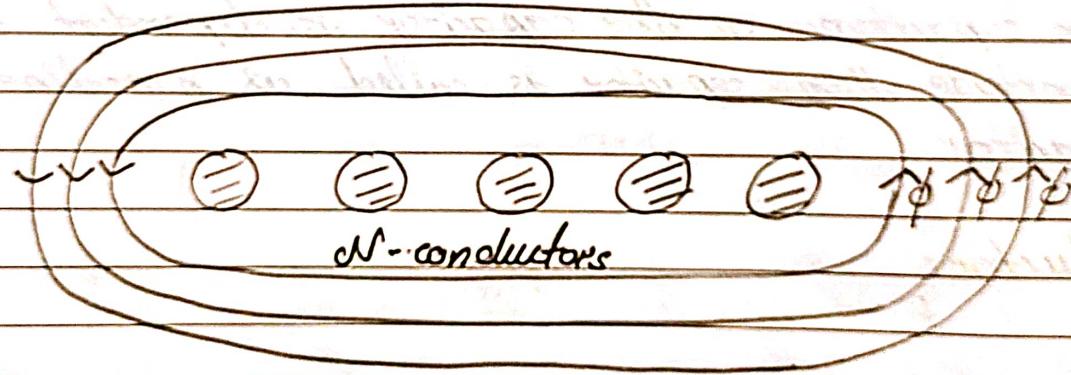

At

Fig: Magnetic field and flux conventions for current direction.

from (i)

- \* The magnetic field density from (i) is constant for a constant distance from the current carrying conductor.

The lines of magnetic field density by the sum of magnetic flux is given by

$$\phi = \int_{\text{cs}} B_a \cos \theta d\theta - \text{(ii)}$$

The total no. of flux linkage

$$\Psi = \sum_{j=1}^N N_j \phi_j - \text{(iii)}$$

~~N no of conductors when linked together in a magnetic field there'll be flux linkage.~~

flux linkage is the linking of the magnetic field with the conductors of a coil when the magnetic field passes through the loops of the coil, expressed as a value.

$$\Psi = N \int_{\text{cs}} B_a \cos \theta d\theta - \text{(iv)}$$

According to Faraday's law

$$V = K \frac{d\Psi}{dt} - \text{(v)}$$

$$K = 1$$

$$V = \frac{d\Psi}{dt} - \text{(vi)}$$

$$\Psi = \int_{-\infty}^t V dt - \text{(vii)}$$

$$Q = \int_{-\infty}^t I dt - \text{(viii)}$$

$$\Psi = \left[ N \int \left( \frac{\mu_0 \cos \vartheta}{4\pi A^2} \right) ds \right] i$$

-ix

$\Psi$  and  $i$  are inductance parameters

$$\Psi = L i - \textcircled{2}$$

$L \rightarrow$  Self Inductance  $\rightarrow$  Both  $\Psi$  and  $i$  have

same physical parameter

If current  $i$  produces flux linkages  $\Psi_2$  in another circuit the parameter is one of the mutual inductance.

$$\Psi_2 = M_{21} i - \textcircled{3}$$

Substitute  $\textcircled{2}$  in  $\textcircled{3}$

$$V = L \frac{di}{dt}$$

$$V = L \frac{dI}{dt}$$

\* We can't change current suddenly as  $\frac{di}{dt} \rightarrow \infty$

$$\therefore V = \frac{di}{dt}$$

$$\therefore V \rightarrow \infty$$

\* In steady state, inductor is short circuit

$$dt \rightarrow \infty$$

$$I = 0$$

## Semi/Non-Linear Inductance:

When the inductance of the inductor depends on the current magnitude, it is known as non-linear inductor.

When the inductance of the inductor depends on the current magnitude, it is known as linear inductor.

## Types of Resistors:

Fixed Resistors

Variable Resistors

### Fixed Resistor



#### Molded carbon composition resistor

(i) Carbon clay composition

(ii) Metallized type

(iii) Wire Wounded Resistor

A resistor has a colour band sequence yellow violet orange and gold. Find the range in which its value must lie so as to satisfy the manufacturer's tolerance.

Yellow  $\rightarrow 9$

Violet  $\rightarrow 7$

Orange  $\rightarrow 10^3$

Gold  $\rightarrow \pm 5$

$$(47 \times 10^3) \pm 5\%$$

$$= 44.65 \times 10^3 - 49.35 \times 10^3$$

$$2350 \Omega$$

### Linear & Non-Linear Inductance:

When the inductance of the inductor depends on the current magnitude, it is known as non-linear inductor.

when the inductance of the conductor depends on the current magnitude, it is known as linear inductor.

### Types of Resistors:

i) Fixed Resistors

ii) Variable Resistors

#### Fixed Resistor



#### Molded carbon composition resistor

→ (i) Carbon clay composition

→ (ii) Metallized type

→ (iii) Wire Wounded Resistor

Q A resistor has a colour band sequence yellow violet orange and gold. Find the range in which its value must lie so as to satisfy the manufacturer's tolerance.

Yellow → 4

Violet → 7

Orange →  $10^3$

Gold →  $\pm 5$

$$(47 \times 10^3) \pm 5\%$$

$$= 44.65 \times 10^3 - 49.35 \times 10^3$$

$$2350 \Omega$$

1st - 2nd Band 3rd Band 4th Band

Bye	Bill	Black	0	$10^0$	Gold $\rightarrow \pm 5\%$
Bye	Brown	Brown	1	$10^1$	Silver $\rightarrow \pm 10\%$
Rosie	Realised	Red	2	$10^2$	No color (brown) $\pm 20\%$
off	only	Orange	3	$10^3$	
Yester	Yesterday	Yellow	4	$10^4$	
Cro	Good	Green	5	$10^5$	
Bristol	Boys	Blue	6	$10^6$	
Via	Value	Violet	7	$10^7$	
Creat	Good	Gray	8	$10^8$	
Western	work	White	9	$10^9$	

- Type of Capacitor:  $\rightarrow$  offers low impedance to AC & high imp. to DC
  - a Fixed Capacitor
  - b Variable Capacitor

Capacitor is used to couple alternating voltage from one circuit to another circuit while at the same time blocking the DC voltage from reaching the next circuit. The capacitor is called as coupling capacitor or blocking capacitor or bypass capacitor.

There types of fixed capacitors:

a MICA

$\hookrightarrow$  5 pF to 10,000 pF

b Ceramic

$\hookrightarrow$  3 pF to 2 uF

ciii Electrolyte

$\hookrightarrow$  more than both

$\Rightarrow$  Capacitance colour code:

1st  $\rightarrow$  Temp. Coefficient


2nd  $\rightarrow$  Significant Digits

3rd  $\rightarrow$  2 zeros


4th  $\rightarrow$  2 zeros

5th  $\rightarrow$  Tolerance


## PN Junction [No external voltage]

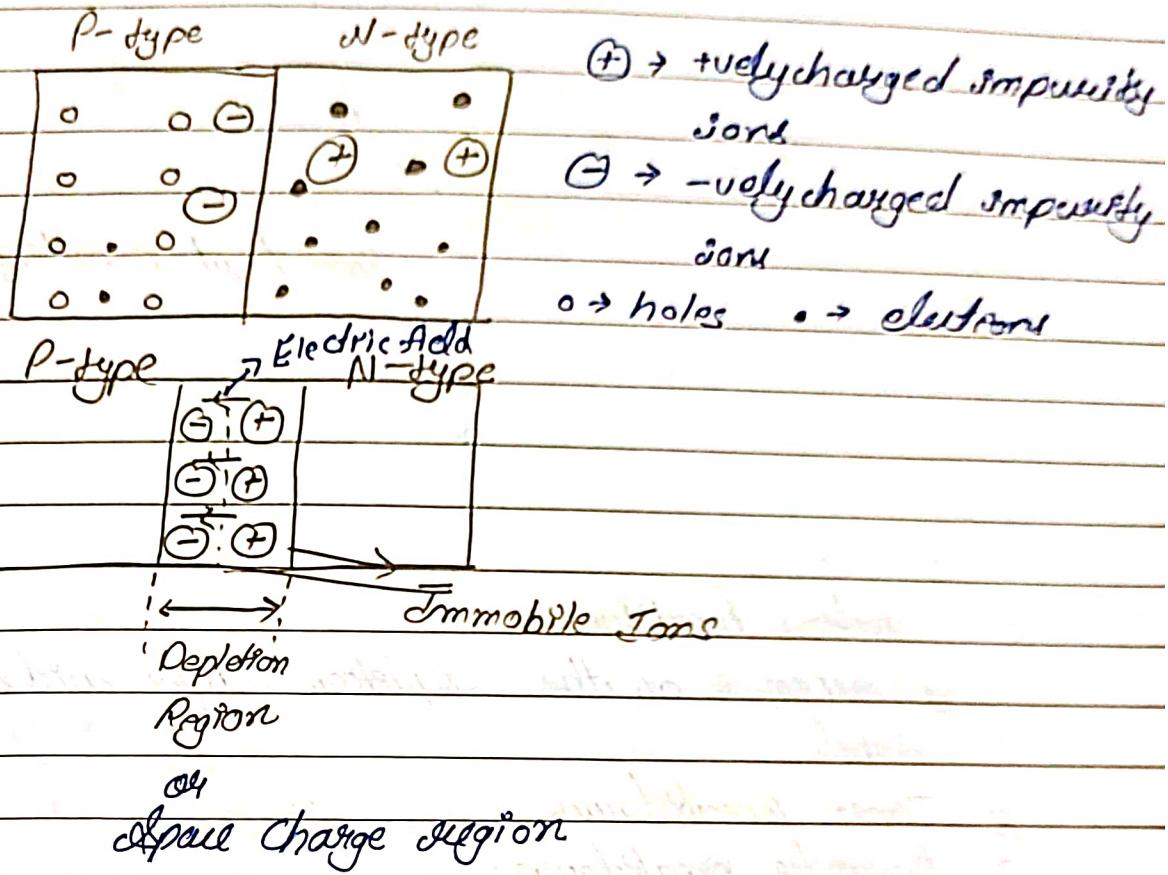

## Forward Bias - PN Junction

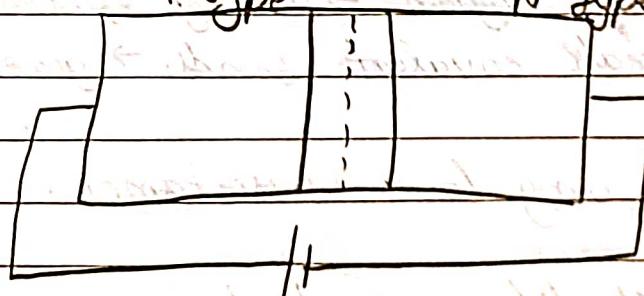
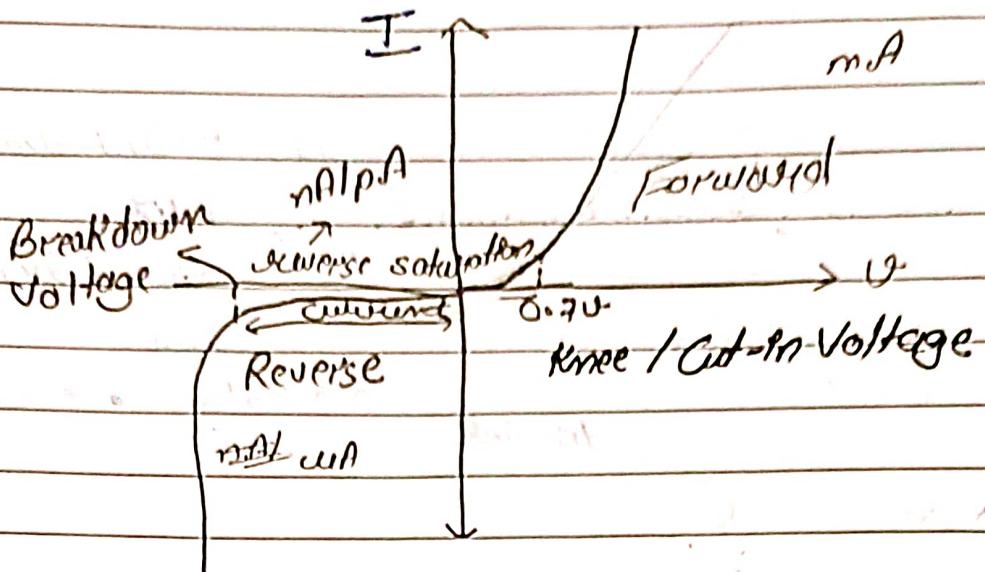
## I-V characteristics of a P-N junction diode:



### Junction Breakdown:

If depends on the depletion layer width and the doping level.

#### 1. Zener Breakdown

#### 2. Avalanche Breakdown

#### 1. Zener Breakdown:

If occurs when semiconductor is highly doped & we have narrow depletion region  $\rightarrow$  strong electric field  $\rightarrow$  strong enough to break covalent bonds  $\rightarrow$  generate e-h pair


Junction has very low resistance.

#### 2. Avalanche Breakdown (flood of carriers)

lightly doped  $\rightarrow$  large depletion region  $\rightarrow$  not strong  $E$   $\rightarrow$  can't break covalent bonds.

high energy  $\leftarrow$  increase v of  $\leftarrow$  minority carriers.

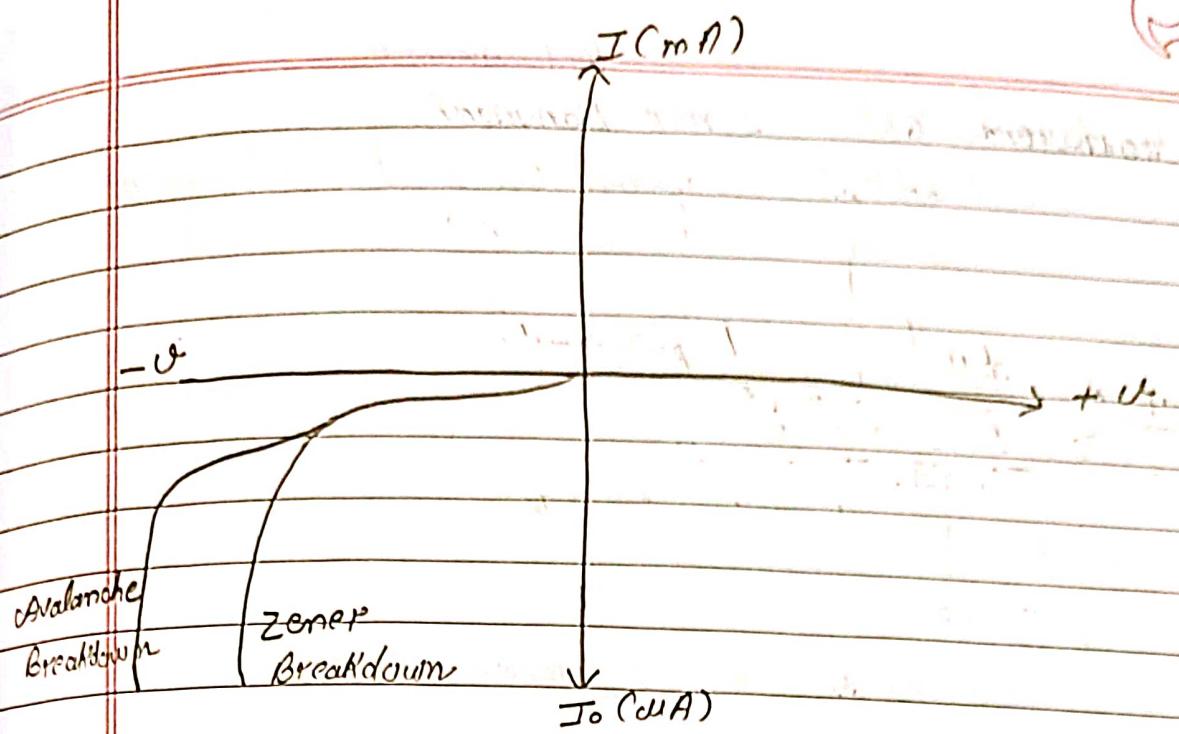have ability to break covalent bonds  $\rightarrow$  generate carriers accelerated by  $E$   $\rightarrow$  more collisions  $\rightarrow$  more generation.




\* Ideal diode can be said of it follows:

- i When its forward biased it conducts with a resistance.
- ii Infinite resistance when reverse biased  $\rightarrow$  open circuit


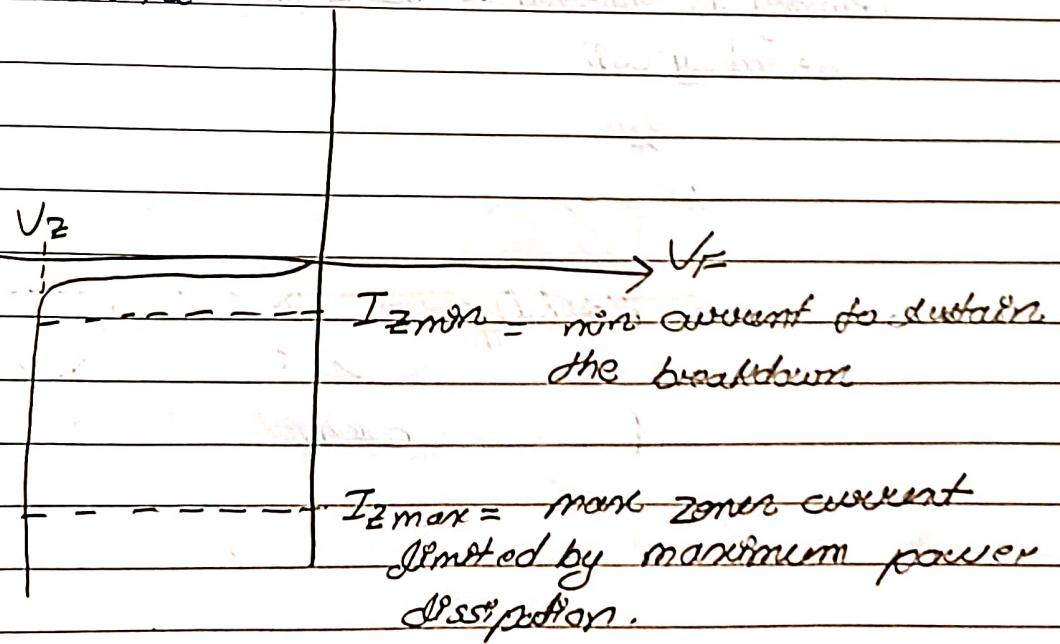
### • Zener Diode:

It is a reverse biased heavily doped silicon/germanium P-N junction diode which is operated in the breakdown region where the current is limited by both external resistance.





Predominance

- # Reverse Voltage  $< 6\text{V}$   $\rightarrow$  Zener Dominant  
 $> 6\text{V} \rightarrow$  Avalanche Dominant Predominant

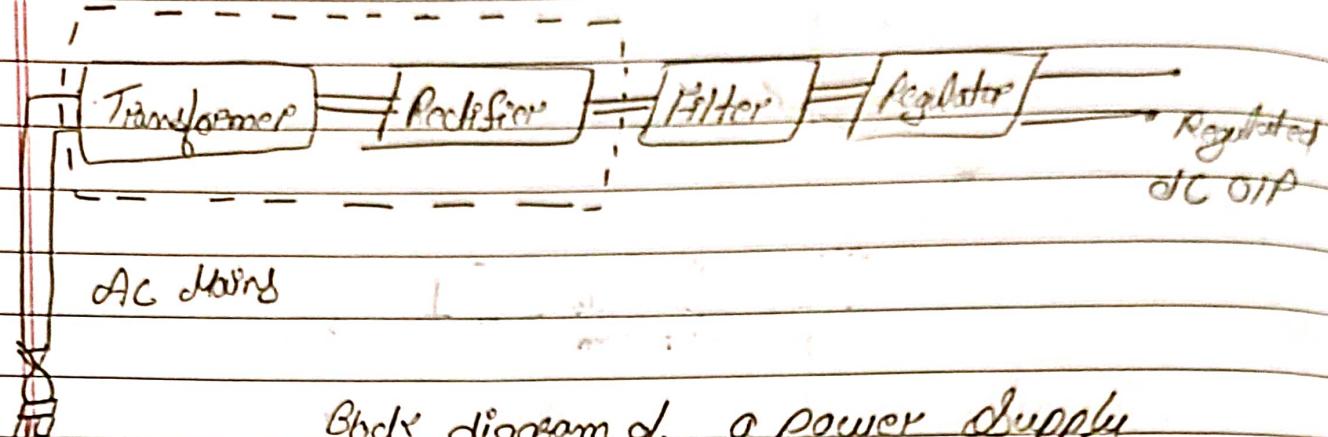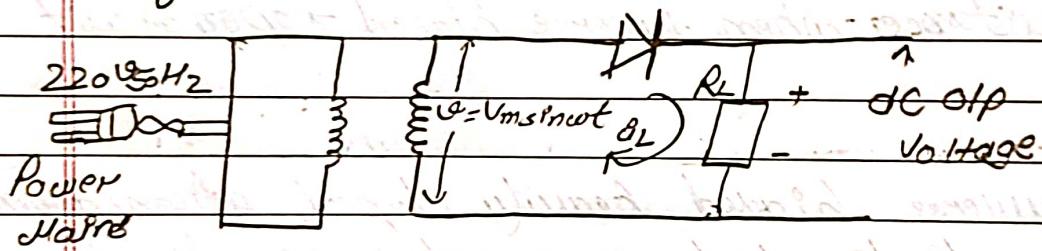
Block diagram of a power supplyRectifiers:1. Half Wave Rectifier -

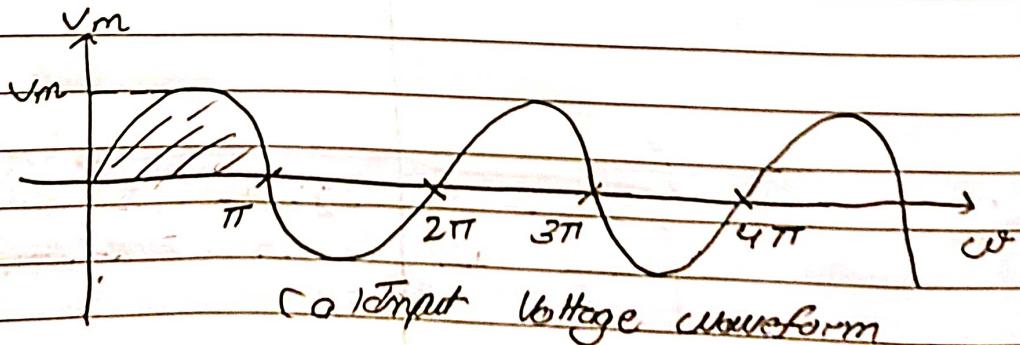Primary is connected to AC supply  $\rightarrow$  induce current in secondary coil.



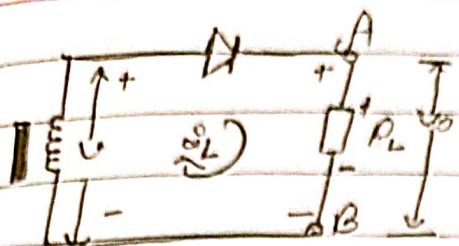

(a) During the half cycle

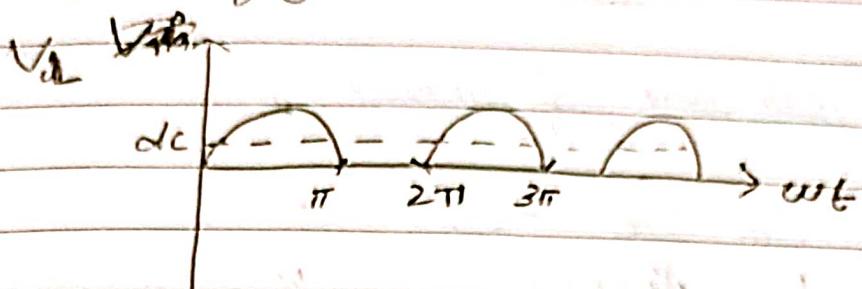


During Reverse bias  $\rightarrow$  No current  $\rightarrow$  no voltage  $\rightarrow$  no graph / current.

• Peak Inverse Voltage:

It will be the maximum voltage induced in secondary coil during reverse bias to withstand during the -ve half cycle of input.

• Output DC Voltage

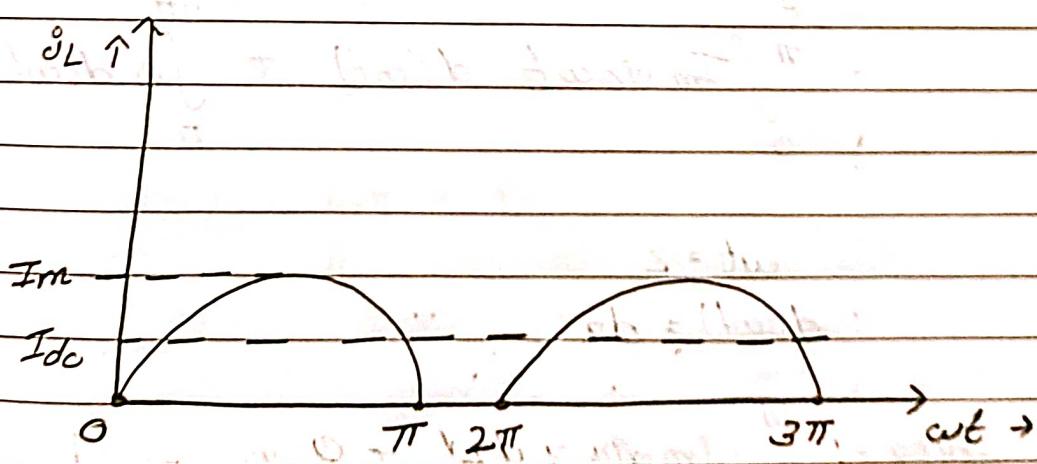

Key: Waveform of current flowing through  $R_L$  in a half wave Rectifier.

$$i_L = I_m \sin \omega t \quad - (1)$$

for  $0 \leq \omega t \leq \pi$

$$i_L = 0$$

for  $\pi \leq \omega t \leq 2\pi$

$I_m$  = peak value of current  $i_L$ .

$$I_m = V_m / R_L \quad - (2)$$

To find the DC or average value of current, we can find the net area under the curve over one complete cycle i.e. for  $0 \leq 2\pi$  and divide this area by the base i.e.  $2\pi$ .

We first integrate & then use eqn. (1) and to find the area.

$$\text{Area} = \int_0^{2\pi} i_L d(\omega t)$$

$$= \pi \int_0^{2\pi} I_m \sin \omega t d(\omega t) + \int_0^{2\pi} 0 d(\omega t)$$

$$\omega t = z$$

$$d(\omega t) = dz$$

$$\text{Area} = \pi \int_0^{\pi} I_m \sin z dz + 0$$

$$= 2 I_m \quad - (3)$$

Average value of the load current

$$I_{avg} = I_{dc} = \frac{\text{area}}{\text{base}} \\ = \frac{2 Im}{2\pi}$$

$$= \frac{Im}{\pi} - \textcircled{1} \cdot \text{Assumption:-} \\ \text{No diode drop forward} \\ \text{Negl. cap. in sec. winding}$$

DC voltage across the Load resistance  $R_L$ ,

$$V_{dc} = I_{dc} \times R_L = \frac{Im \times R_L}{\pi} - \textcircled{2}$$

If diode res. isn't negligible & ~~load~~<sup>diode</sup> resistance is comparable to  $R_L$

$$I_m = \frac{V_m}{R_L} \Rightarrow I_m = \frac{V_m}{(r_d + R_L)}$$

$$V_{dc} = \frac{Im}{\pi} \times R_L$$

$$= \frac{V_m}{\pi(r_d + R_L)} \times R_L$$

$$V_{dc} = \frac{V_m \times R_L}{\pi(r_d + R_L)}$$

$$= \frac{V_m R_L}{\pi(r_d + R_L)} = \frac{V_m}{\pi(r_d + R_L)}$$

$$\pi \left( 1 + \frac{r_d}{R_L} \right)$$



$$= \frac{V_m}{\pi} \left[ \text{if } r_d \ll R_L \right]$$

• Full-Wave Rectifier:

(1) Centre tap Rectifier

(2) Full Bridge Rectifier

(1) Centre tap Rectifier

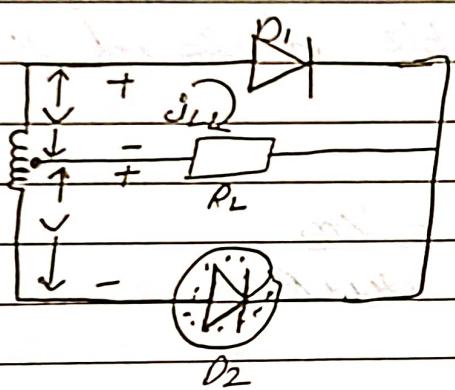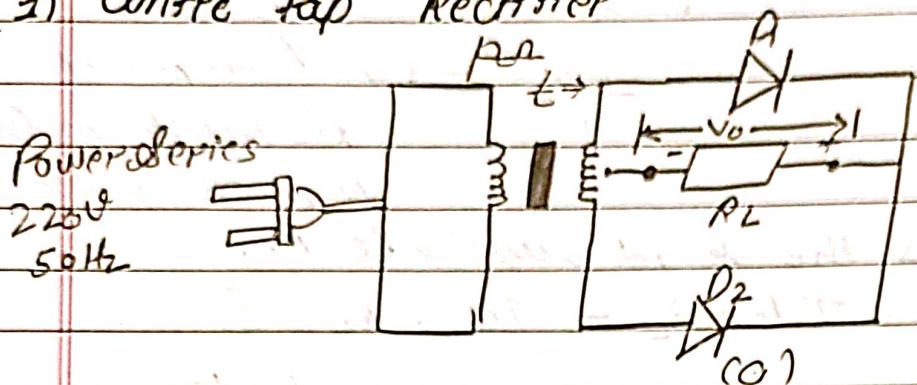


(a)

+ve half cycle

(b)

-ve half cycle

$v_{o(t)}$



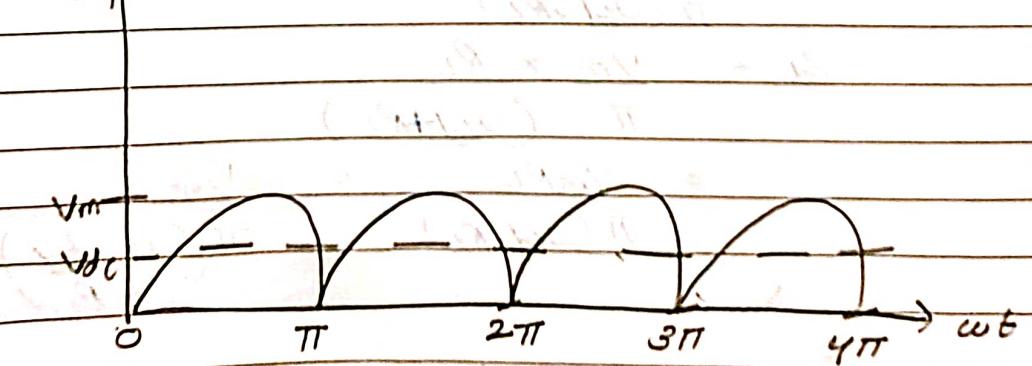


- Full-Wave Rectifier:

- Centre tap Rectifier

- Full Bridge Rectifier

- Centre tap Rectifier

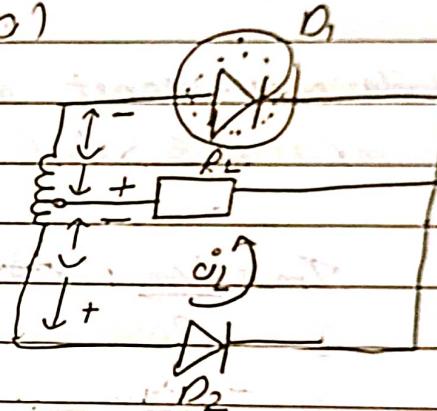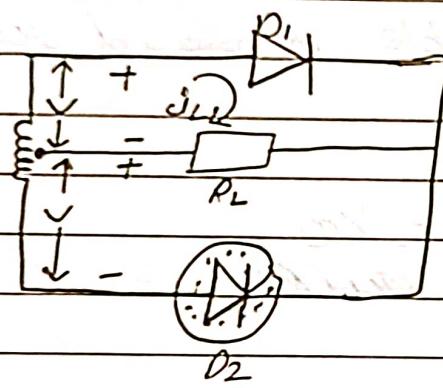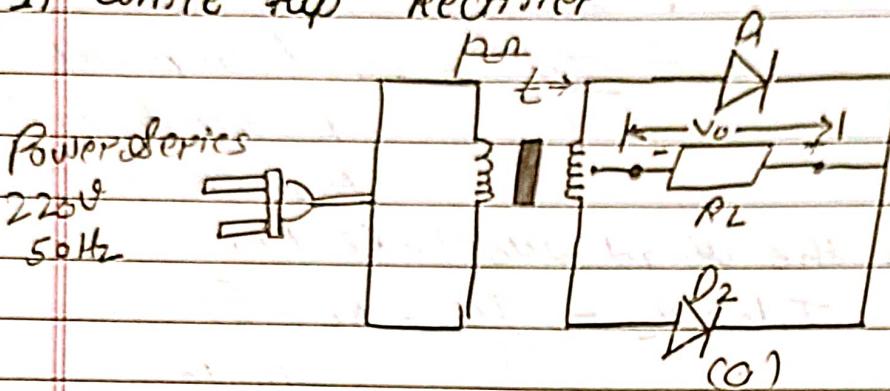

(b)  
+ve half cycle

(c)  
-ve half cycle

$V_{o1}$

$V_{o2}$

$\omega t$


During the +ve half cycle of secondary voltage the diode  $O_1$  is forward biased and  $O_2$  is reverse biased.

The current flows through the diode  $O_1$ , load resistor  $R_L$  and the upper half of the winding as shown in the figure no. (b).

During the -ve half cycle diode  $O_2$  is forward biased and  $O_1$  is reverse biased. Then  $O_2$  will conduct.

The load resistor current in (b) & (c) is same.

PIV for Center Tap:

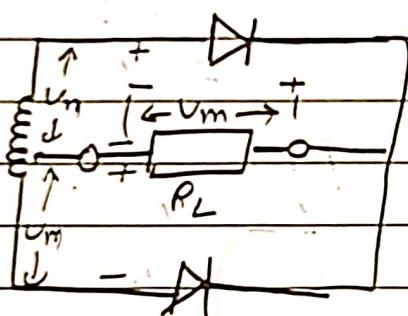

$$\text{PIV} = 2V_m$$

The reverse voltage that appears across the non-conducting diode is the summation of the voltage across the load resistor  $R_L$ .

diode  
cathode  
anode


During the +ve half cycle of secondary voltage the diode  $O_1$  is forward biased and  $O_2$  is reverse biased.

The current flows through the diode  $O_1$ , load resistor  $R_L$  and the upper half of the winding as shown in the figure no. (b).

During the -ve half cycle diode  $O_2$  is forward biased and  $O_1$  is reverse biased. Then  $O_2$  will conduct.

The load resistor current in (b) & (c) is same.


PIV for Center Tap:

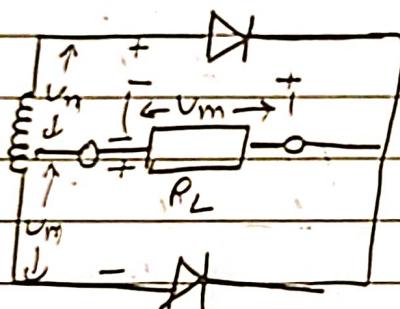

$$\text{PIV} = 2V_m$$

The reverse voltage that appears across the non-conducting diode is the summation of the voltage across the load resistor  $R_L$ .

## 2: Bridge wave Rectifier:

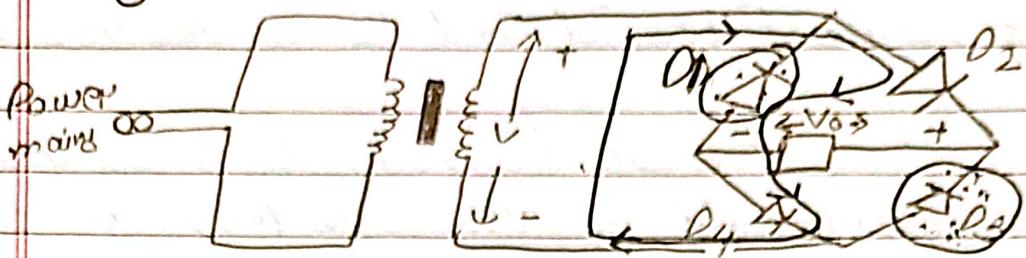


Positive Half Cycle  $D_2 \& D_4 \rightarrow$  forward bias  $\rightarrow$  Conduct

$D_1 \& D_3 \rightarrow$  Reverse Bias  $\rightarrow$  Do not conduct

Negative Half Cycle  $D_1 \& D_3 \rightarrow$  ~~Re~~ for. bias  $\rightarrow$  Conduct

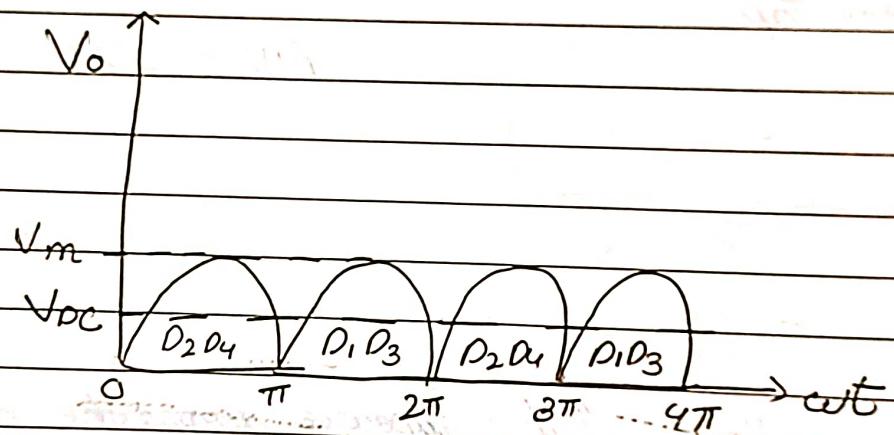$D_2 \& D_4 \rightarrow$  reverse bias  $\rightarrow$  Do not conduct



PIV:  $V_m$

- \*  $V_m$  is the max. voltage across secondary winding in bridge wave &  $V_m$  is the max. voltage across half the secondary winding in centre tap.

Output DC Voltage in voltage rectifiers:

$$V_{DC} = \frac{2 V_m}{\pi}$$

The output voltage of a full-wave rectifier is described as:

$$v_o = V_m \sin \omega t \quad 0 \leq \omega t \leq \pi \\ = -V_m \sin \omega t \quad \pi \leq \omega t \leq 2\pi$$

The average or the DC value of voltage is

$$V_{DC} = \frac{1}{2\pi} \int_0^{2\pi} V_o d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t) - \int_{\pi}^{2\pi} V_m \sin \omega t d(\omega t)$$

$$= \frac{1}{2\pi} V_m \left[ - \int_0^{\pi} \frac{V_m}{2} \sin \omega t dt - \int_{\pi}^{2\pi} \sin \omega t dt \right]$$

~~$$= \frac{1}{2\pi} \left[ - \cancel{\cos \omega t} + [\cancel{\cos \omega t}] \right]_{\pi}^{2\pi}$$~~

~~$$= \frac{(1+2+2)}{2\pi} \frac{V_m}{2}$$~~

$$= \frac{2V_m}{\pi}$$

Ripple Factor:

Ripple factor is a measure of purity of DC output of a rectifier

$R_f = \frac{\text{RMS value of components of wave}}{\text{average DC value}}$

- Rectification efficiency:

It tells us what percentage of total input AC power is converted into DC output power.

$$\eta = \frac{\text{DC power delivered to load}}{\text{AC input power from Transformer (T_x) secondary}}$$

$$= \frac{P_{dc}}{P_{ac}}$$

- Performance of half-wave rectifiers:

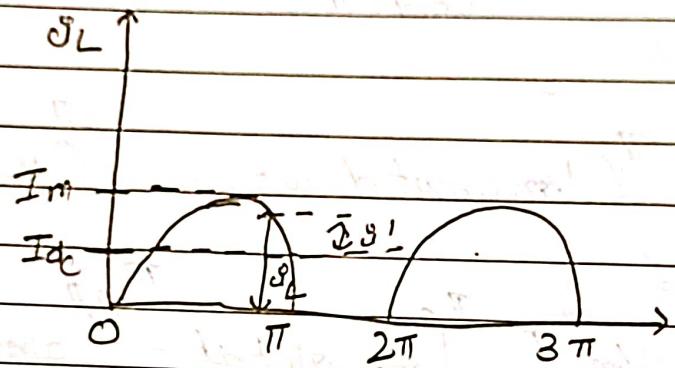


Fig: Half-Wave Rectified Current Value.

The instantaneous AC component of current is the difference b/w instantaneous total current & DC current i.e.

$$i'_L = i_m - i_{dc}$$

$$i'_L = \begin{cases} i_m & \text{for } 0 \leq wt \leq \pi \\ 0 & \text{for } \pi \leq wt \leq 2\pi \end{cases}$$

$\Rightarrow$  RMS value of current =

The sum or effective value of the current flowing through the load is given by,

- Rectification efficiency:

It tells us what percentage of total input AC power is converted into DC output power.

$$\eta = \frac{\text{DC power delivered to load}}{\text{AC input power from Transformer (T)}_2 \text{ secondary}}$$

$$= \frac{P_{dc}}{P_{ac}}$$

- Performance of half-wave rectifiers:

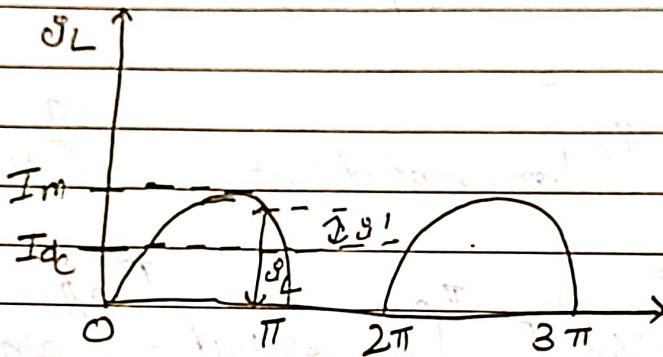


Fig: Half-Wave Rectified Current Value.

The instantaneous ac component of current is the difference b/w instantaneous total current & DC current i.e.

$$i' = i_L - i_{dc}$$

$$i_L = \begin{cases} i_{m\sin wt} & \text{for } 0 \leq wt \leq \pi \\ 0 & \text{for } \pi \leq wt \leq 2\pi \end{cases}$$

$\Rightarrow$  RMS value of current =

The rms or effective value of the current flowing through the load is given by,

$$I_{D\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} j_L^2 d(\omega t)}$$

$$= \frac{I_m}{\sqrt{2\pi}} \sqrt{\int_0^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t)}$$

$$= \frac{I_m}{\sqrt{2\pi}} \sqrt{\frac{\pi}{2} - \left[ \frac{\sin \omega t}{2} \right]_0^{\pi}}$$

$$= \frac{I_m}{2}$$

$$\ddot{j}' = \ddot{j}_L - \dot{j}_d c$$

The rms value of ac component.

$$I'_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (\dot{j}_L - \dot{j}_d c)^2 d(\omega t)}$$

$$I'_{\text{rms}} = \sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2}$$

$$\mathcal{R} = \frac{I'_{\text{rms}}}{I_{\text{dc}}}$$

$$= \sqrt{I_{\text{rms}}^2 - I_{\text{dc}}^2}$$

$$= \sqrt{\frac{I_{\text{rms}}^2 - I_{\text{dc}}^2}{I_{\text{dc}}^2}}$$

$$= \sqrt{(0.57)^2 - 1}$$

$$\boxed{I_{\text{dc}} = 1.21}$$

- Rectification efficiency of half-wave rectifier:

The DC power delivered to the load,

$$P_{dc} = I^2_{dc} R_L = \left(\frac{I_m}{\pi}\right)^2 R_L$$

The total AC input power is

$$\begin{aligned} P_{ac} &= I^2_{rms} (S_d + R_L) \\ &= \left(\frac{I_m}{2}\right)^2 (S_d + R_L) \end{aligned}$$

$$\therefore \eta = \frac{P_{dc}}{P_{ac}} = \left(\frac{I_m}{\pi}\right)^2 \times \left(\frac{2}{I_m}\right)^2 \times \frac{R_L}{S_d + R_L}$$

$$= \frac{4}{\pi} \times 100 \% \times \frac{R_L}{1 + S_d / R_L}$$

~~$$= \frac{R_L}{\pi (1 + S_d / R_L)} = \frac{40.6 \%}{1 + S_d / R_L}$$~~

- Performance of full-wave rectifier.

RMS value of current

$$\begin{aligned} I_{rms} &= \sqrt{\frac{1}{2\pi} \int_0^{\pi} I_m^2 \cos^2 wt + \int_0^{2\pi} I_m^2 \sin^2 wt} \\ &= \frac{I_m \times \sqrt{2}}{\sqrt{2\pi}} \int_0^{\pi} \cos^2 wt \\ &= \frac{I_m}{\sqrt{\pi}} \int_0^{\pi} \frac{\pi - \sin 2wt}{2} \\ &= \frac{I_m}{\sqrt{\pi}} \cdot \frac{I_m}{\sqrt{2}} \end{aligned}$$

RMS value of current

$$\begin{aligned} I_{\text{rms}} &= \frac{1}{\sqrt{2\pi}} \int_0^{\pi} I_m \sin \omega t \, dt \\ &= \frac{I_m}{\sqrt{2\pi}} \times \sqrt{\pi} \\ &= \frac{I_m}{\sqrt{2}} \end{aligned}$$

$$i' = i_L - i_{dc}; i_{dc} = \frac{2I_m}{\pi}$$

$$I'^{\text{rms}} = \sqrt{I^2_{\text{rms}} - i_{dc}^2} = \sqrt{I^2_{\text{rms}} - \left(\frac{2I_m}{\pi}\right)^2} = \sqrt{I^2_{\text{rms}} - \frac{4I_m^2}{\pi^2}}$$

$$\begin{aligned} M &= \frac{I'^{\text{rms}}}{I_{dc}} \\ &= \sqrt{\frac{I^2_{\text{rms}} - 1}{I_{dc}^2}} \\ &= \sqrt{\left(\frac{I_m}{\sqrt{2}}\right)^2 \times \frac{\pi^2}{4I_m^2} - 1} \\ &= \sqrt{\frac{\pi^2}{8} - 1} \\ &= 0.482 \end{aligned}$$

$\Rightarrow$  Rectification efficiency:

$$P_{dc} = I^2_{dc} R_L = \left(\frac{2I_m}{\pi}\right)^2 R_L$$

$$\begin{aligned} \text{Total ac Power} &= I^2_{\text{rms}} (C_{rd} + R_L) \\ &= \frac{I_m^2}{2} (C_{rd} + R_L) \end{aligned}$$

$$\begin{aligned} \eta &= \frac{\frac{4I_m^2}{\pi^2} \times R_L \times 100}{\frac{I_m^2}{2} (C_{rd} + R_L)} = \frac{8}{\pi^2} \times 100 \times \frac{1}{\frac{C_{rd}}{R_L} + 1} \\ &= 81.2\% \end{aligned}$$

• Comparison of different rectifiers

Half-Wave Rectifier

Full-Wave Rectifiers.

Centre tap

Full Wave

1. No. of diodes

1

2

4

2. Toc  
necessary

No

Yes

~~Yes~~ No

3. Peak Vm

2Vm

Vm

Sec. Volt.

4. Peak  
load current  
 $I_{Lm}$

Vm

$$\frac{V_m}{R_L + R_s} = \frac{V_m}{R_L}$$

5. Ims

$$\frac{I_m}{2}$$

$$\frac{3I_m}{\sqrt{2}}$$

$$\frac{I_m}{\sqrt{2}}$$

6. Idc

$$\frac{I_m}{\pi}$$

$$\frac{2I_m}{\pi}$$

$$\frac{2I_m}{\pi}$$

7. Ir

$$1.21$$

$$0.482$$

$$0.482$$

8. η

$$40.6\%$$


$$81.2\%$$

$$81.2\%$$



# Transformer may be used for isolation even if not required for stepping up or down the input ac.

- Filters:

To minimise the ripple content.

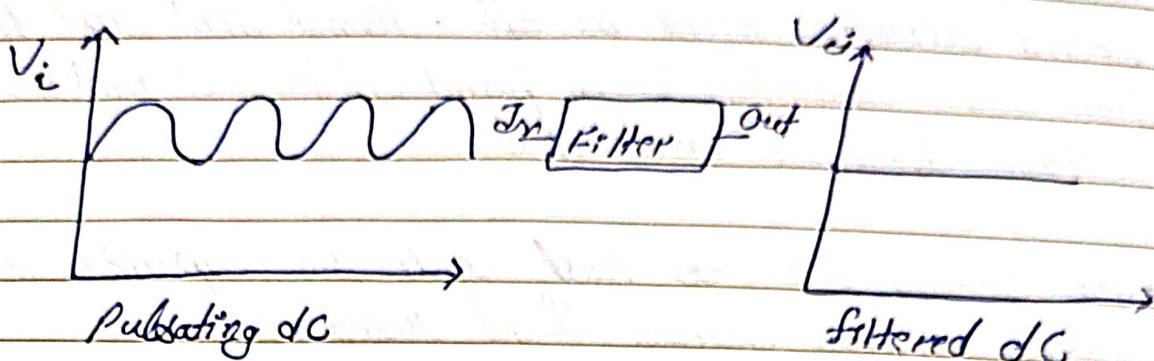

- Shunt Capacitor Filter  $\rightarrow$

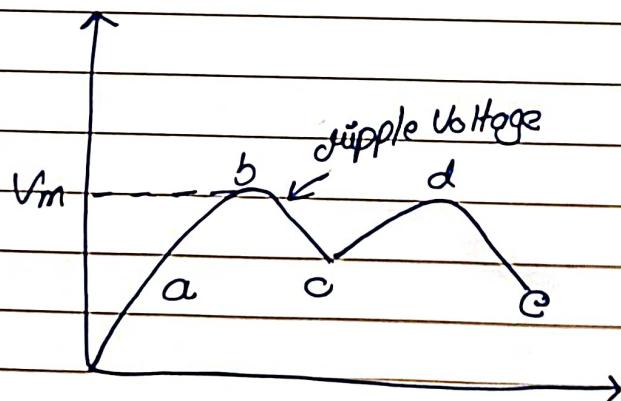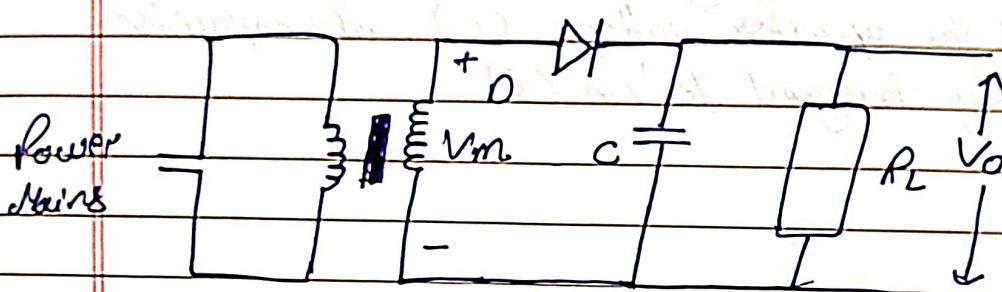

When the true half cycle of the AC input is applied the diode is in forward bias and hence it'll conduct. So this allows the capacitor to quickly charge upto  $V_m$ , i.e., upto (b).

- iii After we fully charge, the capacitor holds the charge till the input ac supply to the rectifier goes negative.
- iv During the -ve half cycle the capacitor attempts to discharge. However, it can't discharge through diode being reverse bias as off. Hence it still ~~can't~~ discharge from load resistor from point (b) to (c) and its voltage decreases somewhat.
- v Even during the -ve half cycle the capacitor maintains large voltage across load resistor.
- vi During the next +ve half cycle when the rectifier voltage exceeds the capacitor voltage (c), the capacitor is again quickly charged to  $V_m$  (d).