

Part 2A/B - I

(Gaurav Jha)

## Experiment 1 : Diode Characteristics

### Objective :-


Measure the I-V Characteristics of Diode.

### Materials Required

1. Breadboard
2. Equipment : DC Power supply and Benetech Digital Multimeter
3. Components :
  - Diode : One - IN4007 (Diode voltage drop  $V_D = 0.7\text{V}$ ).
  - Resistance : One -  $100\Omega$ .
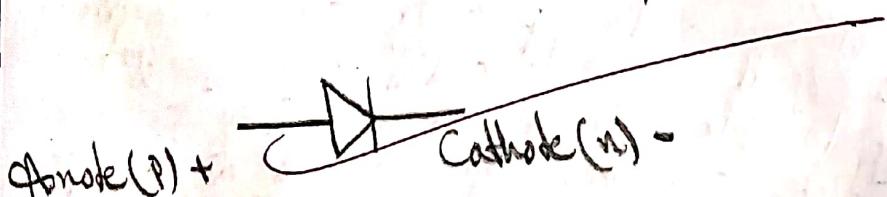
### Structure of P-N Junction Diode

The diode is a device formed from a junction of n-type and p-type semiconductor material. The lead connected to the p-type material is called the anode and the lead connected to the n-type material is cathode. In general the cathode of a diode is marked by a solid line on the diode.



## Biassing of PN junction Diode

### Forward bias Operation

The P-N junction supports uni-directional current flow. If +ve terminal of the input supply is connected to P-side and -ve terminal is connected to N-side, then diode is said to be forward biassed condition. In this condition the height of the potential barrier at the junction is lowered by an amount equal to given forward biassing voltage. Both the holes from P-side and electrons from N-side cross the junction simultaneously thereby decreasing the depleted region. This constitutes through the diode to be very large, the diode can be approximated as short - Circuit switch Diode after a very small resistance called forward resistance.

### Reverse bias Operation

If negative terminal of the input supply is connected to P-side and +ve terminal is connected to a N-side then the diode is said to be reverse biassed. In this condition an amount equal to reverse biassing voltage increases the height of the potential barrier at the junction. Both the holes on P-type and electrons on N-type tend to move away from the junction thereby increasing the depleted region. However the process cannot continue indefinitely, thus a small current called reverse saturation current continues to flow in the diode. This current is negligible; the diode can be approximated as an open circuit switch it offers a very high resistance called reverse resistance.


## Diode Characteristics:

The nonlinear characteristics of diodes are used extensively in the design of digital and analog circuits. The terminal current voltage (IV) characteristic of diode is described by Shockley's equation and is given by

$$I_D = I_S (e^{\frac{V_D}{n k T}} - 1)$$

where  $I_D$  is the diode current,  $V_D$  is diode voltage,  $I_S$  is the diode saturation current,  $n$  is the ideality factor,  $k$  is Boltzmann's constant, and  $T$  is the absolute temperature.

## Circuit Diagram

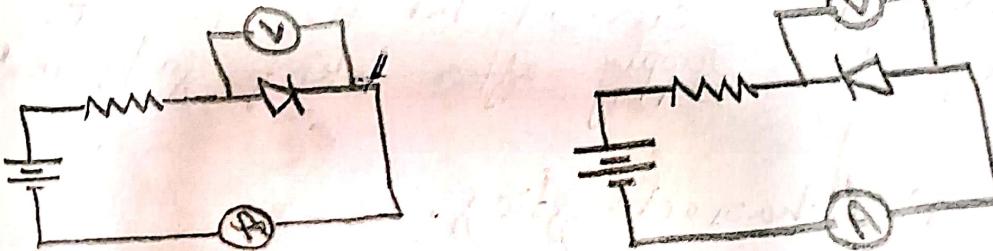

Forward Biasing

Reverse Biasing

Fig 1 (a) Forward Bias (b) Reverse Bias

## Procedure:

Before you proceed, identify the p and n-side of the diode in order to connect properly in forward and reverse bias mode.

## Forward Bias Characteristics:

1. Assemble the circuit on your breadboard as shown in Fig 1(a). Connect to the 0-30V DC power supply.
2. Switch on the power supply. Slowly increase the supply voltage in steps of 0.1 volt using the fine adjustment knob and note down the corresponding diode current. When you find the change in current is large, increase the supply voltage in steps of 0.5 to note down current.
3. Using multimeter in appropriate mode, measure voltage drop across the diode and the current in the circuit. Switch off the supply after taking sufficient readings.
4. Plot the IV characteristics.

## Reverse Bias Characteristics:

1. Assemble the circuit on your breadboard as shown in Fig 1(b), connect to the 0-30V DC power supply.
2. Switch on the supply. Increase the supply voltage in steps of 0.5 volt to note down the diode current.
3. Use multimeter for voltage and current measurements. Keep in mind the magnitude of current flowing in the circuit will be very small, so chose current range properly. Switch off the supply after taking sufficient readings.
4. Plot the IV characteristics and estimate the reverse saturation current.

Forward bias	Voltage applied (V)	Current, $I_D$ (mA)	Voltage applied (V)	Current, $I_D$ (mA)	Kerridge sweep
			Voltage, $V_D$ (V)	Voltage, $V_D$ (V)	
0.1	-0.19mV	-0.001mA	0	-0.142mV	
0.2	99.84mV	0.003mA	0.1	-99.291mV	
0.3	199.712mV	0.013mA	0.2	-199.405mV	
0.4	0.299V	0.32mA	0.3	-300mV	
0.5	0.392V	6.87mA	0.4	-400mV	
0.6	0.457V	11.98mA	0.5	-499mV	
0.7	0.494V	105mA	0.6	-599mV	
0.8	0.518V	195.93mA	0.7	-699mV	
0.9	0.535V	0.236mA	0.8	-799mV	
1.0	0.549V	0.355mA	0.9	-899mV	
1.1	0.614V	0.466mA	1.0	-999mV	
1.2	0.639V	0.421mA	1.1	-1999mV	
1.3	0.656V	0.424mA	1.2	-2999mV	
1.4	0.668V	0.438mA	1.5	-3998mV	
1.5	0.544mA	0.000mA	1.6	-4997mV	

## Exercise

1. Write the values of the resistance (in  $\Omega$ ,  $k\Omega$  or  $M\Omega$ ) having the following colour bands:

- Green, Blue, Black, Gold:  $56\Omega \pm 5\%$ .
- Red, Red, Red, Silver:  $2200\Omega \pm 10\%$
- Yellow, violet, Red, Gold:  $4700\Omega \pm 5\%$
- Brown, Black, Green, Silver:  $1000000 \pm 10\%$

2. Answer the following questions on a separate sheet and attach it to this sheet.

- Write the colour code used to specify the value of a resistance.

Ans :-

Colour	Digit	Multiplicator	Tolerance
Black	0	1	
Brown	1	10	$\pm 1\%$
Red	2	100	$\pm 2\%$
Orange	3	1000	
Yellow	4	10000	
Green	5	100,000	$\pm 0.5\%$
Blue	6	1,000,000	0.25%
Violet	7	10,000,000	0.1%
Grey	8	<del>100,000,000</del>	0.05%
White	9	<del>1000000000</del>	
Gold	0		$\pm 5\%$
Silver			$\pm 10\%$


cathode and anode are generally indicated on a  
?

On a physical diode, you will notice two terminal  
from a tin can shape in the middle. One  
the positive terminal called the anode. The other  
is the negative end, called the cathode.

What does the notch on a transistor indicate?

In a practical transistor, there is a notch present  
on emitter lead for identification.

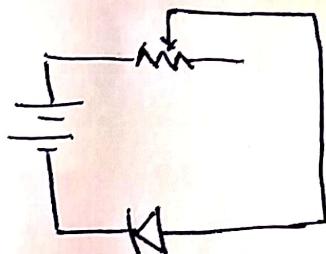See a circuit diagram to generate a variable  
voltage from 0-5V using a Potentiometer and a  
power supply of 5V.




### Conclusion

From this experiment, we learnt  
about the IV characteristics of a diode

Kaelan  
20/1/24.

## IV characteristics

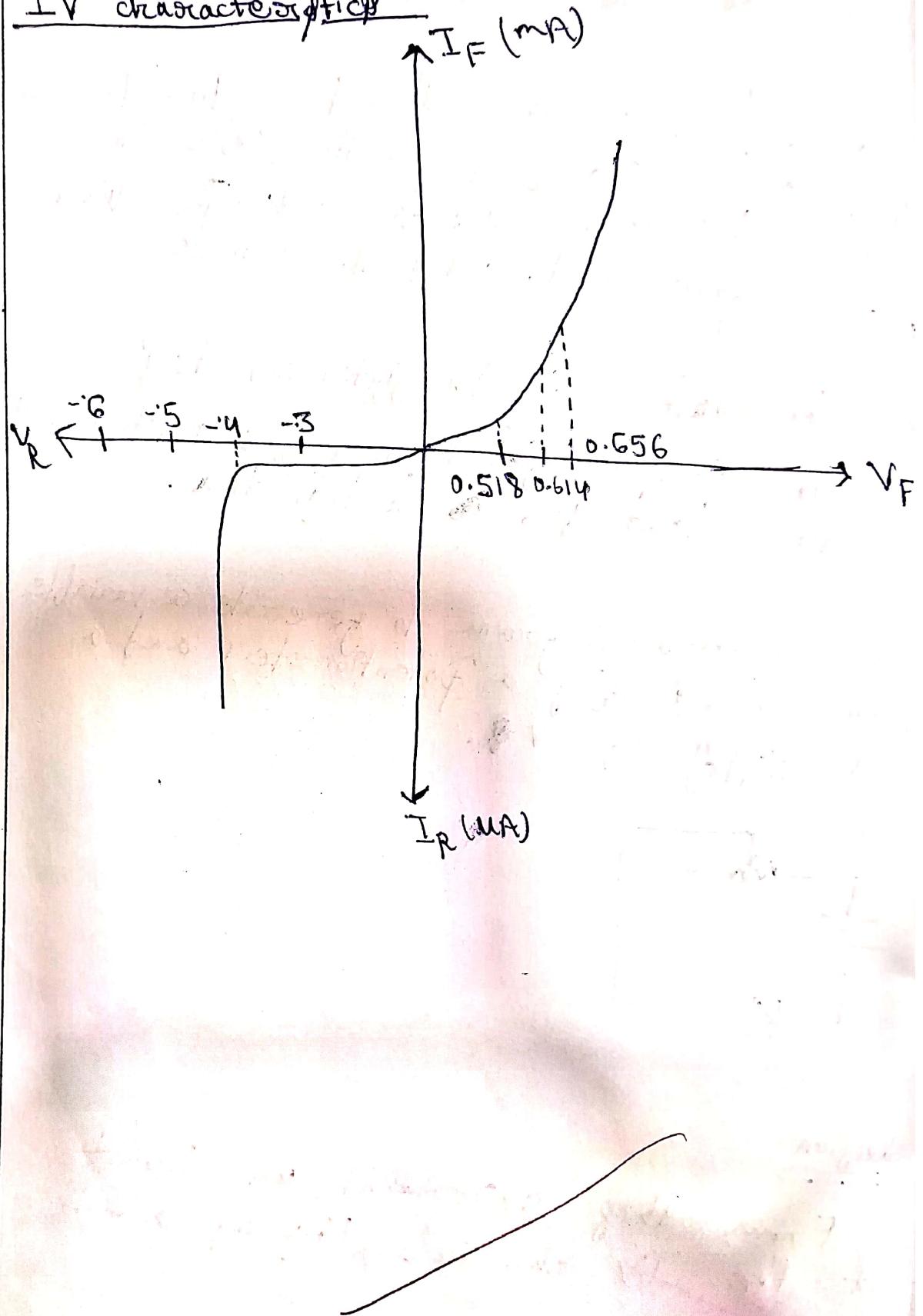

## Experiment - 2 (POST-LAB) (ABHISHEK)

### Half Wave and Full Wave Rectifier Circuits

#### Objective:

Design and analysis of half wave and full wave rectifier circuits.

#### Materials Required:

Breadboard.

- Equipment function generator and oscilloscope.
- Components:
  - Transformer : One - 230V to 12-0-12V
  - Diode : Two - 1N4007 (Diode voltage drop  $V_D = 0.7V$ )
  - Resistors :  $1\text{ k}\Omega$ ,  $2.2\text{ k}\Omega$

#### General guidelines/precautions:

- Connect the diode with correct polarity. Check the diode voltage first to confirm if the diode is working.

Keep ground terminals of oscilloscope probes and function generator output connected throughout the experiment.

- In an oscilloscope, for higher precision, increase vertical sensitivity (i.e. lower value of volt/div), especially while measuring small amplitude levels (e.g. ripple voltage). You may need to switch to ac coupling while doing so.

- 4- In the case of full wave rectifier, switch on the mains supply to the transformer etc only after you have made all other circuit connections (in order to avoid electric shock) supply
- 5- Also, while making any changes in the DC circuit, switch off the mains supply definitely.
- 6- Use "line" as the source of trigger signal in the oscilloscope. Put the oscilloscope in the CHOP mode.
- 7- Make sure that the power lines in a breadboard given on the top and bottom. Care for the power supply must be used full from these you connect to the other parts of the circuit.
- 8- Switch off the supply to all the components before you make any changes in the circuits.

## II Half Wave and FULL Wave Rectifier

the very important applications of one diod is as a rectifier to convert AC into DC power supply is required for the operation of most of the electronic and circuits (For example: Television, radio, telephone, mobile as well as measurement instruments like multi-meter, oscillators, etc.)

eters etc.). Now a days, almost all electro-  
nic equipment includes a circuit that converts  
AC supply into DC supply. The first block  
for DC power supply is rectifier. Rectifier may  
be defined as an electronic device used to  
convert AC Voltage or current into unidirectional  
voltage or current. Since a diode p-n  
junction conducts in one direction but not in  
the reverse direction, diodes can be used  
as a rectifier. Rectifier broadly divided into  
two categories : Half wave rectifier and  
full wave rectifier.

### Part A : Half Wave Rectifier

In positive half cycle, diode D is forward biased, and conducts. Thus, the output voltage is same as the input voltage. In the negative half cycle, D is reverse biased, and therefore output voltage is zero.

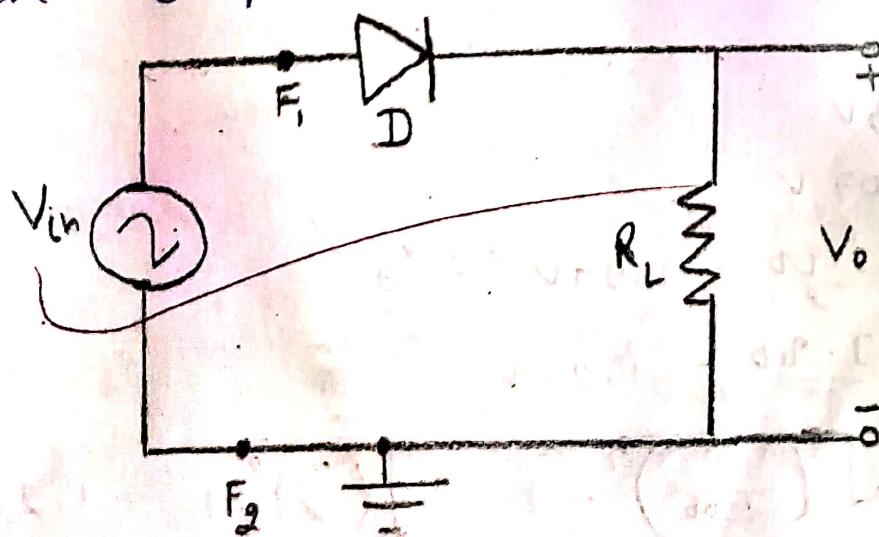
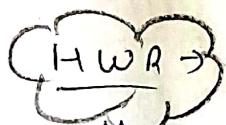


Figure 4 Half wave Rectifier circuit

- Determine the average value  $V_{dc}$  and maximum efficiency.
- Set the function generator to obtain 10V  $\frac{V_{pp}}{2\pi}$  to peak sine wave at 500 Hz frequency. Do not connect any circuit to the function generator. Keep DC offset equal to 0. Set the function generator output on the oscilloscope and verify sine wave generation.
- Set up the circuit as shown in Fig. 2 taking  $R_L = 2.2 \text{ k}\Omega$ .
- Now, connect the function generator to circuit at points F1 & F2 as shown in Fig. 2.

Display  $V_i$  and  $V_o$  simultaneously on the oscilloscope. Sketch  $V_i$  and  $V_o$  below the other with identical time and amplitude axes.

 H.W.R.

$$V_m = 3.88 \text{ V}$$



$$V_{pp} = 4.07 \text{ V}$$

$$V_{rms} = \frac{3.88}{\sqrt{2}} = 1.94 \text{ V} = \frac{V_m}{\sqrt{2}}$$

$$V_{dc} = \frac{3.88}{\pi} = 1.23 \text{ V} = \frac{V_m}{\pi}$$

$$R.F. = \sqrt{\left(\frac{3.88}{\frac{3.88}{\pi}}\right)^2 - 1} = \sqrt{\left(\frac{\pi}{2}\right)^2 - 1} = 1.208$$
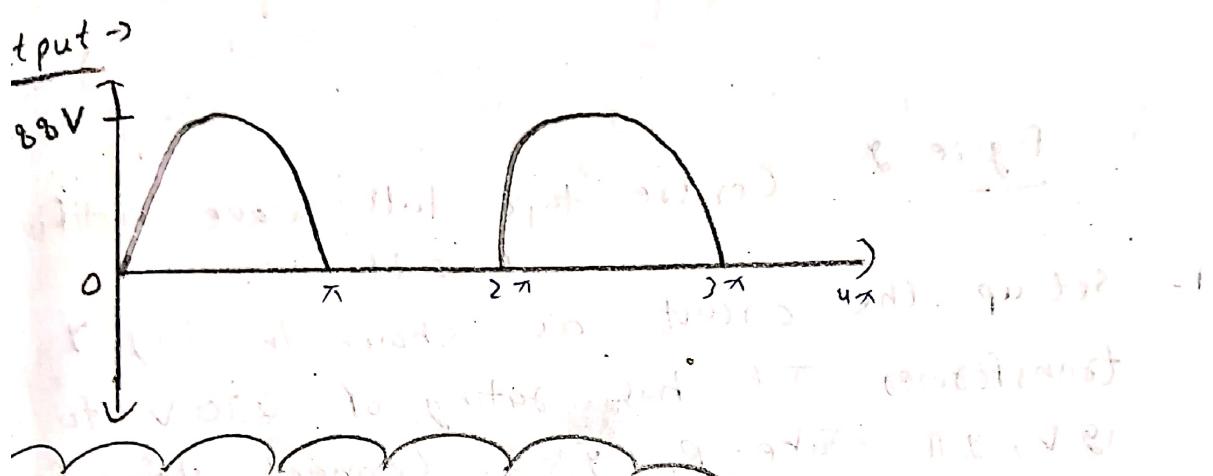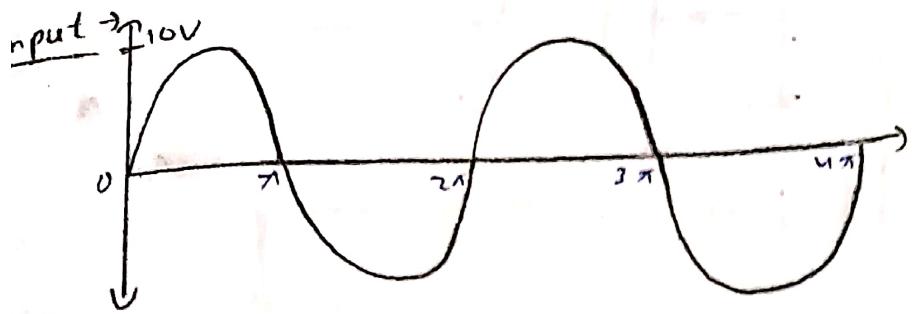
$$n = \left(\frac{\pi}{2}\right)^2 \times 100 = 40.52 \approx \left(\frac{V_{dc}}{V_{rms}}\right)^2 \times 100$$



### RT B: Full Wave Rectifier

centre tapped full wave rectifier that uses two diodes connected to the secondary of a centre tapped transformer, as shown in Fig. 2. The centre tap is usually considered as the ground point or the zero-voltage reference point. As shown in Fig. 2 an AC input voltage is applied to the primary coils of the transformer. The input makes the secondary ends A and B become positive and negative alternatively. For the positive half of the AC signal, the secondary point A is positive, ground point will have zero voltage and D<sub>1</sub> will be forward biased and diode D<sub>2</sub> will be reverse biased.

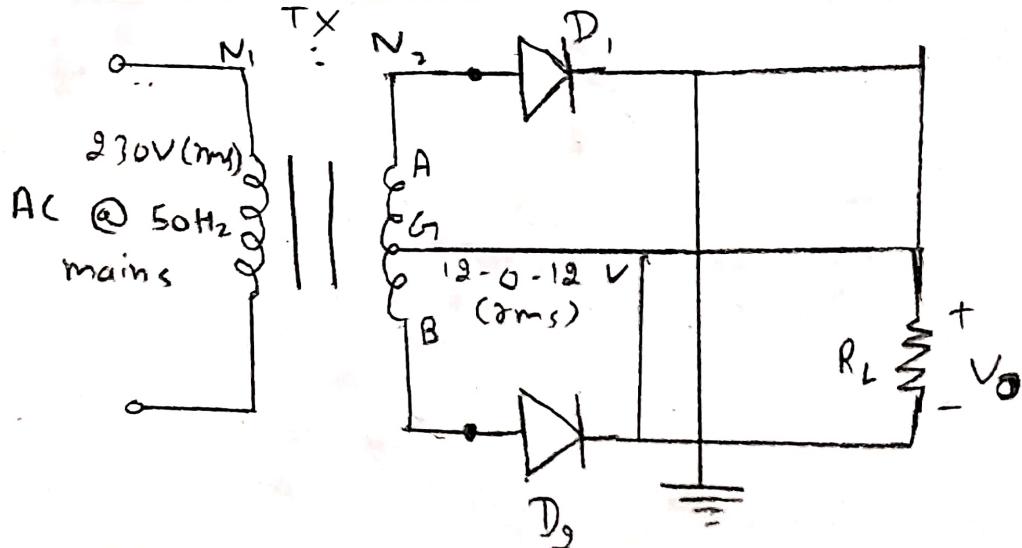


Figure 2: Centre tap full wave Rectifier circuit

1. Set up the circuit as shown in Fig. 2. The transformer TX has rating of 230V to 12.6V, 2A. Take  $R_L = 2\text{ k}\Omega$ . Connect transformer primary to the mains and switch on the mains.  
Display the secondary voltages  $V_{AN}$  and  $V_{BN}$  ( $V_{AN}$  to Ch-1;  $V_{BN}$  to Ch-2) on the oscilloscope. Make sure that both the "probe grounds" are connected to the circuit ground. Sketch the waveforms overlapping, with the same time and amplitude axes. They should be  $180^\circ$  out of phase. Measure the output voltage ( $V_m$  &  $V_{p-r}$ ) at the transformer in the oscilloscope.
2. Display and sketch the full-wave rectified output  $V_o$  across  $R_L$ . Measure the peak voltages in both halves.

FWR  $\rightarrow$

$$V_{BG} = 16.8 \text{ V}$$

$$V_{AC} = 17.2 \text{ V}$$

$$V_{PP} = 34 \text{ V}$$

$$V_m = 16.1 \text{ V}$$

$$V_{P.P.} = 16.3 \text{ V}$$



$$\frac{V_m}{\sqrt{2}} \leq V_{rms} = \frac{16.1}{\sqrt{2}} = 11.38 \text{ V}$$

$$\frac{2V_m}{\pi} \leq V_{AC} = 10.94 \text{ V}$$


$$\sqrt{\left(\frac{V_{rms}}{V_{AC}}\right)^2 - 1} \leq R.F. = \sqrt{\left(\frac{11.38}{10.94}\right)^2 - 1} = 0.45$$

$$\frac{V_{AC}}{V_{rms}} \times 100 \approx n = \left(\frac{10.94}{11.38}\right)^2 \times 100 \approx 90\%$$

Input  $\rightarrow$

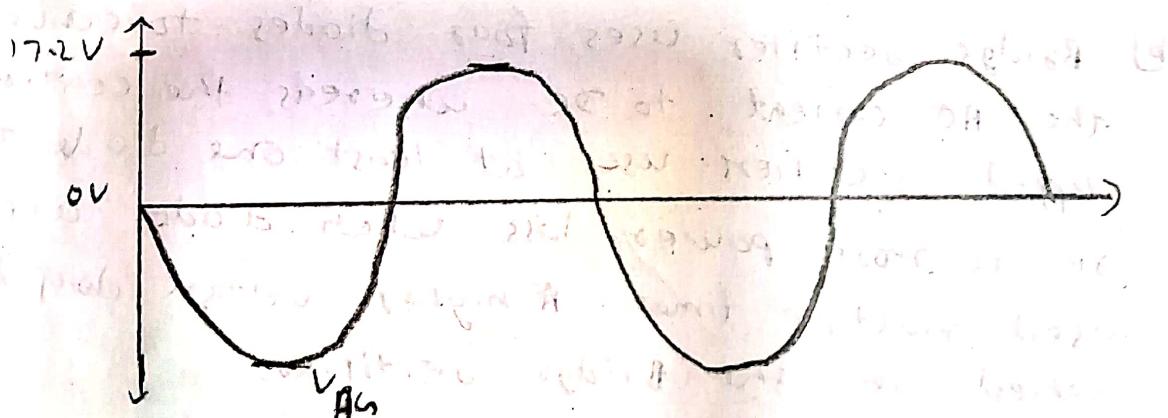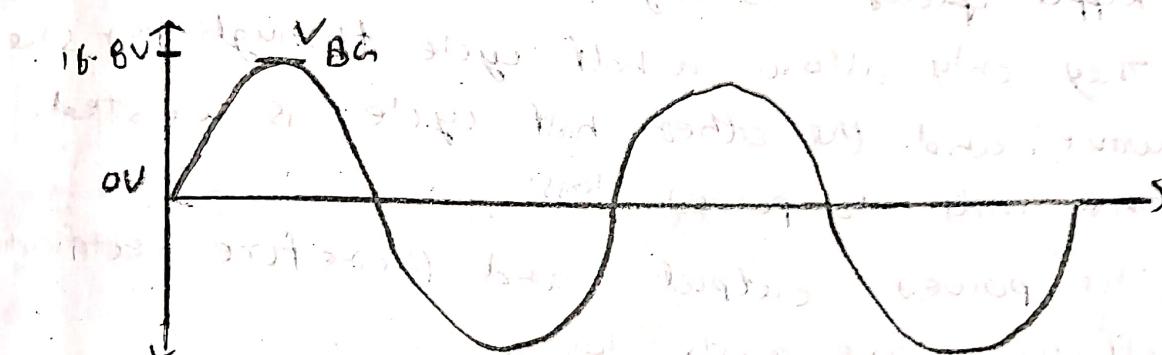

Output  $\rightarrow$

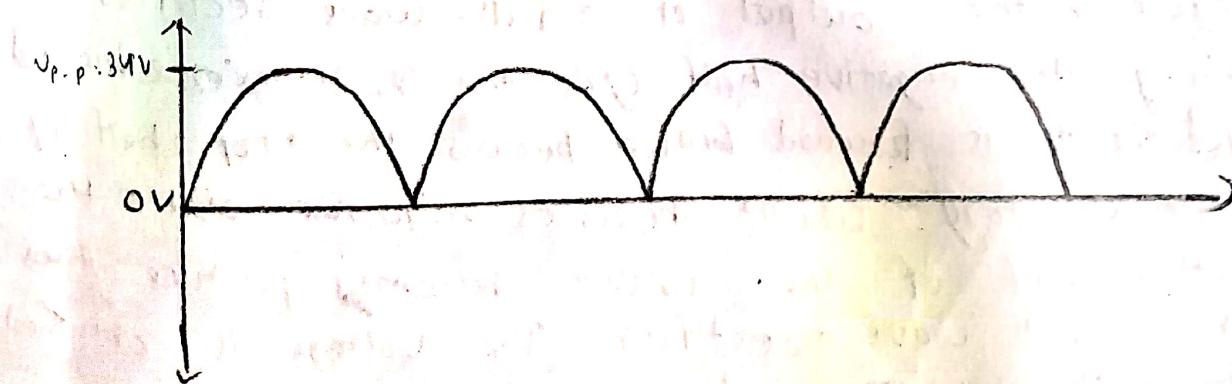

Note:- If the peak amplitudes are not equal,  
what could be the reason?

Questions:-

1. What is the disadvantage of
  - a) A half wave rectifier
  - b) Bridge circuit rectifier as compared to the wt. re tap rectifier.
- a) Disadvantage of half wave rectifier:
  - ① The transformer utilisation factor is zero.
  - ② They produce a low output voltage.
  - ③ Ripple factor is high.
  - ④ They only allow a half cycle through per sine wave, and the other half cycle is wasted. This leads to power loss.
- ⑤ The power output and therefore rectification efficiency are quite low.
- b) Bridge rectifier uses four diodes to convert the AC current to DC whereas the centre-tapped rectifiers uses at least one diode. There is more power loss when diodes are used multiple times. A higher voltage drop is sensed in the bridge rectifiers.
2. How is the negative cycle got inverted to positive cycle in the output of a full-wave rectifier?  
→ During the negative half cycle, the  $D_1$  is reverse biased and the  $D_2$  is forward biased because the top half of the secondary circuit becomes negative and the bottom half of the circuit becomes positive. Thus in a full wave rectifier, DC voltage is obtained for both positive and negative half cycle.

# Experiment-3 (POST LAB REPORT) → [MAYANK]

Half wave and full wave Rectifiers  
circuits with filter

Objectives: Design and analysis of half wave and full wave rectifier circuits with filter.

Materials Required:

- 1.) Breadboard
- 2.) Equipment : Function generator and oscilloscope.
- 3.) Components :
  - a) Transformer : One - 230V to 12 or 12 V
  - b) Diode : Two - IN4007 (Diode voltage drop  $V_D = 0.7\text{V}$ )
  - c) Resistance : Six -  $1\text{k}\Omega$  and  $2.2\text{k}\Omega$
  - d) Capacitance : Two -  $22\mu\text{F}$ ,  $100\mu\text{F}$

General Guidelines / Precautions:

- 1.) Connect the capacitor with the correct polarity. The capacitor being of electrolytic type, it is polarized and will be damaged if connected with incorrect polarity. Similarly, confirm the polarity of diodes before connecting.
- 2.) Keep ground terminals of oscilloscope probes and function generator output connected together throughout the experiment.
- 3.) In an oscilloscope, for higher precision, increase vertical sensitivity (i.e. lower value of volt/div.), especially while measuring small amplitude levels (e.g. ripple voltage). You may need to switch to AC coupling while doing so.
- 4.) In the case full wave rectifier, switch on the main supply to the transformer only after you have made all other connections in order to avoid electric shock.
- 5.) Also, while making any changes in the circuit, switch off the mains supply to the transformer.
- 6.) Make sure that the power lines in the breadboard given on the top and bottom for the power supply must be used and connect to the other parts of the circuit.
- 7.) Switch off the supply to all the equipments before you make any changes in the circuit.

## Half wave rectifier with capacitor filter:-

- 1.) Now connect a capacitor  $C = 22\mu F$  in the circuit with correct polarity as shown in Fig. 1(a).

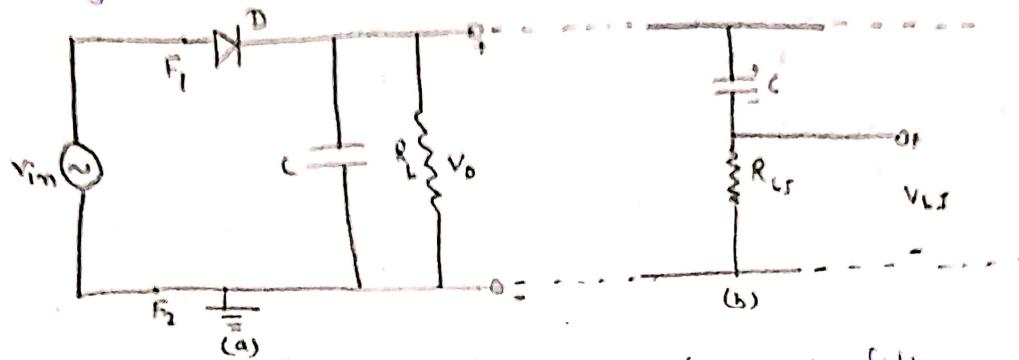


Fig. 1: Half wave rectifier with filter

- 2.) Now display  $V_i$  and  $V_o$  simultaneously on the oscilloscope. Sketch  $V_i$  and  $V_o$  overlapping with the same time and amplitude axes.

- 3.) Measure peak-to-peak ripple voltage on oscilloscope by enlarging  $V_o$  to the maximum extent. You may have to put the input coupling in the AC mode while doing this experiment. See the guidelines given at the end. Repeat steps 2 and 3 for  $R_L = 1k\Omega$  and  $4.7k\Omega$ . Comment on the output waveforms and ripple voltages.

- 4.) Connect a  $R_{L_1} = 5\text{ }k\Omega$  resistance in series with  $C$  of Fig 1(b). The points across this  $R_{L_1}$  are marked as  $p$  and  $q$ . Note: The resistance  $5\text{ }k\Omega$  is chosen small enough not to affect the overall performance of the circuit and at the same time to ensure an appreciable voltage across it. This voltage represents the current flowing through the capacitor.
- 5.) Display and sketch  $V_o$  and  $V_{RL}$  (i.e. Voltage across  $R_{L_1}$  between 'p' and 'q') are below the others with identical time axes. mask the ground reference line.

## Full wave rectifier with capacitor filter:-

- 1.) Setup the circuit as shown in fig. 2 with the capacitor  $C$ . The transformer  $T_X$  has rating of 230V. to 12 or 12V, 1A. Take  $R_L = 1k\Omega$ . Connect transformer primary to the mains and switch on the mains. Display the secondary voltages  $V_{A2}$  and  $V_{B2}$  ( $V_{A2}$  to ch-1,  $V_{B2}$  to ch-2) on oscilloscope. Make sure that both the "probe grounds" are connected to the circuit's ground. Sketch the waveforms overlapping, with the same time and amplitude axes. They should be  $180^\circ$  out of phase. Measure the output voltage ( $V_m$  and  $V_{P-P}$ ) of the transformer in the oscilloscope.

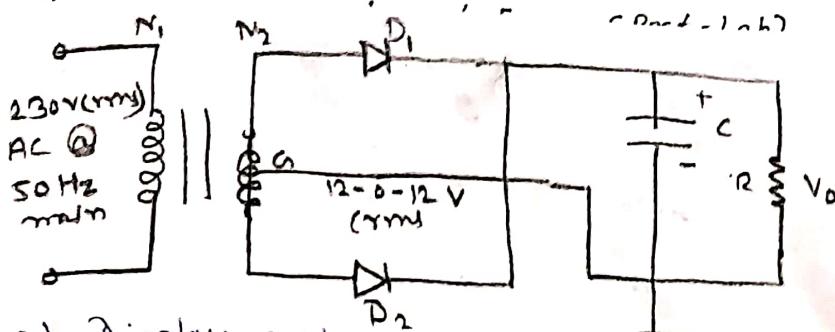


Fig-2:  
Full wave rectifier  
with filter.

- 2.) Display and sketch the full-wave rectified output  $V_0$  across  $R_L$ . Measure the peak voltages in both halves. Note: If the peak amplitudes are not equal, what could be the reason?
- 3.) Now connect  $C = 100\mu F$  as shown in fig.2 (Read the guideline 3). Sketch  $V_0$  and measure  $V_r$  (Peak-to-Peak ripple voltage). Set the oscilloscope channel to AC coupling and increase vertical sensitivity (decrease  $V/div$ ) while measuring  $V_r$ .
- 4.) Calculate ripple factor by using the formulas  
Ripple factor  $\gamma = \frac{1}{4\sqrt{3}f.C.R}$

Observations:-


### 1) For half wave rectifier:-

$$\text{Input : } V_{pp} = 9.60 \text{ V}$$

$$V_m = 4.40 \text{ V}$$

$$\text{frequency} = 500 \text{ Hz}$$

Input wave forms:-

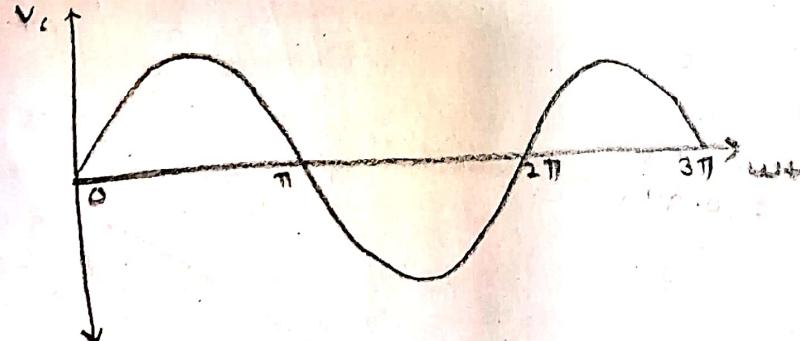

Output :-

$$V_r (P-P) = 200 \text{ mV}$$

$$V_{rms} (\text{rms}) = \frac{V_r (P-P)}{2\sqrt{3}}$$

$$= 0.57 \text{ V}$$

$$\checkmark \gamma = \frac{1}{2\sqrt{3} \times 500 \times 1000 \times 22 \times 10^{-6}}$$

$$\gamma = \frac{1}{2\sqrt{3} f R C}$$

$$= \frac{1}{2.2\sqrt{3}}$$

$$= 0.0262$$

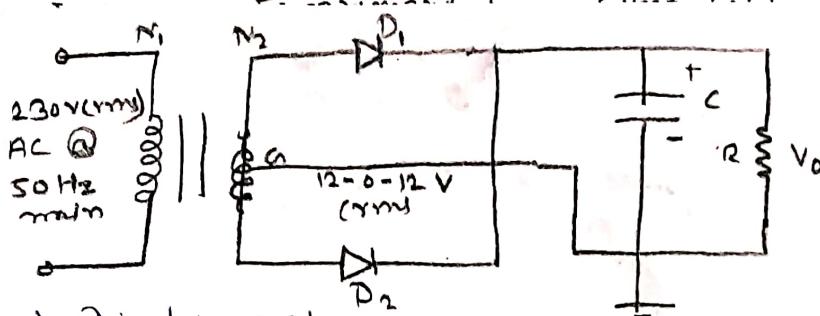


Fig-2:  
Full wave rectifier  
with filter


- 2.) Display and sketch the full-wave rectified output  $V_o$  across  $R_L$ . Measure the peak voltages in both halves. Note: If the peak amplitudes are not equal, what could be the reason?
- 3.) Now connect  $C = 100\mu F$  as shown in fig.2 (Read the guideline 3). Sketch  $V_o$  and measure  $V_r$  (Peak-to-Peak ripple voltage). Set the oscilloscope channel to AC coupling and increase vertical sensitivity (decrease V/div) while measuring  $V_r$ .
- 4.) Calculate ripple factor by using the formulas  
Ripple factor  $= \frac{1}{\sqrt{3} f_c \cdot \gamma}$

Observations:-

#### 1) For half wave rectifier:-

Input :-  $V_{pp} = 9.60\text{ V}$   
 $V_m = 4.40\text{ V}$   
 frequency =  $500\text{ Hz}$

Input wave form:-

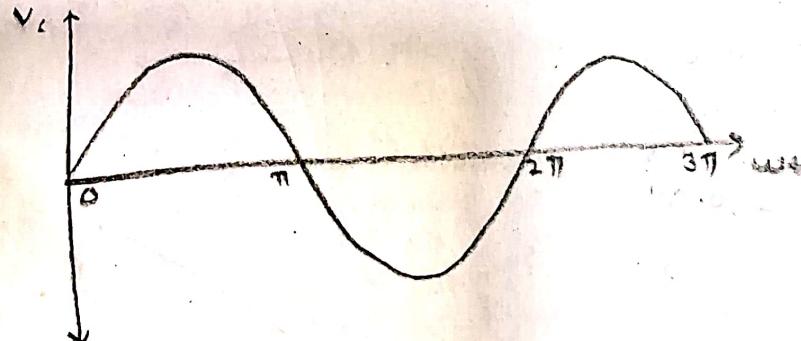

Output :-

$$V_r(p-p) = 200\text{ mV}$$

$$V_{rr}(rms) = \frac{V_r(p-p)}{2\sqrt{3}}$$


$$\checkmark \quad \frac{1}{2\sqrt{3} \times 500 \times 1000 \times 22 \times 10^{-6}} = 0.57\text{ V}$$

$$\gamma = \frac{1}{2\sqrt{3} f R L}$$

$$= \frac{1}{22\sqrt{3}}$$

$$= 0.0262$$

## Output wave form:-

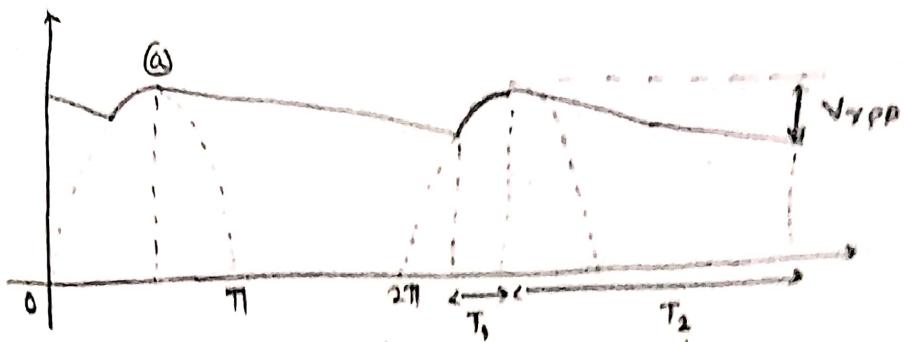

## 2.1 For full wave rectifier:-


Input :

$$V_{A \text{ a(m)}} = 16.4 \text{ V}$$

$$V_{B \text{ a(m)}} = 16.4 \text{ V}$$

$$V_{pp} = 32.8 \text{ V}$$

## Input wave form:-

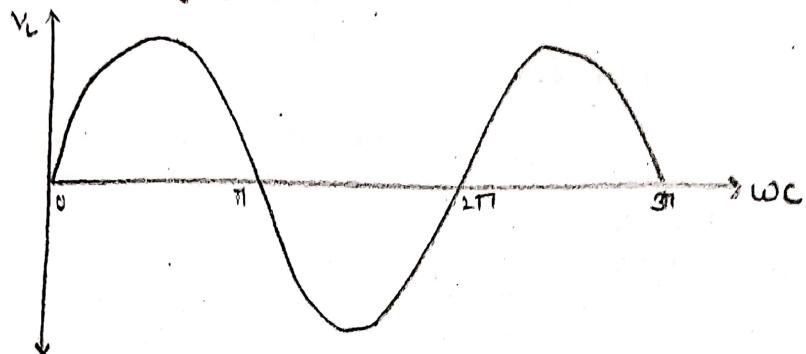

## Output:-

$$V_r (P-P) = 1.18 \text{ V}$$

$$V_r (\text{rms}) = \frac{1.18}{\sqrt{3}}$$

$$= 0.34 \text{ V}$$


$$V_m = 14.3 \text{ V}$$

$$r = \frac{1}{4\sqrt{3} f R C}$$

$$= \frac{1}{4\sqrt{3} \times 1000 \times 100 \times 10^{-6} \times 50}$$

$$= 0.028$$

## Output wave form:-

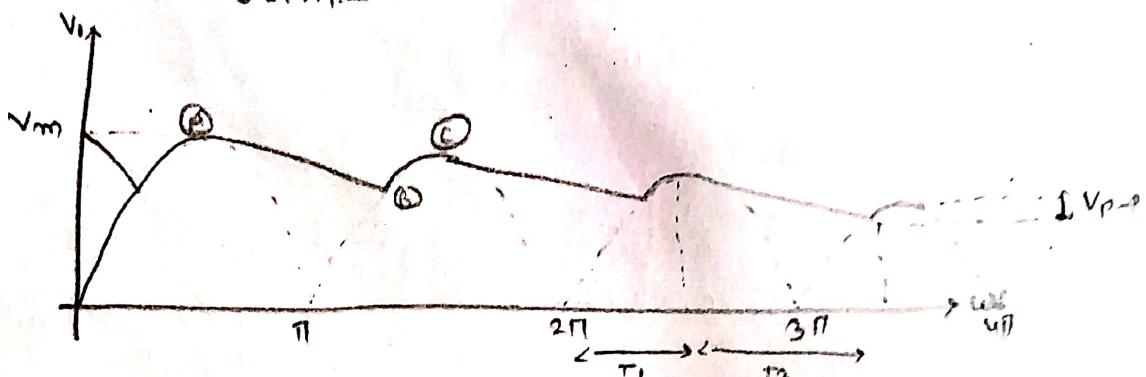

## Post LAB QUESTIONS:-

(Post-Lab)

→ Abhishek

Ques. 1. Define peak inverse voltage (PIV)? And write its value for full wave rectifier?

Ans. The peak inverse voltage is either the specified maximum voltage that a diode rectifier can block or alternatively, the maximum voltage that a rectifier needs to block in a given circuit. PIV for full wave rectifier is  $2V_{max}$ .

Ques. 2. What is the necessity of the transformer in the rectifier circuit?

Ans. 1.) It is used to change the voltage level from the 115V AC to another level, either higher or lower, to accommodate the needs of the rest of the circuit.

2.) It provides isolation between the power mains and the circuit power for safety reasons.

Ques. 3. Explain how capacitor helps to improve the ripple factor?

Soln:- The ripple can be reduced by smoothing capacitors which converts the ripple voltage into a smoother dc voltage. Aluminium electrolytic capacitors are widely used for this and have capacitances of 100μF or more. The repeated dc pulses charges the capacitor to peak voltage.

Conclusion:-

In this experiment, we have learnt design and analysis of half-wave and full-wave rectifier circuits with filters in depth. We learnt about their functions, mechanism and at what input what output will going to be coming and also tested their mechanics and structure clearly.

Rahul  
6/7/24

## Experiment 4 : Clipping and Clamping Circuits

Objective & Design and analysis of wave shaping Circuits.

### Materials Required

1. Breadboard.
2. Equipment's function generator and oscilloscope.
3. Components :-

- Diode : Two - 1N4007 (Diode voltage drop  $V_D = 0.7V$ )
- Zener Diode : One - (Zener voltage  $V_Z = 3.9V$ )
- Resistance : Three - 1K $\Omega$ , 2.2K $\Omega$ , 100K $\Omega$ .
- Capacitor : One - 22 uF.

### I General Preparation :-

1. Connect the capacitor with correct polarity. The Capacitor being of electrolytic type, it is polarized, and will be damaged if connected with incorrect polarity. Similarly, confirm the polarity of the diodes before connecting.
2. Keep ground terminals of oscilloscope probes and function generator output connected together throughout the experiment.
3. Make sure that the power lines in the breadboard open on the top and bottom for the power supply must be used and from them you connect to the other parts of the circuit.
4. ~~switch off the supply to all the equipment before you make any changes in the circuit.~~

## II PART A : Clipping Circuit

Clippers are the circuit that employ diodes to remove a portion of an input signal without distorting the remaining part of the applied wave form. A clipper can serve as a protective measure, preventing a signal from exceeding the clip limit. A practical application of a clipper is to prevent an amplified speech signal from overdriving a radio transmitter. Over driving the transmitter generates spurious radio signals which causes interference with other station. The clipper is a protective measure.

### II.I Clipping Circuit - Positive Clipping

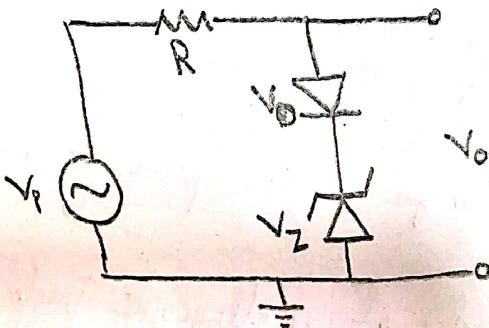


Fig. 1 : Positive Clipper

1. Connect the circuit as shown in fig. 1 with  $R = 2.2\text{ k}\Omega$ .
2. Set the function generator to get 20V peak-to-peak sine wave at 500Hz frequency. Observe the function generator output on the oscilloscope and verify the wave generation.
3. Connect the function generator output to the circuit as shown fig. 1.
4. Display and sketch  $V_s$  and  $V_o$  one below the other with identical time and amplitude axes.
5. Superimpose the two waveforms  $V_s$  and  $V_o$  and observe.

6. Set the oscilloscope in X-Y mode ( $V_x$  to Ch2  $\circ$  X-input and  $V_y$  to Ch1  $\circ$  Y-input) and sketch  $v_o$  versus  $v_i$  with equal x and y scales. Label the graph and ticks on the axes.



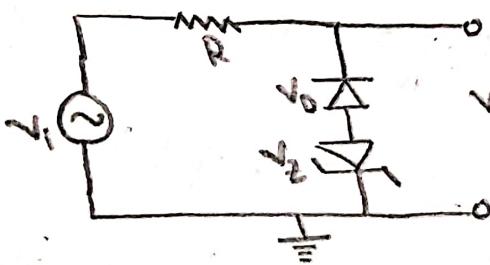


Fig 1.2  $\circ$  Negative Clipper


Expected waveforms at step no. 4

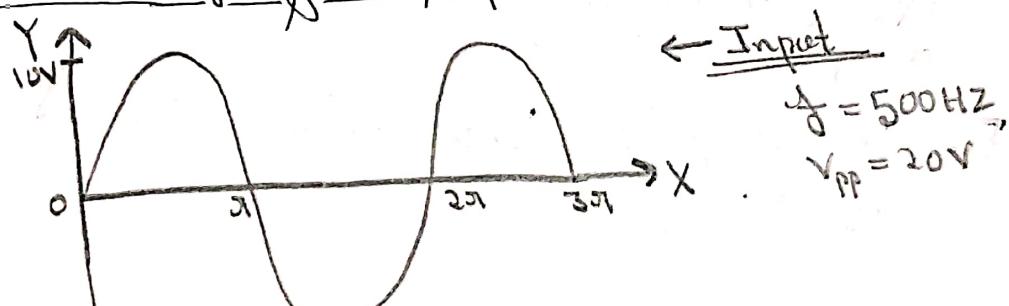

Input sinusoidal signal

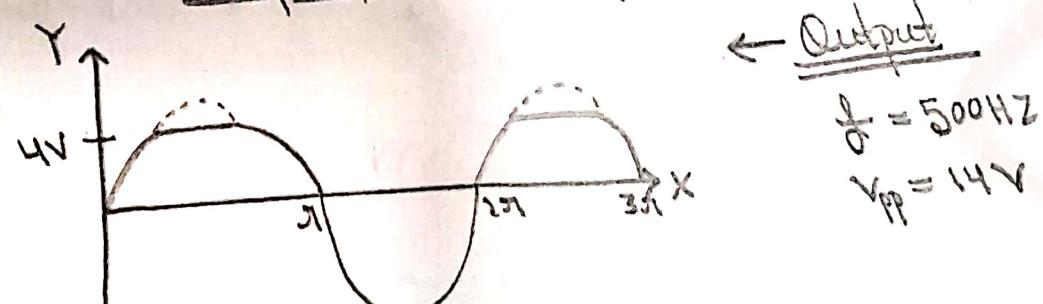





Positive Clipper

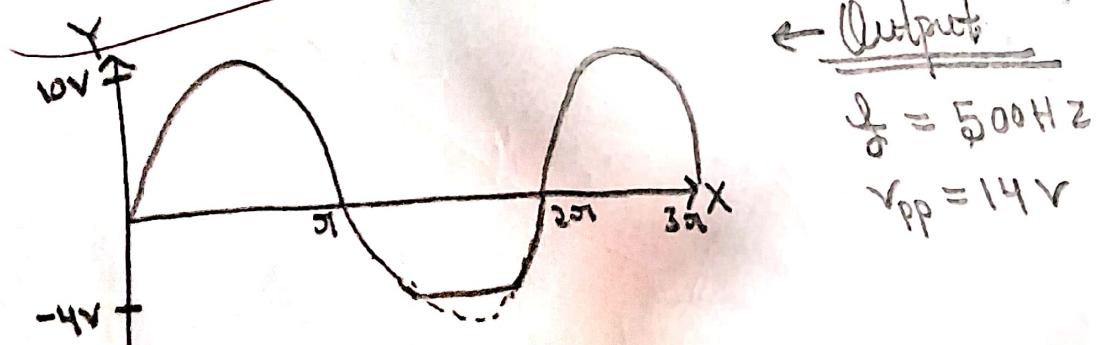


Negative Clipper

### III. I. 1 Symmetrical Clipping Circuit

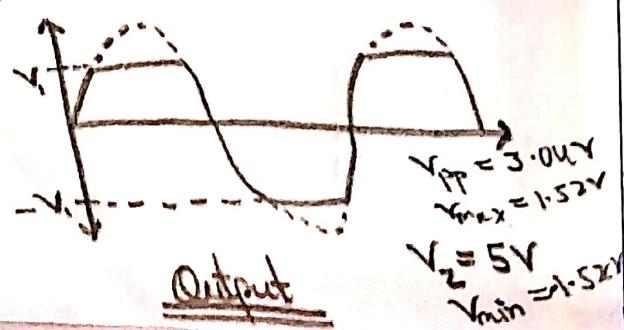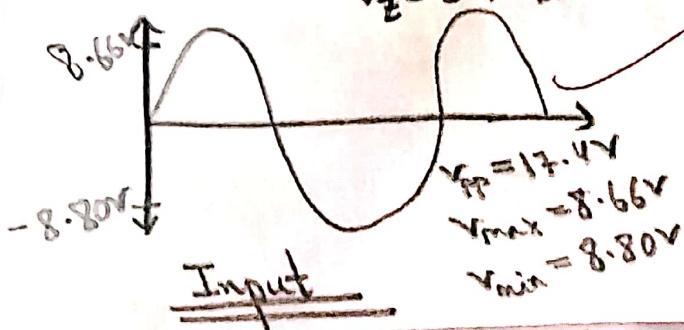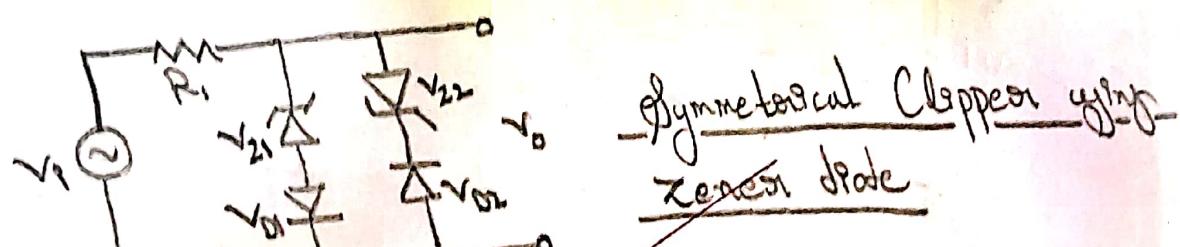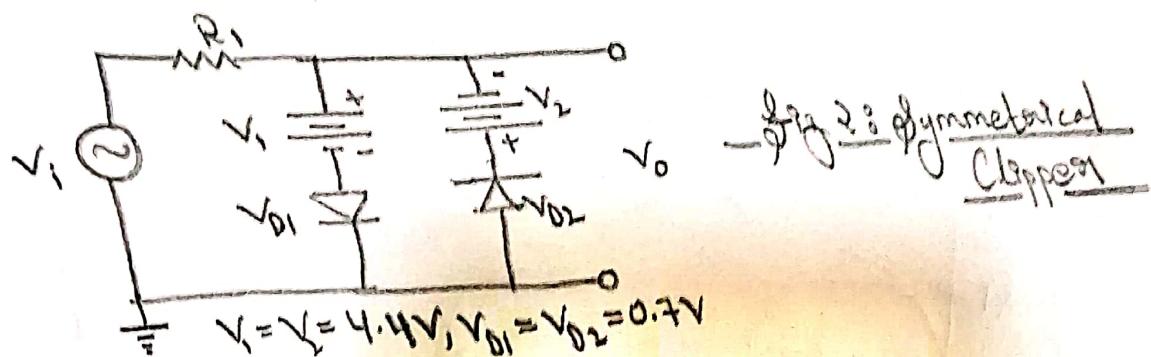1. Connect the circuit as shown in Fig. 2 with  $R_1 = 2\text{ k}\Omega$ .
2. Set the function generator to get 20V peak-to-peak sine wave at 500Hz frequency. Observe the function generator output on the oscilloscope and read off the generation.
3. Connect the function generator output to the circuit as shown in Fig. 2.
4. Display and sketch  $v_1$  and  $v_o$  one before the other with identical time and amplitude axes.
5. Superimpose the two waveforms  $v_1$  and  $v_o$  and observe.



Input :-

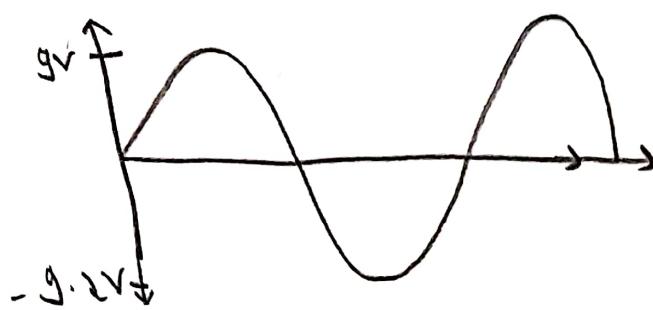


$$v_{pp} = 18\text{ V}$$

$$v_{max} = 9\text{ V}$$

$$v_{min} = -9\text{ V}$$

Output :-

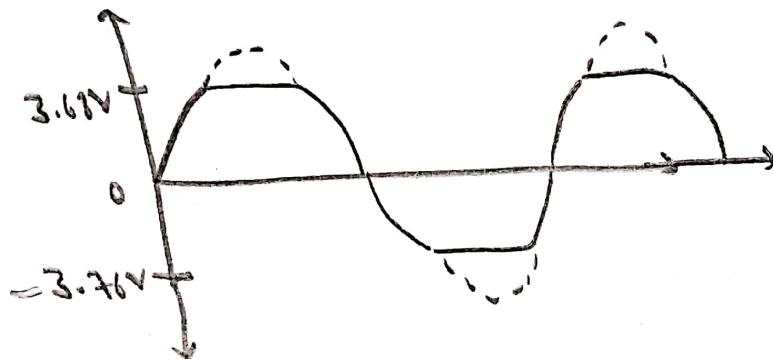


$$v_{pp} = 7.44\text{ V}$$


$$v_{max} = 3.87\text{ V}$$

$$v_{min} = -3.76\text{ V}$$

Zener Reverse :-

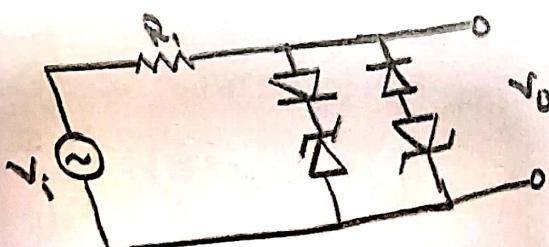

Input :-

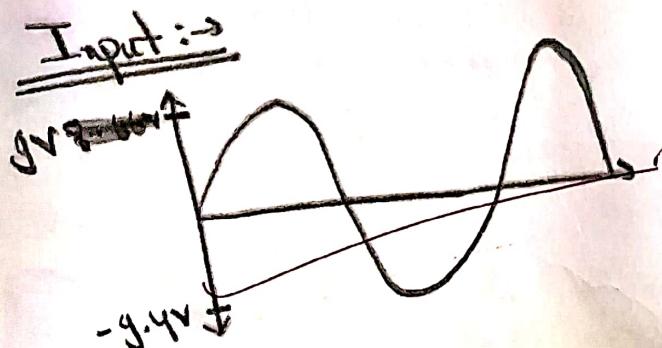


$$v_{pp} = 18.4\text{ V}$$

$$v_{max} = 9\text{ V}$$

$$v_{min} = -9.4\text{ V}$$

Output :-

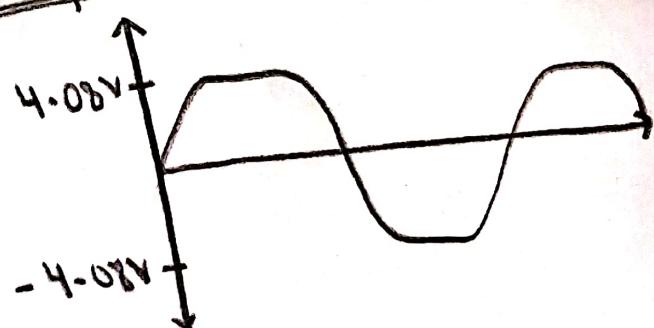

$$v_{pp} = 8.16\text{ V}$$

$$v_{max} = 4.08\text{ V}$$

$$v_{min} = -4.08\text{ V}$$

### III Clamper Circuits

Clamping is a process of introducing a DC level into a signal. Clamper circuit consists of diode and capacitor that shifts the input waveform by different DC level, without changing the appearance of the applied waveform.

1. When the diode is forward biased, it will conduct and charge the capacitor. The output voltage across the diode is zero.

2. The capacitor is charged to peak input voltage quickly because of small time constant of the circuit.

3. Connect the circuit as shown in Fig. 3 with  $R_L = 100\text{ k}\Omega$ .

4. During the -ve cycle when diode is reverse biased, the diode becomes to its off state. In this case, the output voltage is equal to the sum of the input voltage and the voltage across the terminals of the capacitor which have the same polarity with each other.

5. Set the function generator to get 20V peak-to-peak square with a period of 2ms. Observe the function generator output on the oscilloscope and verify square wave generation.

6. Connect the function generator output to the circuit as shown in Fig. 3

7. Display and sketch  $v_o$  and  $v_o'$  one below the other with identical time and amplitude axes.

8. Superimpose the two waveforms  $v_o$  and  $v_o'$  and observe.

Negative →



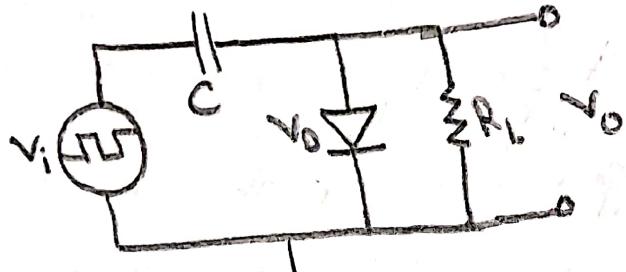


fig 3: Clamping Circuit


Input : →

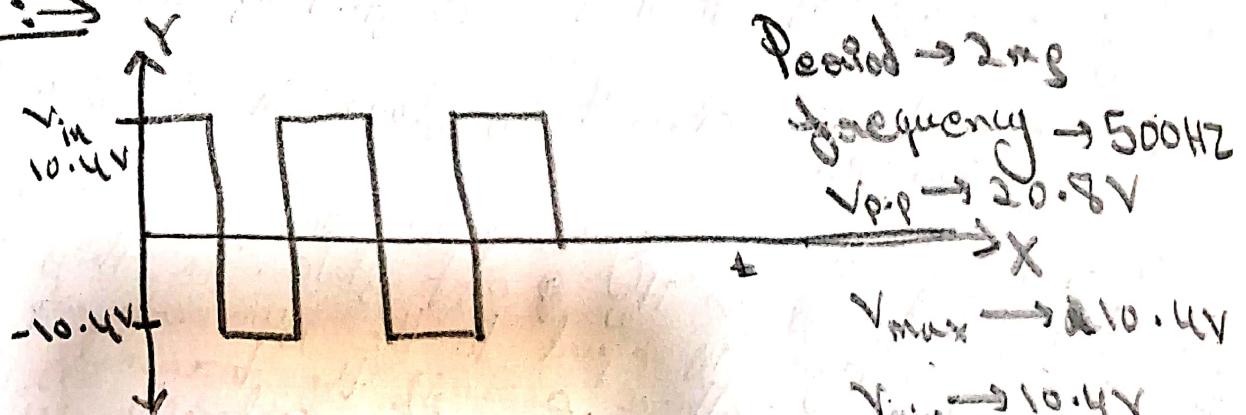


Output : →

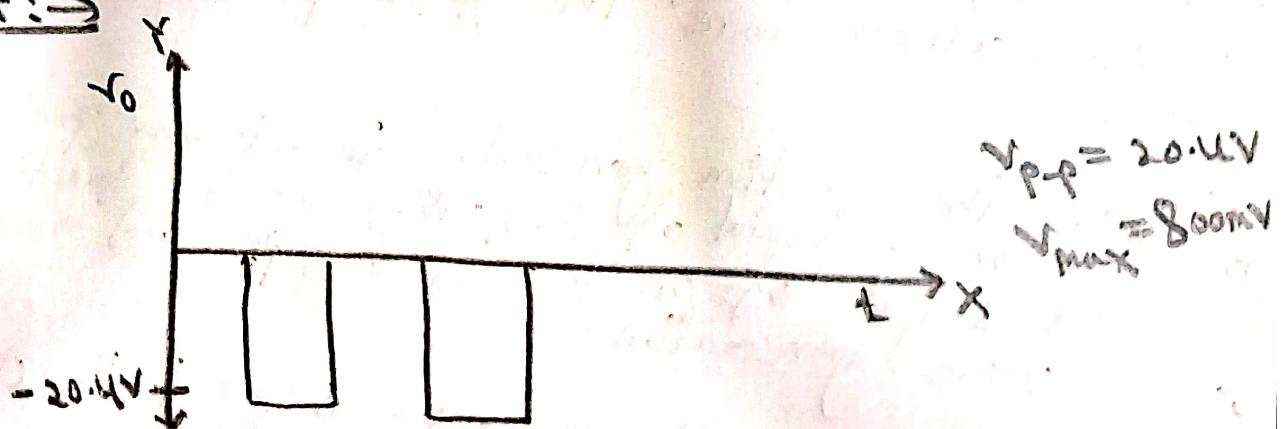

## Positive Clamper

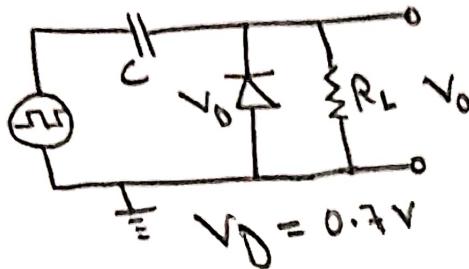


Input :  $\rightarrow$

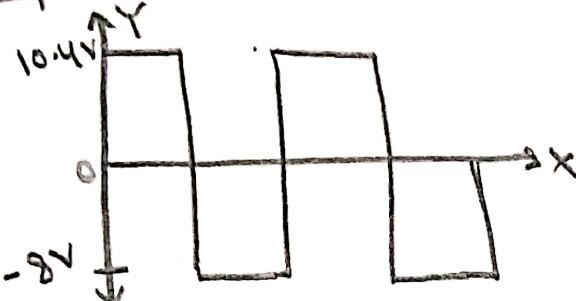

$$\begin{aligned}f &= 500 \text{ Hz} \\V_{pp} &= 18.4V \\V_{max} &= 10.4V \\V_{min} &= 8V\end{aligned}$$

Output :  $\rightarrow$

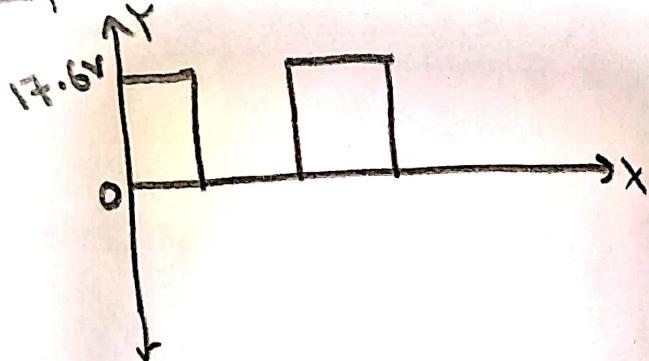

$$\begin{aligned}f &= 500 \text{ Hz} \\V_{pp} &= 18.8V \\V_{max} &= 17.6V \\V_{min} &= 1.2V\end{aligned}$$

Conclusion :  $\rightarrow$

Clippers reduce the amplitude while clamps shift the DC level. Both are useful circuits in various high-level applications of electronics as well as communication. Clippers are used in communication circuits such as transmitters and receivers.

Kiran  
27/2/2022

Operational Amplifier

Objective →

Analyzing of inverting and non-inverting OP-Amp

Circuits:

Material Required →

1- Bread board

2- Equipment : Multi-output DC power supply, Function

3- Components: Generator, Oscilloscope

• OP-Amp : One - LM741.

• Resistance: Five -  $1\text{ k}\Omega$  (2 nos),  $10\text{k}\Omega$  (1 no),  $12\text{k}\Omega$  (2 nos),  
 $100\text{k}\Omega$  (2 nos).

I General Guidelines / Prequestions :

- 1- The Op-amp generally works on split power supply (e.g.  $\pm 12\text{V}$ ). Both positive and negative power supplies must be present whenever op-amp is powered. The range of power supply is from  $\pm 5\text{V}$  to  $\pm 15\text{V}$ . Do not forget to connect the common terminal of the power supply to the ground on the breadboard.
- 2- Connecting only one side of power supply or interchanging positive and negative power supplies damages the op-amp.
- 3- For connecting power supply, you have to follow the procedure as given below.
  - (a) Disconnect the power supply to op-amps.
  - (b) Switch on the power supply.
  - (c) Set the output voltage as required (e.g.  $\pm 12\text{V}$ ).

- (d) Switch off the power supply.
- (e) Connect the power supply to op-amps.
- (f) Switch on the power supply.

4. For any IC, never exceed the input voltage beyond the power supply limits.

5. Keep ground terminals of the oscilloscope probe, and function generator output and power supply common connected together through out the experiment.

6. Make sure that the power lines in the breadboard given on the top and bottom for the power supply must be used and from their you connect to the other parts of the circuit.

7. Switch off the supply to all the equipments before you make any changes in the circuit.

## II Operational Amplifiers

An operational amplifier is a very high gain amplifier having very high input impedance ( $2 \text{ M}\Omega$  for LM741), low output impedance (less than  $1 \text{ }\Omega$ ), high open loop gain (200000 for LM741) and high unity gain bandwidth ( $1.5 \text{ MHz}$  for LM741). The two op-amp circuits are most widely used; one is inverting amplifier and the other one is non-inverting amplifier. The inverting op-amp will have  $V_o$  is equal to minus  $KV_i$ , where the minus sign comes because of the phase inversion. The output will be inverted by  $180^\circ$  degrees.

The Inverting amplifier is the most basic op-amp circuit. It uses the simple resistive feedback network to stabilize the overall voltage gain. The gain of the non-inverting amplifier is positive i.e.  $V_o$  is equal to  $KV_i$ .

II. I

### PART A: Inverting Amplifier

Obtain theoretical values of  $V_o/V_i$  for step 3 of Part A. Do this for Part B also.

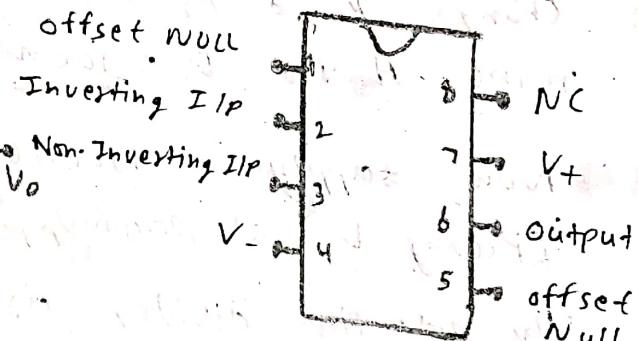
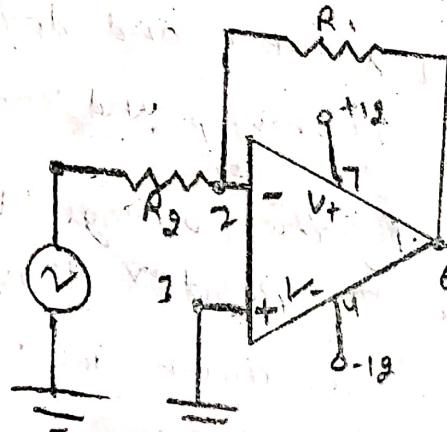


Fig. 4: Inverting Amplifier

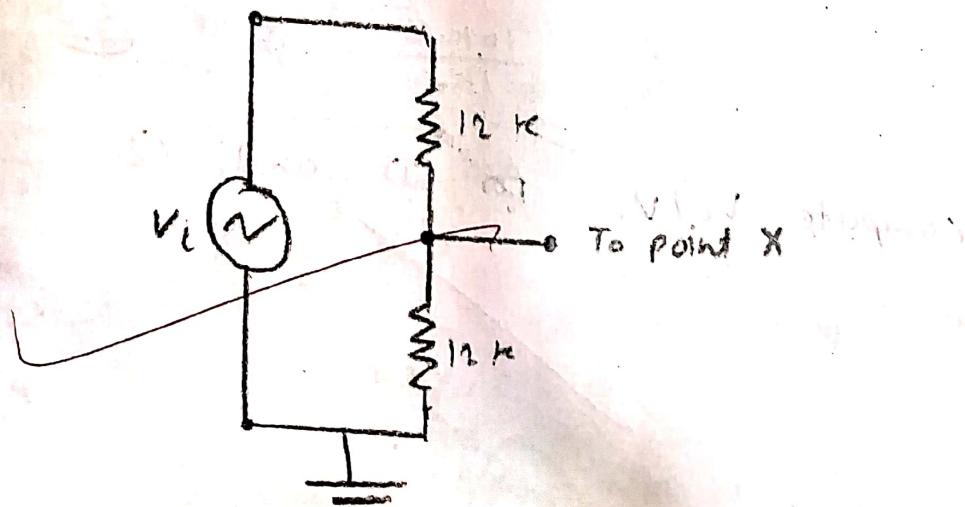



Fig. 2: Voltage Divider.


- 1- Assemble the circuit shown in Fig 2 with  $R_1 = 10\text{ k}\Omega$  and  $R_2 = 1\text{ k}\Omega$ . Make sure the power supply ground is connected to the circuit ground.
2. Apply  $200\text{ mV}_{\text{p-p}}$ ,  $2\text{ kHz}$  sine wave at  $V_i$  from the function generator and see the output in the oscilloscope.
3. Observe  $V_o$  and  $V_i$ , and determine voltage gain  $A = V_o/V_i$ . Also obtain  $A$  for  $V_i = 100\text{ mV}_{\text{p-p}}$  and  $300\text{ mV}_{\text{p-p}}$ .
4. Change  $R_1$  &  $R_2$  to  $100\text{ k}\Omega$  &  $10\text{ k}\Omega$  and determine  $A$  for  $V_i = 100\text{ mV}_{\text{p-p}}$ ,  $200\text{ mV}_{\text{p-p}}$  and  $300\text{ mV}_{\text{p-p}}$ .
5. Now supply a fraction of the voltage  $V_i$  (keeping  $V_i$  at  $200\text{ mV}_{\text{p-p}}$ ) to the point X through the potential divider circuit as shown in Fig.2 and note the values of  $V_o$  for

$$\frac{R_1}{R_2} = \frac{100\text{ k}\Omega}{10\text{ k}\Omega} \quad \text{--- (1)}$$

$$\frac{R_1}{R_2} = \frac{10\text{ k}\Omega}{1\text{ k}\Omega} \quad \text{--- (2)}$$

Compute  $V_o/V_i$  for (1) and (2)

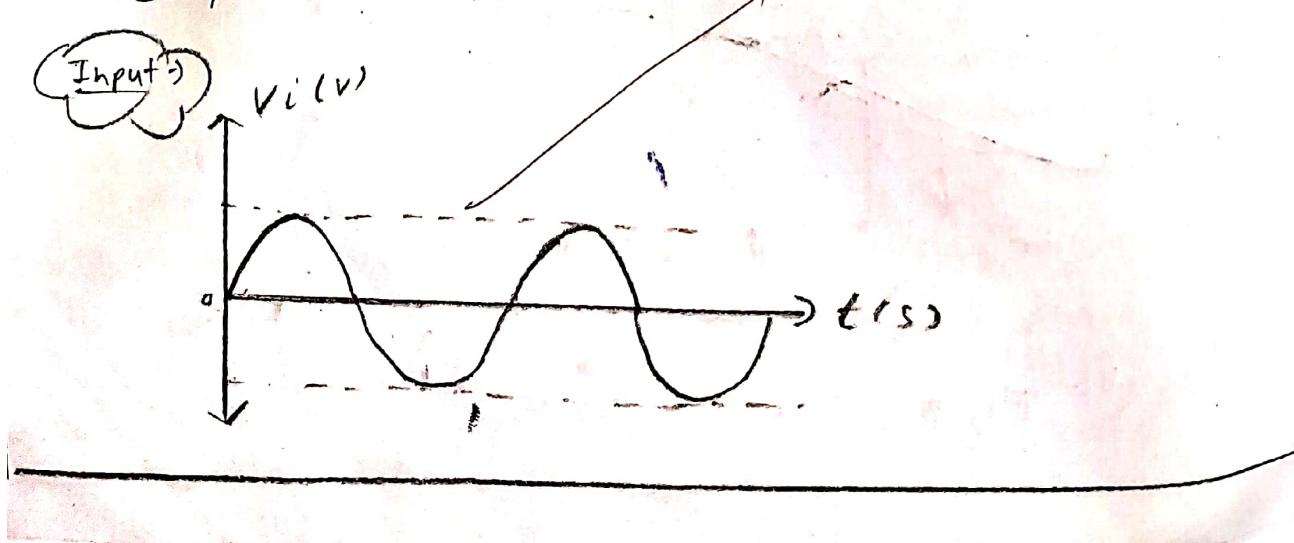

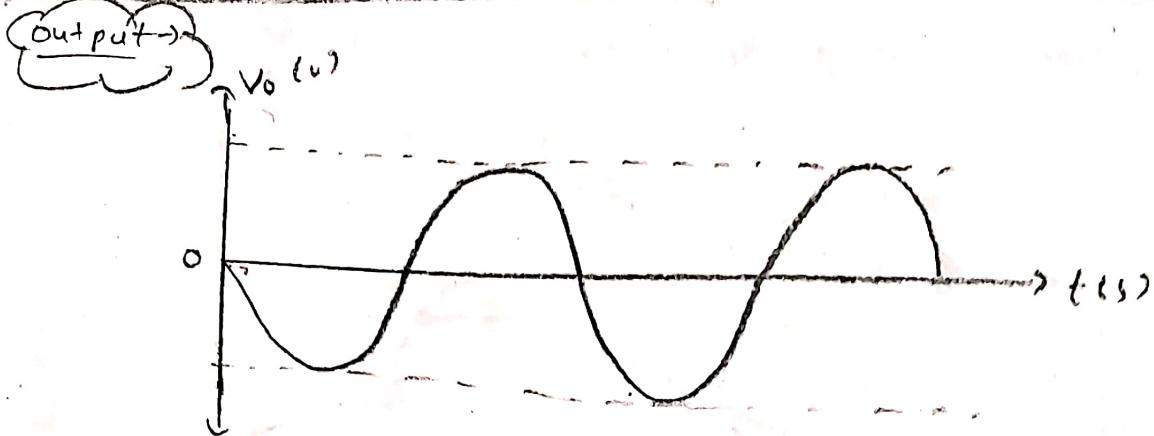

Result  $\rightarrow$

$$\textcircled{1} \quad R_1 = 10 \text{ k}\Omega, \quad R_2 = 1 \text{ k}\Omega$$

$V_{P-P}$ Input	$V_{P-P}$ Output	$A = \frac{V_o}{V_i}$
100mV	8.6mV	10.1
200mV	16.9mV	10.1
300mV	25.6mV	10.1

$$\textcircled{2} \quad R_1 = 100 \text{ k}\Omega, \quad R_2 = 10 \text{ k}\Omega$$

$V_{P-P}$ Input	$V_{P-P}$ Output	$A = \frac{V_o}{V_i}$
100mV	1.09V	10.9
200mV	2.08V	10.4
300mV	3.08V	10.2

Using Voltage divider

$$\textcircled{1} \quad R_1 = 100 \text{ k}\Omega, \quad R_2 = 10 \text{ k}\Omega$$

$$V_i = 2.10 \text{ mV}, \quad V_o = 6.64 \text{ mV}, \quad A = \frac{6.64}{2.10} = 3.16 \text{ (with } 6.64)$$

$$\textcircled{2} \quad R_1 = 10 \text{ k}\Omega, \quad R_2 = 1 \text{ k}\Omega$$

$$V_i = 212 \text{ mV}, \quad V_o = 158 \text{ mV}, \quad A = \frac{158}{212} = 0.74$$

PART 'B': Non-Inverting Amplifier

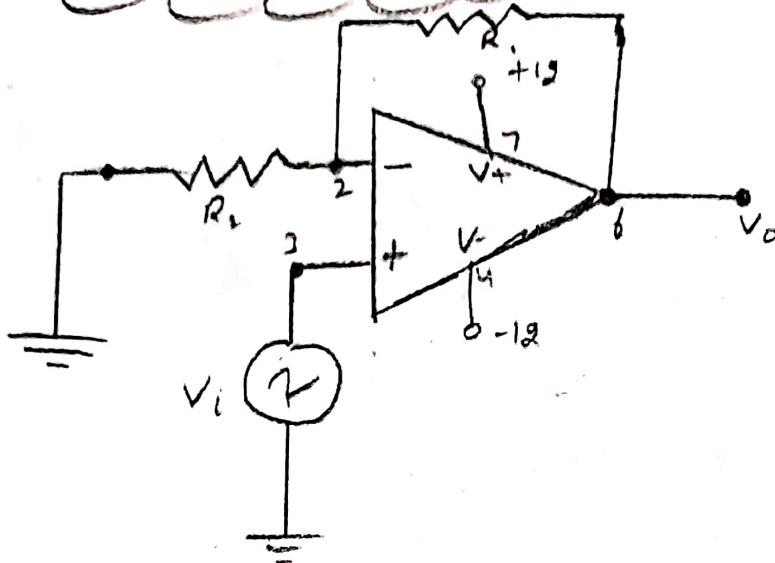


Fig. 3: sym Non-Inverting Amplifier


- 1- Assemble the circuit shown in Fig. 3 with  $R_1 = 10\text{k}\Omega$  and  $R_2 = 1\text{k}\Omega$ , make sure the power supply ground is connected to the circuit ground.
- 2- Apply  $200\text{mV}_{\text{p-p}}$ ,  $2\text{kHz}$ , sine wave at  $V_i$  from the function generator and see the output on the oscilloscope.
- 3- Observe  $V_o$  and  $V_i$ , and determine voltage gain  $A = V_o/V_i$ , Also obtain  $A$  for  $V_i = 100\text{mV}_{\text{p-p}}$  and  $300\text{mV}_{\text{p-p}}$ .
- 4- Change  $R_1$  &  $R_2$  to  $100\text{k}\Omega$  &  $10\text{k}\Omega$  and determine  $A$  for  $V_i = 100\text{mV}_{\text{p-p}}$ ,  $200\text{mV}_{\text{p-p}}$  and  $300\text{mV}_{\text{p-p}}$ .
- 5- Now apply a fraction of the voltage  $V_i$  (keeping  $V_i$  at  $200\text{mV}_{\text{p-p}}$ ) to the point X through the potential divider circuit as shown in Fig. 2 and note the values of  $V_o$  for

$$\frac{R_1}{R_2} = \frac{100\text{k}\Omega}{1\text{k}\Omega} - \textcircled{1}$$


$$\frac{R_1}{R_2} = \frac{1\text{k}\Omega}{10\text{k}\Omega} - \textcircled{2}$$

Compute.  $V_o/V_i$  for  $\textcircled{1}$  and  $\textcircled{2}$  for various values.

Input ->

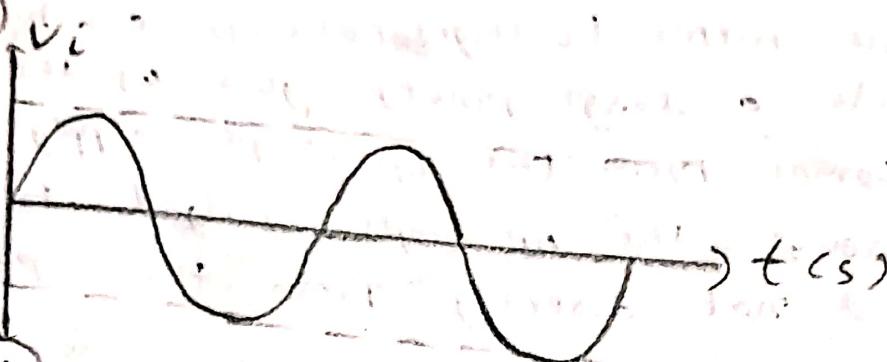

Output ->

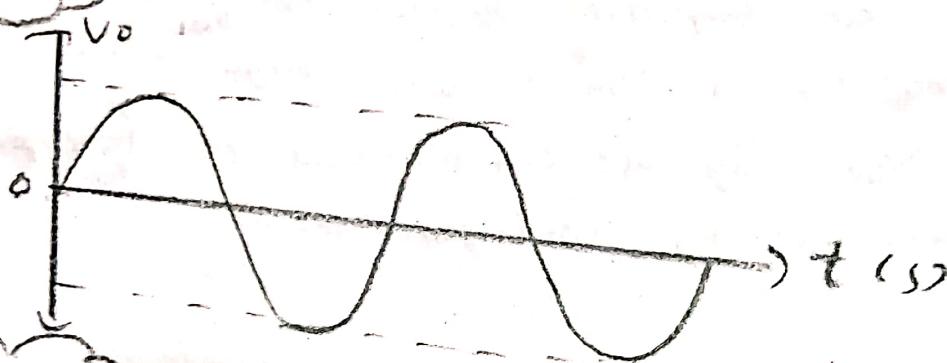

Results ->

$$\textcircled{1} R_1 = 10\text{k}\Omega$$

$$R_2 = 1\text{k}\Omega$$

$V_i$	$V_o$	$A = \frac{V_o}{V_i}$
108mV	1.2V	10.8
208mV	2.32V	10.6
304mV	3.4V	10

$\approx 10$

$$\textcircled{2}$$

$$R_1 = 100\text{k}\Omega, R_2 = 10\text{k}\Omega$$

$V_i$	$V_o$	$A = \frac{V_o}{V_i}$
112mV	1.16V	10.35
204mV	2.28V	10.9
308mV	3.4V	10.7


$\approx 10$

Note :

- (a) For a source with high internal impedance which config. (inverting or non-inverting) will be suitable for design. ing a good amplifier?
- Non-inverting Operational Amplifier Voltage follower.
- As the input impedance is extremely high, the unity gain buffer (voltage follower) can be used to provide a large power gain as the extra power comes from the op-amps supply rails and through the op-amps output to the load and not directly from the input.

- (b) Design an Amplifier System to obtain a gain of -50 for a source with high internal resistance. You may use combinations of inverting and non-inverting configurations?

→

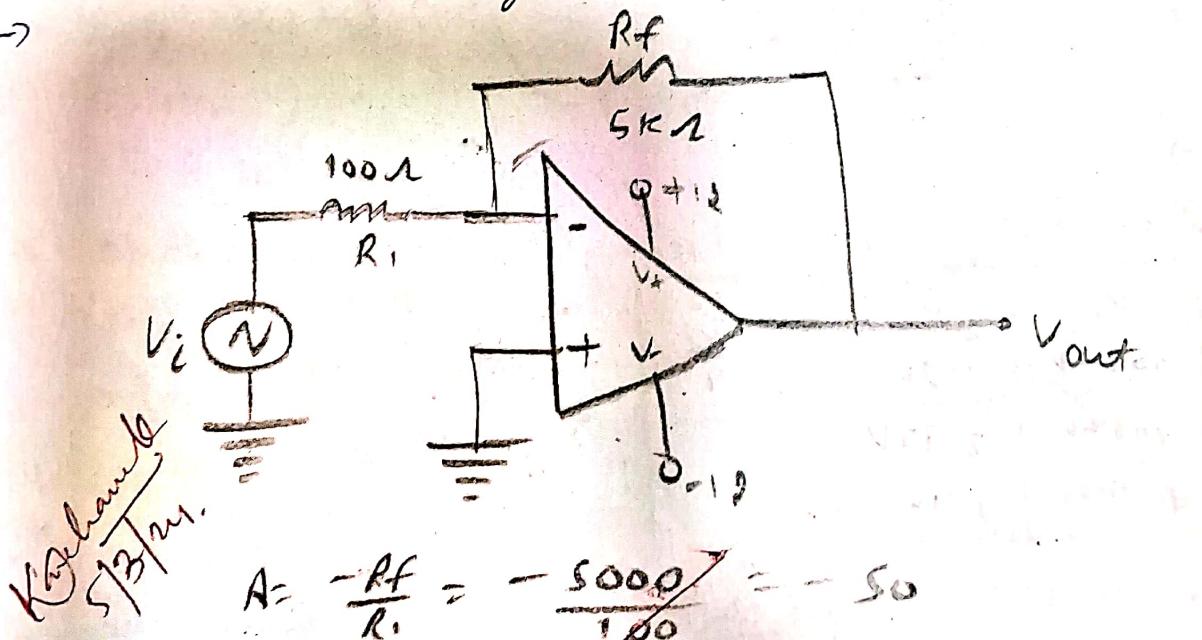

Conclusion :

In this experiment we have learnt the inverting and non-inverting OP-Amp circuits.

Objective:- Designing a voltage follower, Integrator, Differentiator, for and precision Rectifier for a small AC Signal.

Material Required:-

- 1- Bread board
- 2- Equipment: Multi output DC power supply, function generator, oscilloscope.
- 3- Components:
  - Op-Amp: two - LM741 (2 nos).
  - Diode: Two - IN4007 (2 nos).
  - Resistance: Ten -  $1\text{ k}\Omega$  (3 nos),  $10\text{ k}\Omega$  (3 nos),  $1\text{ M}\Omega$  (4 nos)
  - Capacitor:  $100\text{ }\mu\text{F}$  (3 nos)
  - Capacitor: Two -  $0.1\text{ }\mu\text{F}$ ,  $10\text{ HF}$ .

I => General Guidelines / Precautions:-

- 1) The op-amp generally works on split power supply (e.g.  $\pm 12\text{ V}$ ) both positive and negative power supplies must be present whenever op-amp is powered. The range of power supply is from  $\pm 5\text{ V}$  to  $\pm 15\text{ V}$ . Do not forget to connect the common terminal of the power supply to the ground on the breadboard.
- 2) Connecting only one side of power supply or interchanging positive and negative power supplies damages the op-amp.
- 3) For connecting power supply →
  - (a) Disconnect the power supply to op-amps.
  - (b) Switch on the power supply.
  - (c) Set the output voltage as required (e.g.  $+12\text{ V}$ ).
  - (d) Switch off the power supply.
  - (e) Connect to power supply to op-amps.
  - (f) Switch on the power supply.
- 4) For any IC, never exceed the input voltage beyond the power supply limits.
- 5) Key ground terminals of the oscilloscope probes and function generator output, and power supply common connected together throughout the experiment.
- 6) Make sure that the power lines in the breadboard given on the top and bottom for the power supply must be used and from their you connect to the other parts of the circuit.
- 7) Switch off the supply to all the equipments before you make any changes in the ckt.

II => Operation Amplifier Applications:-

High I/p impedance low o/p impedance, high open loop gain, high unity gain bandwidth.

## II. I → Voltage follower :- ( $B=1$ )

This connection forces the op-amp to adjust its o/p voltage simply equal to the i/p voltage ( $V_o$  follows  $V_i$ ) so the ckt is normal op-amp voltage follower.

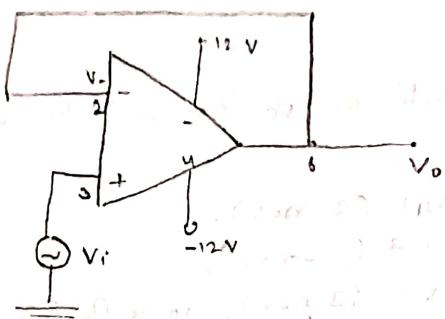


Fig :- Voltage follower Amplifier

### Voltage follower:-

It is used to transfer a voltage from a first ckt having a high o/p impedance level, to a second ckt with a low i/p impedance level.


### Current follower:-

It is used to transfer current from a first ckt, having a low o/p impedance level, to a second ckt with a high i/p impedance level. The voltage follower with a high prevents the second ckt from loading the first ckt unacceptably and interfering with its desired operation.

### Observation:-

1. measure the power supply  $\pm 12V$  from the bread board dines with respect to ground using multimeter.
2. Connect the ckt as shown in Fig.1. make sure the power supply ( $\pm 12V$ ) ground is connected to ckt to ckt ground.
3. Apply  $2V_{pp}, 1\text{kHz}$  sine wave at  $V_i$  from the function generator and see the o/p in the oscilloscope.
4. Before you connecting i/p voltage to the ckt measure the function generator o/p voltage using the oscilloscope.
5. Observe  $V_o$  and  $V_i$  and determine voltage gain  $A = \frac{V_o}{V_i}$ .

### Wave form:-

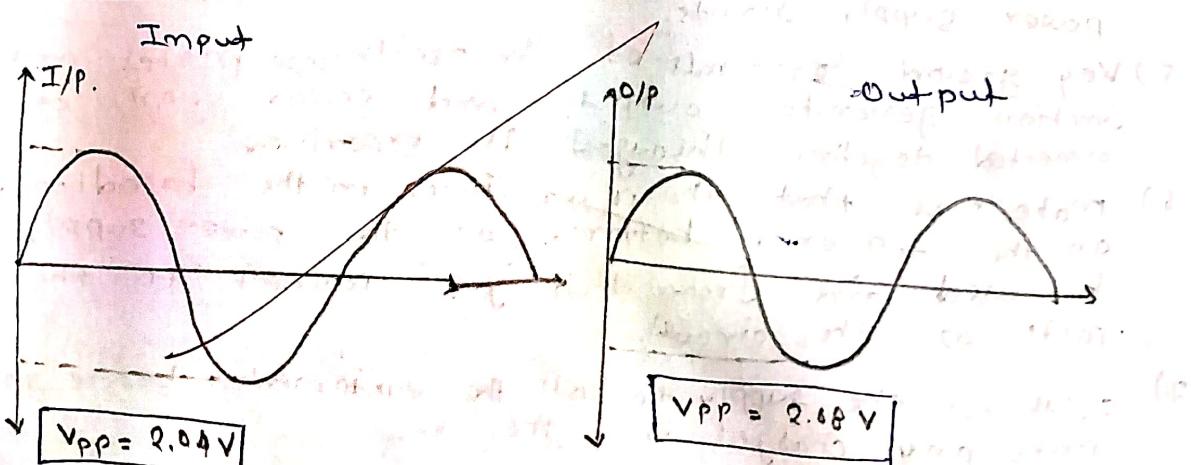

$$\therefore \max = 1V ; \min = 1.08V$$

$$\text{Gain} = A = \frac{V_o}{V_i} \Rightarrow V_o = 2.08, V_i = 2.04 \therefore A = \frac{2.08}{2.04} = 1.019 \approx 1$$

## II.II $\Rightarrow$ Integrator :-

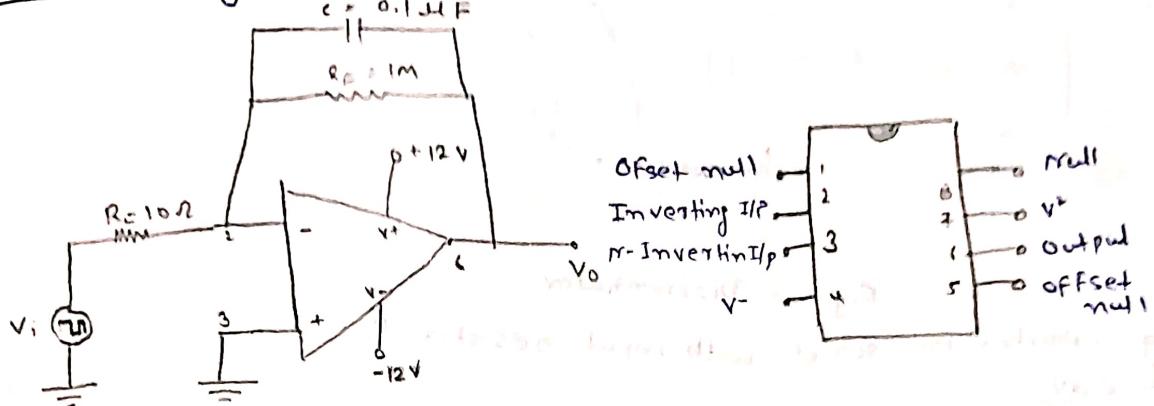


Fig. 2: Integrator

→ By adding capacitor in parallel with feed such Resistor  $R_f$  in a inverting amplifiers, the op-amp can be used as perform integration. An ideal or fault less integrator ( $R_f = \infty$ ) perform the computation.


$$V_o = -\frac{1}{R_f C} \int V_i dt. \text{ Thus a square } (R_f \ll \infty)$$

$$\tau = R_f C$$

=> Observation:-

- 1.) Assemble the ckt as shown in fig. 2 make sure that power supply ( $\pm 12V$ ), ground is connected to ckt + to ckt ground,
- 2.) Apply  $10 V_{pp}$  a square wave with period of  $2ms$  at  $V_i$  from the function generator and see the o/p in the oscilloscope.
- 3.) Before you connecting i/p voltage to the ckt measure the function generator o/p voltage using the oscilloscope (measure  $V_i$  and time period)
- 4.) Observe  $V_o$  and  $V_i$ , and determine voltage  $V_{ol}$  and connect on the o/p voltage (draw the i/p/o/p wave form together)

=> Wave form:-

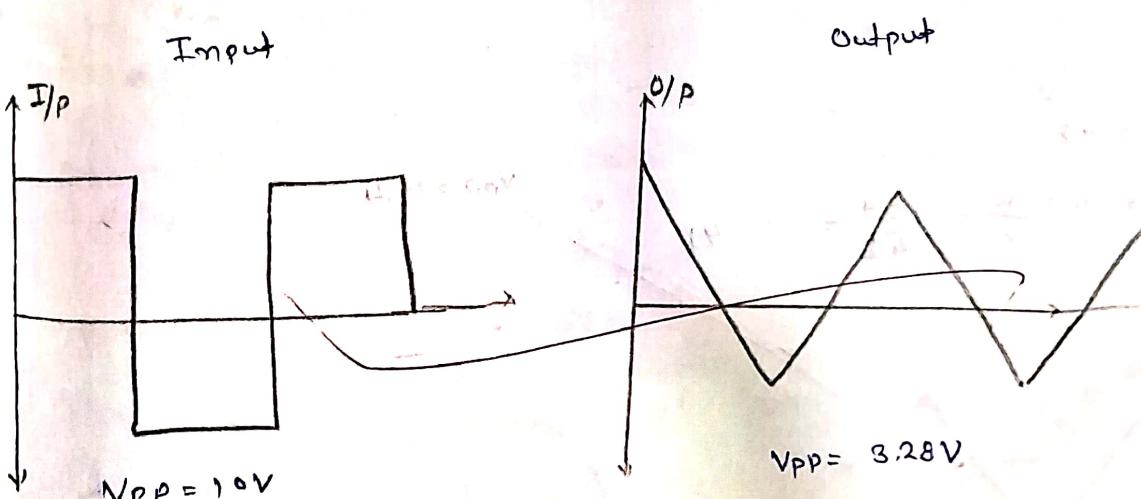

$$V_{pp} = 10V$$

$$\therefore \text{Max} = 4.24V \quad \& \text{min} = 920mV$$

$$\Rightarrow \text{Gain} \approx A = \frac{V_o}{V_i} \quad \text{So} \quad A = \frac{3.28}{10} = 0.328 \text{ A}$$

### II. III Differentiator

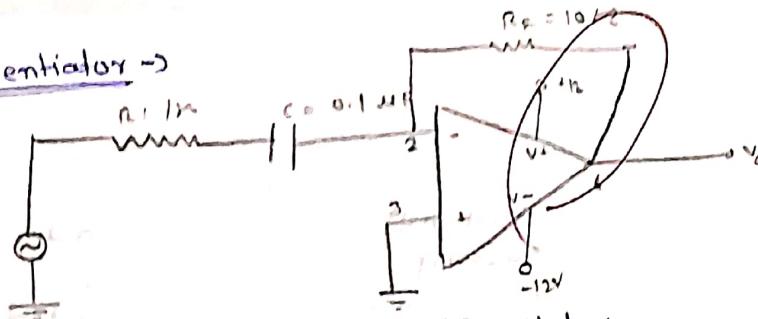


Fig. 3 → Differentiator

By adding capacitor in series with input resistor  $R_1$ .

$$\rightarrow V_o = -R_2 \frac{dV_i}{dt}$$


→ Triangular wave input would cause a square wave o/p.

→ However in a real ckt, will ( $R_1 > 0$ ) have some memory of the system state (like a lossy integrator) with exponential decay of time constant of  $\tau = R_1 C$ .




Observations →

- 1) Assemble the ckt as shown in Fig. 3 make sure the power supply ( $\pm 12V$ ) ground is connected to ckt float ground.
- 2) Apply  $5V_{pp}$ , triangular wave with period of 1ms or sine wave with  $1\text{ kHz}$  at  $V_i$  from the function generator and see the output in the oscilloscope.
- 3) Before you connecting input voltage to the ckt measure the function generator o/p voltage using the oscilloscope (measure  $V_i$  and time period)
- 4) Observe  $V_o$  and  $V_i$ , determine  $A$  and comment on the o/p voltage (draw the i/p/o/p wave form together)

→ **WAVE FORMS :-**

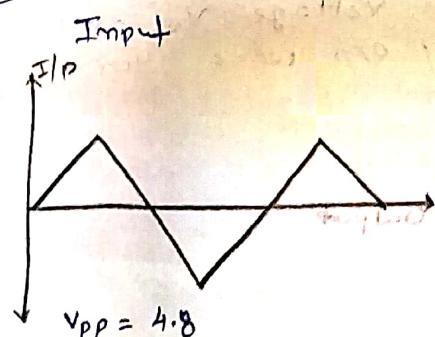

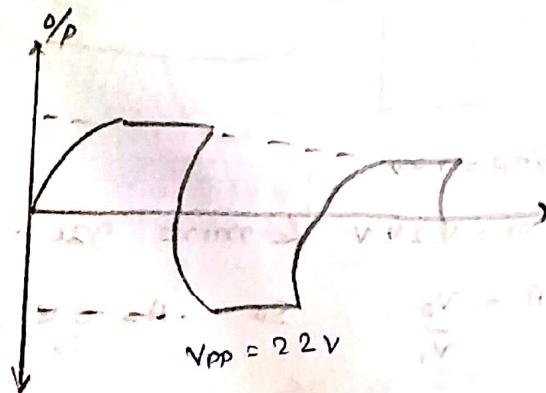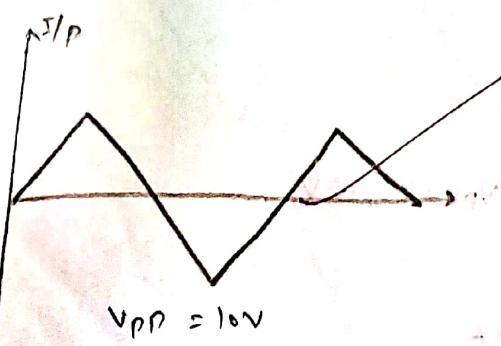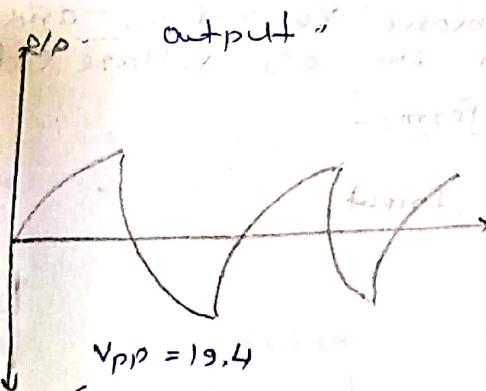
$$\text{Gain } A = \frac{V_o}{V_i} = \frac{19.4}{4.8} = 4.04$$




$$\text{Gain } A = \frac{V_o}{V_i} = \frac{22}{10} = 2.2$$
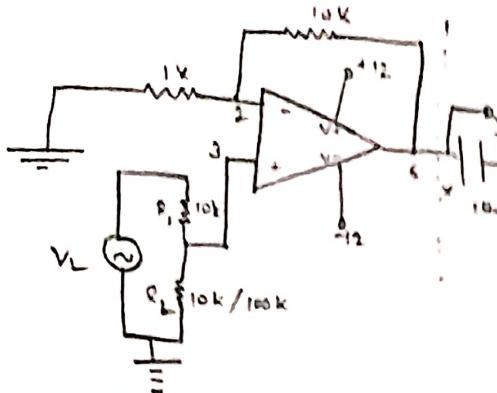
## II. IV Precision Rectifiers for a small AC signal



Non inverting Amplifier

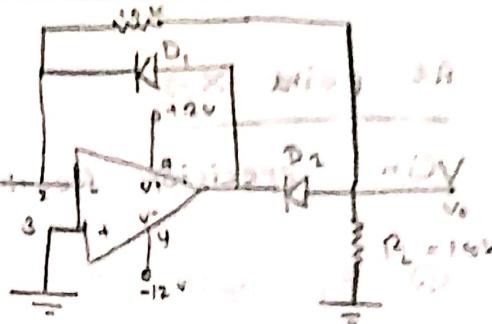

Half wave precision rectifier with gain

The circuit shown in fig 4 is of precision rectifier for a small AC signal as it consists of two stages.

• Stage -1: Non inverting Amplifier.

• Stage -2: Half wave precision rectifier with gate.

Pre experimental reading:-

Draw O/P waveforms and 'y' (stage 2 O/P) with magnitude at points 'x' (Stage 1 O/P) and 'y' (stage 2 O/P)

• with  $R_2 = 10\text{ k}\Omega$  and

• without  $R_2$  open (i.e., disconnected)

Observations:-

1) Assemble the ckt shown in Fig.4 with  $R_1=100\text{k}\Omega$  and  $R_2=1\text{k}\Omega$ . Make sure the power supply ground is connected to the circuit ground.

2) Apply  $100\text{mV}_{\text{pp}}$ ,  $1\text{kHz}$  sine wave at  $V_i$  from the function generator. and see the output in the oscilloscope.

3) Observe  $V_o$  at 'y' for:

- (a)  $R_2=1\text{k}\Omega$  (i) with capacitor 'c' and (ii) without capacitor 'c' (i.e. replace with a short circuit)
- b)  $R_2=10\text{k}\Omega$  (i) with capacitor 'c' and (ii) without capacitor 'c' (i.e. replace with a short circuit)
- c)  $R_2=100\text{k}\Omega$  (i) with capacitor 'c' and (ii) without capacitor 'c' (i.e. replace with a short circuit)
- d)  $R_2$  open [disconnected] (i) with capacitor 'c' and (ii) without capacitor 'c' (i.e. replace with a short circuit).

4) Draw the appropriate waveform for  $V_o$  at 'y' and define the values (Theoretical and practical).

At point X →

(In precision Rectifier)

①  $R_2 = \text{open}$


$$A = \frac{1.16}{0.106}$$

$$A = 11.32$$


②  $R_2 = 10\text{k}\Omega$

$$A = \frac{104}{106}$$


$$A = 0.98$$

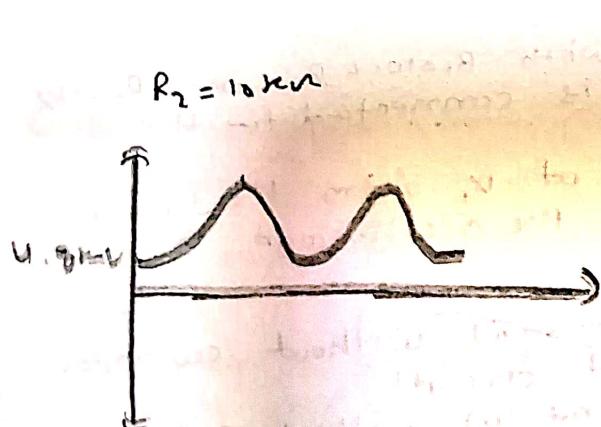

$R_2 = \text{open}$

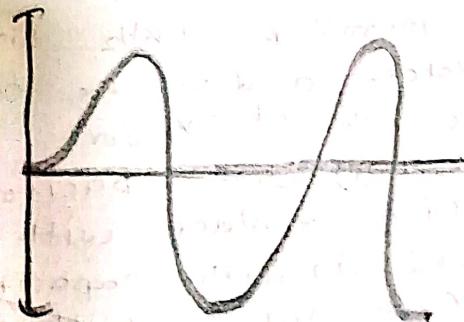

at point Y →

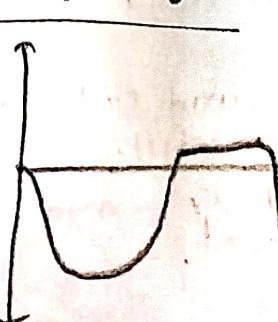

$R_1 = 10\text{k}\Omega$



$R_2 = \text{open}$

Precision Rectifier


with capacitors

$$\textcircled{1} \quad R_2 = 1\text{ k}\Omega$$

$$V_i = 106\text{ mV}$$

$$V_o = 63.2\text{ mV}$$

$$A_{CL} = \frac{63.2}{106} = 0.59$$

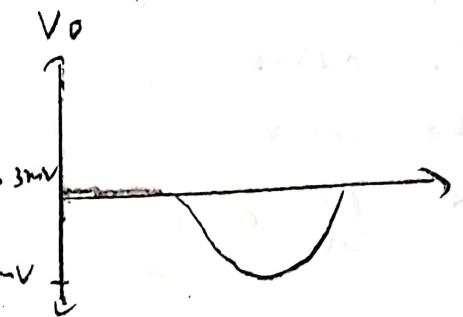


$$\textcircled{2} \quad R_2 = 10\text{ k}\Omega$$

$$V_i = 106\text{ mV}$$

$$V_o = 512\text{ mV}$$

$$A_{CL} = \frac{512}{106} = 4.830$$

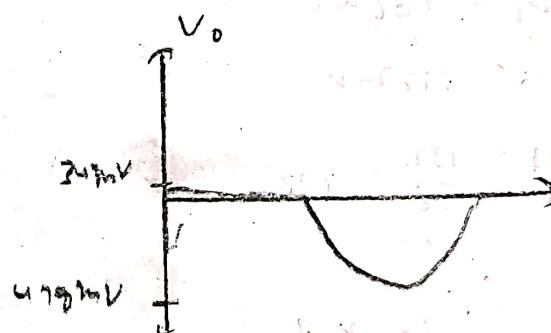


$$\textcircled{3} \quad R_2 = 100\text{ k}\Omega$$

$$V_i = 106\text{ mV}$$

$$V_o = 2.6\text{ V}$$

$$A_{CL} = \frac{2.6}{0.106} = 24.52$$

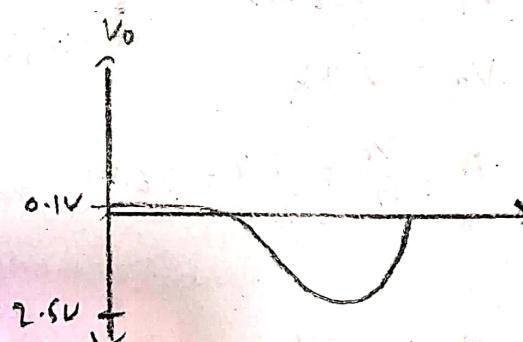


$$\textcircled{4} \quad R_2 = \text{open}$$

$$V_i = 106\text{ mV}$$

$$V_o = 5.6\text{ V}$$

$$A_{CL} = \frac{5.6}{0.106}$$

$$= 52.83$$

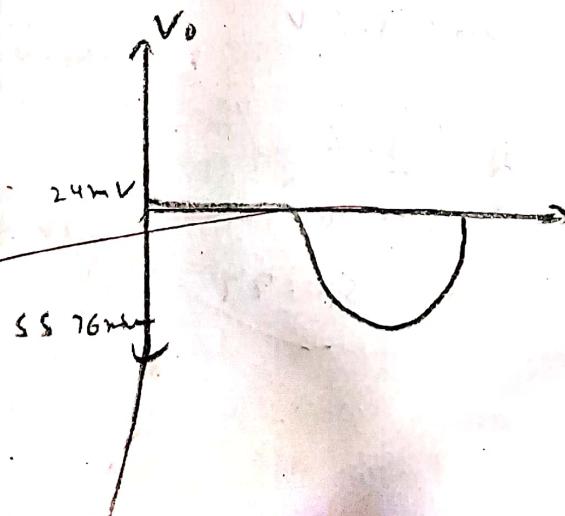


without capacitor

①  $R_2 = 1k\Omega$

$V_i = 106mV$

$V_o = 602mV$
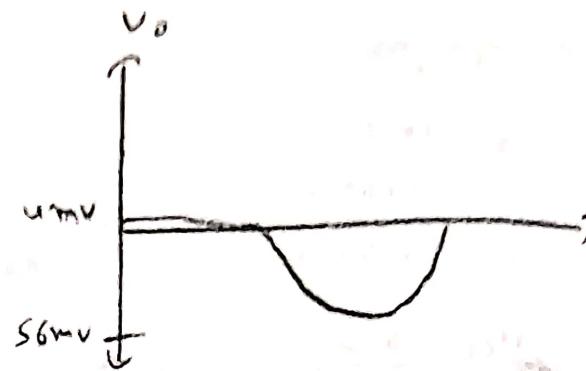
$$A = \frac{V_o}{V_i} = \frac{602}{106} = 5.69$$




②  $R_2 = 10k\Omega$

$V_i = 106mV$

$V_o = 332mV$
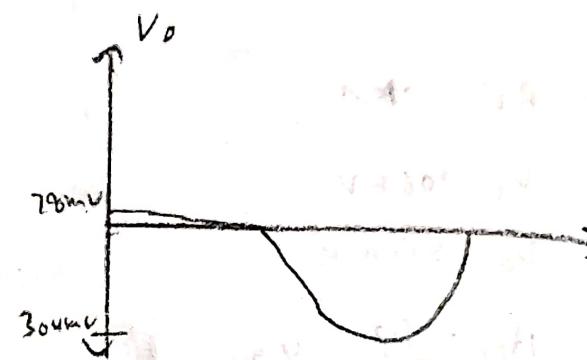
$$A = \frac{V_o}{V_i} = \frac{332}{106} = 3.13$$




③  $R_2 = 100k\Omega$

$V_i = 106mV$

$V_o = 2.8V$
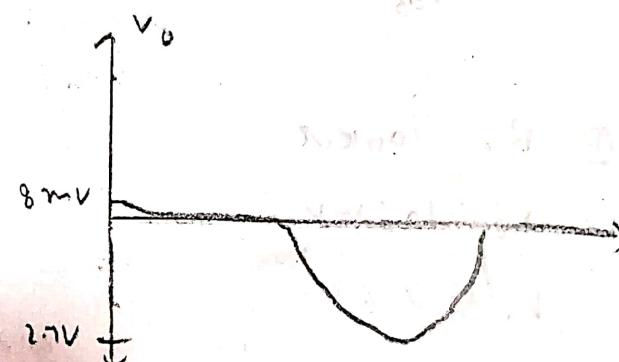
$$A = \frac{V_o}{V_i} = \frac{2.8}{0.106} = 26.41$$




④  $R_2 = \text{open}$

$V_i = 106mV$

$V_o = 5.6V$

$$A = \frac{5.6}{0.106} = 52.83$$

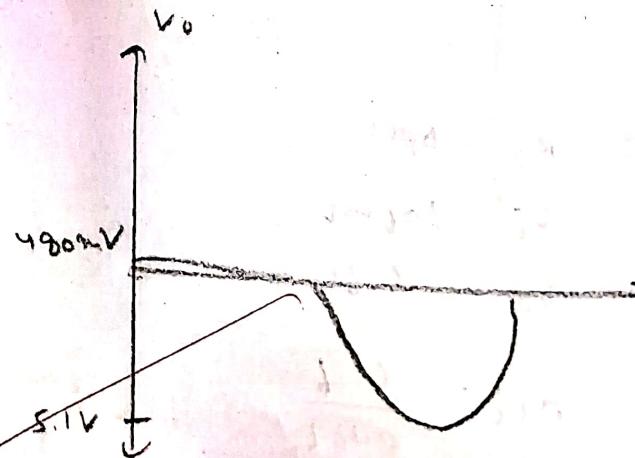

Questions:-

→ i) What is effect of  $B=1$  on op-amp characteristics?

Sol<sup>n</sup>: When  $B=1$  in an op-amp it means that the feedback n/w has unity gain, indicating that the o/p voltage is equal to the input voltage i.e. a voltage follower.

→ ii) How did you measure the internal input impedance of 741 op-amp justify?

Sol<sup>n</sup>: Impedance is represented by  $Z = \frac{\Delta V}{\Delta I}$ . The variation against the variation in the input common-mode voltage range.

→ iii) How did you measure the internal output impedance of 7410 op-amp justify?

Sol<sup>n</sup>: Impedance is represented by the ratio of the current variation  $\Delta I$  to the voltage variation  $\Delta V$ ,  $Z = \frac{\Delta V}{\Delta I}$ .

In a voltage follower configuration, the variation in the output voltage is measured by changing the o/p source and sink currents. In some o/p circuit configurations, the impedance may be different b/w the source and sink sides. Therefore, the variation in output voltage should be checked during both o/p current sourcing and sinking.

→ iv) What is the role of feedback resistor  $R_f$ ?

- Sol<sup>n</sup> (i) Gain control
- (ii) Stability
- iii) Input impedance
- iv) Output impedance.

→ v) If the polarities of all the diodes are changed, what will be the waveform at point X & Y.

Sol<sup>n</sup>: At point X the waveform will remain similar to the opposite waveform of a non-inverting amplifier but at point Y the o/p will be opposite i.e. in-ve half cycle there will be o/p and not in-ve half cycle.

## \* Conclusion:-

we learnt about working of voltage follower, integrator, differentiator & precision rectifier and also studied the output waveform with different values of resistance.

Harsh  
19/3pr

## Experiment 7: Find the Order Filters

### Objective :-

Designing a Active Low Pass Filter, Active High Pass Filter and Active Band Pass Filter.

### Materials Required

1. Breadboard

2. Equipment: Multi-Output DC power supply, Function Generators, Oscilloscope.

3. Components:

- Op-Amp: Two - LM741 (2 nos).

- Resistor: Four - 470Ω (1 no), 1kΩ (2 nos), 10kΩ (1 no).

- Capacitor: Two - 0.1μF, 10μF.

### I General Guidelines :-

1. The op-amp generally works on split power supply (e.g.  $\pm 12V$ ). Both positive and negative power supplies must be present whenever op-amp is powered. The range of power supply is from  $\pm 5V$  to  $\pm 15V$ . Do not forget to connect the common terminal of the power supply to the ground on the breadboard.

2. Connecting only one side of power supply or Interchanging positive and negative power supply damages the op-amp.

3. For connecting power supply, You have to follow the procedure as given below.

- a) Disconnect the power supply to op-amps.

- b) Switch on the power supply.

- c) Set the output voltage as required (e.g.  $\pm 12V$ ).

- d) Switch off the power supply.

- e) Connect the power supply to op-amps.

- f) Switch on the power supply.

4. For any IC, never exceed the input voltage beyond the power supply limits.

5. Keep ground terminals of the oscilloscope probes and function generator output, and power supply common connected together throughout the experiment.

6. Make sure that power lines in the breadboard goes on the top and bottom for the power supply must be used and from there you connect to the other parts of the circuit.

7. Switch off the supply to all the equipments before you make any changes in the circuit.

## II Active RC Filters

If a filter is a circuit that has designed to pass a specified band of frequencies while attenuating all signals outside the band.

Active filtering employ transistors or op-amps in addition to resistors, capacitors and inductors. Active filters offer several advantages over passive filters. The high input and low output resistance of the op-amp, the active filter does not cause loading of the source or load.

If low pass filter has a pass band from 0 Hz to a high cut off frequency of  $f_H$ . This cut off frequency is defined as the frequency where the voltage gain is reduced to 0.707, that is at  $f_H$  the gain is down by 3dB; after that ( $f > f_H$ ) it decreases as frequency increases. The frequencies between 0Hz and  $f_H$  are pass band frequencies whereas the frequencies beyond  $f_H$  are stop band frequencies. The stop band frequencies are the so-called stop band frequencies. A common use of a low pass filter is to remove noise or other unwanted high frequency components in a signal for which you are only interested in the DC or low frequency components.

Correspondingly, a high pass filter has a stop band for  $\omega < f_L$ , where  $f_L$  is the low cut off frequency. As common use for a high pass filter remove the ac component of a signal for work with dc.

If a band pass filter has a pass band between two cut off frequencies  $f_L$  and  $f_H$  ( $f_H > f_L$ ), and two stop bands at  $f < f_L$  and  $f > f_H$ . The bandwidth of a bandpass filter is equal to  $f_H - f_L$ .

## II. I Active low pass filter

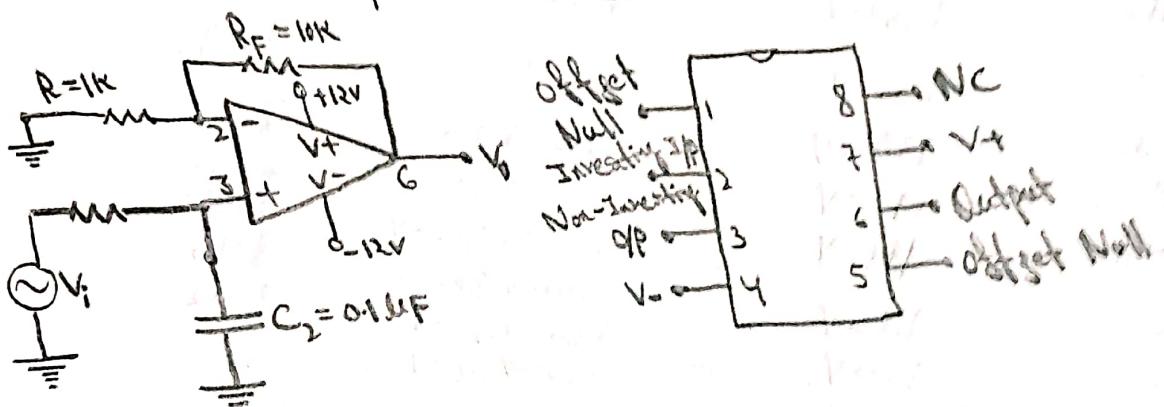


Fig. 1 Active low pass filter

### Observations:

- Measure the power supply  $\pm 12V$  from the breadboard power pins with respect to ground using multimeter.
- Fig. 1 shows a high pass filter. Connect the circuit and note the power supply ( $\pm 12V$ ) ground is connected to the circuit ground.
- Apply a sinusoidal signal of  $150mV$  as a input to the circuit from a function generator, and vary the input signal frequency ( $f$ ) from  $10Hz$  to  $30kHz$ . Observe the output voltage corresponding to the input voltage at different frequencies like  $10Hz, 100Hz, 1kHz, 5kHz, 10kHz, 15kHz, 17kHz, 18kHz, 19kHz, 20kHz, 21kHz, 22kHz, 23kHz, 25kHz, 30kHz$ .
- Observe the output voltage  $V_o$  and output voltage  $V_i$  together on the oscilloscope.

5. Draw the frequency response curve (Gain in dB vs f).  
 6. Calculate the corner cut off frequency  $f_H$  and compare with the theoretical value.

Note 8



- a) What is the output voltage for DC input voltage of 300mV.  
 b) Gain in dB  $A_v = 20 \log \frac{V_o}{V_i}$

Frequency	$V_i$	$V_o$	Gain = $\frac{V_o}{V_i}$
10 Hz	154 mV	1.74 V	11.29
100 Hz	156 mV	1.76 V	11.28
1000 Hz	150 mV	1.64 V	10.83
3.3 kHz	112 mV	<del>800mV</del> 1.02 V	8.64
3.5 kHz	148 mV	<del>500mV</del> 1 V	7.47
3.7 kHz	912 mV	<del>320mV</del> 960 mV	8.13
5 kHz	112 mV	<del>300mV</del> 820 mV	2.32
10 kHz	100 mV	<del>280mV</del> 500 mV	5
15 kHz	94 mV	300 mV	3.4
17 kHz	94 mV	280 mV	3.19
18 kHz	94 mV	280 mV	2.97
19 kHz	94 mV	260 mV	2.97
20 kHz	94 mV	240 mV	2.76
21 kHz	94 mV	240 mV	2.55
22 kHz	94 mV	220 mV	2.55
23 kHz	94 mV	200 mV	2.34
25 kHz	94 mV	1.32 mV	2.12
30 kHz	94 mV	1.08 V	9.85
2 kHz	134 mV	920 mV	8.85
3 kHz	122 mV		8.21
4 kHz	112 mV		

$$f = 100 \text{ Hz}$$

$$V_p = 154 \text{ mV}$$

$$V_o = 1.76 \text{ V}$$

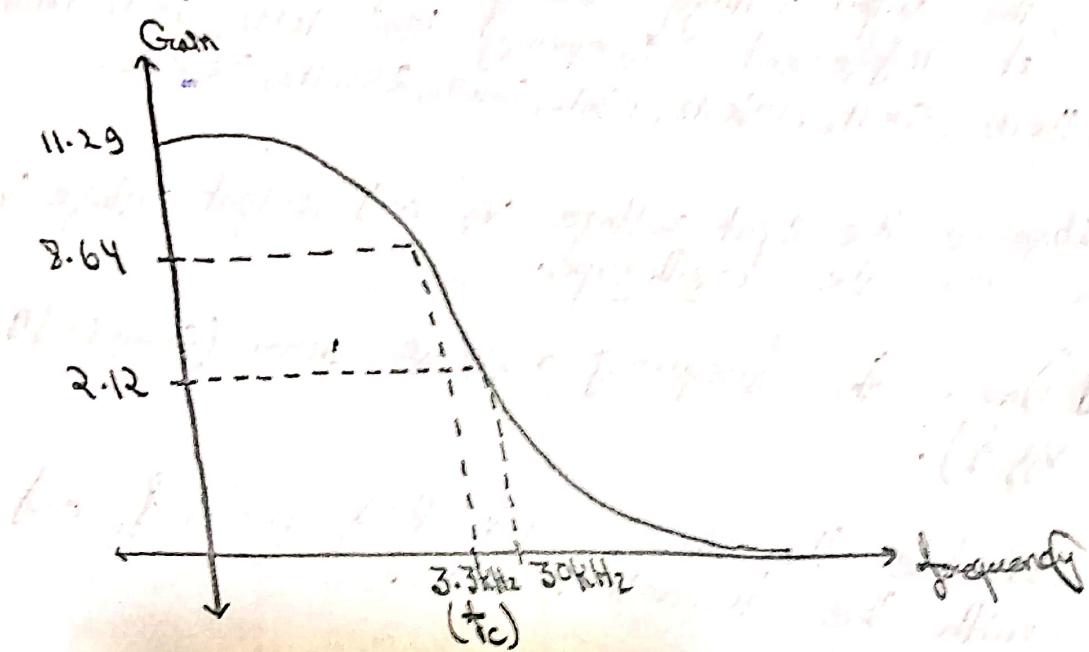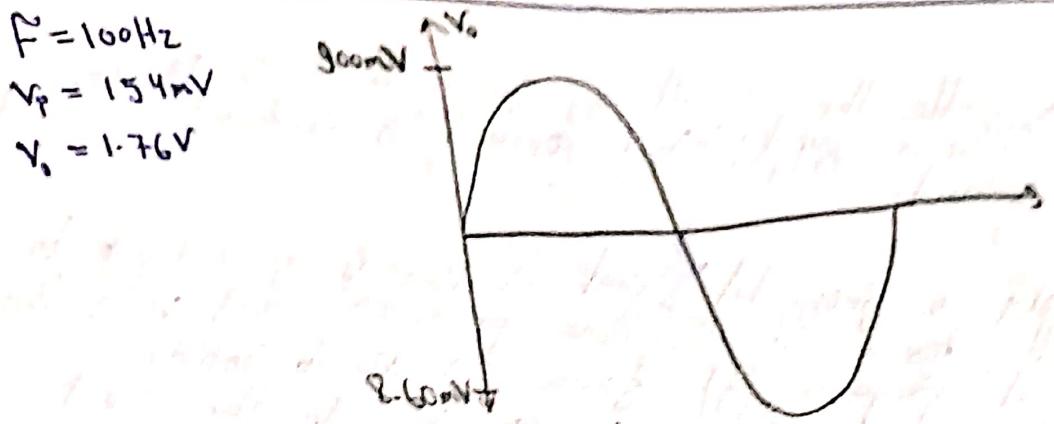

## II. II Active High Pass Filter

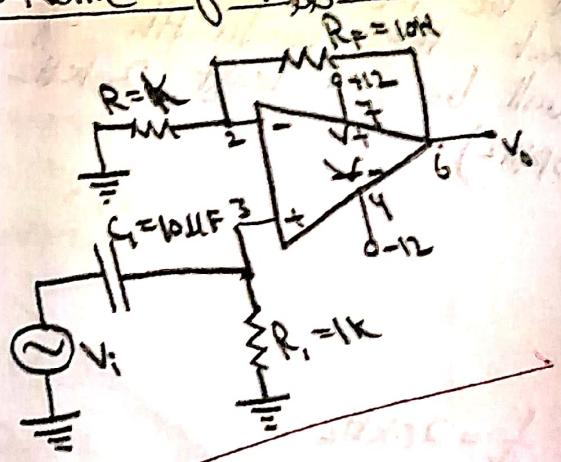


Fig. 2: Active High Pass Filter

## Observation :-

1. Assemble the circuit as shown in Fig.2. Make sure the power supply ( $\pm 12V$ ) ground is connected to circuit ground.

2. Apply a sinusoidal signal of  $150\text{mV}$  of a input to the circuit from a function generator, and vary the input signal frequency ( $f$ ) from  $10\text{Hz}$  to  $30\text{kHz}$ . Observe the output voltage corresponding to the input voltage at different frequency like  $10\text{Hz}$ ,  $50\text{Hz}$ ,  $100\text{Hz}$ ,  $500\text{Hz}$ ,  $1\text{kHz}$ ,  $5\text{kHz}$ ,  $10\text{kHz}$ ,  $15\text{kHz}$ ,  $20\text{kHz}$ ,  $25\text{kHz}$ ,  $30\text{kHz}$ .

3. Observe the input voltage  $V_i$  and output voltage  $V_o$  together on the Oscilloscope.

4. Draw the frequency response curve (Gain in dB vs f).

5. Calculate the lower cut off frequency  $f_L$  and compare with the theoretical value.

Note:-

a) What could be the maximum closed loop gain so that the bandwidth of the op-amp will be at least  $20\text{kHz}$  ( $G_B = 1.5\text{MHz}$ ).

$$\Omega_{CL} = \frac{f_{GB}}{f_C - f_{GB}}$$

Given,  $f_{GB} = 1.5\text{MHz}$  and  $f_C = 20\text{kHz}$

Let's plug the values into the formula:

$$\Omega_{CL} = \frac{1.5\text{MHz}}{20\text{kHz} - 1.5\text{MHz}} = \frac{1.5 \times 10^6}{-1.48 \times 10^6}$$



$$\Rightarrow \Omega_{CL} = -1.01$$

<u>Frequency</u>	<u><math>V_i</math></u>	<u><math>V_o</math></u>	$\text{Gain} = \frac{V_o}{V_i}$
10Hz	142mV	9.0mV	6.33
12Hz	142mV	1V	7.64
14Hz	142mV	1.08V	7.60
16Hz	138mV	1.14V	8.26
18Hz	138mV	1.18V	8.33
20Hz	138mV	1.20V	8.69
25Hz	130mV	1.26V	9.69
30Hz	130mV	1.32V	10.15
40Hz 30Hz	130 mV	1.34V	10.20
40Hz 35Hz	130 mV	1.36V	10.46
5kHz 40Hz	130 mV	1.39V	10.61
10kHz 45Hz	130 mV	1.40V	10.61
15kHz 50Hz	128mV	1.44V	10.43
20kHz 100Hz	128mV	1.46V	11.25
25kHz 1kHz	128mV	1.46V	11.40
30kHz 5kHz	128mV	1.48V	11.58
10kHz	126mV	1.4V	11.51
15kHz	126mV	1.38V	11.11
20kHz	126mV	1.38V	10.95
25kHz	126mV		
30kHz	126mV		

$$F = 10\text{Hz}$$

$$V_p = 142\text{mV}$$

$$V_o = 800\text{mV}$$

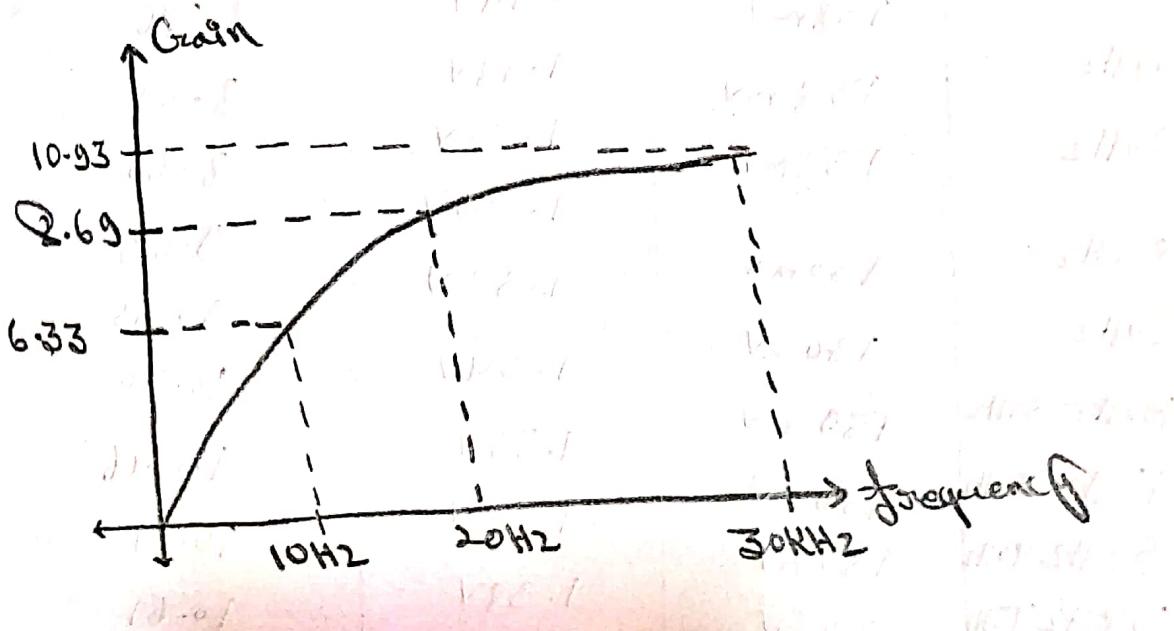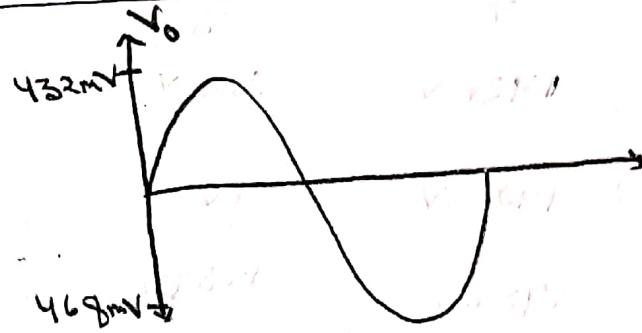

## II. III Active Band Pass Filter

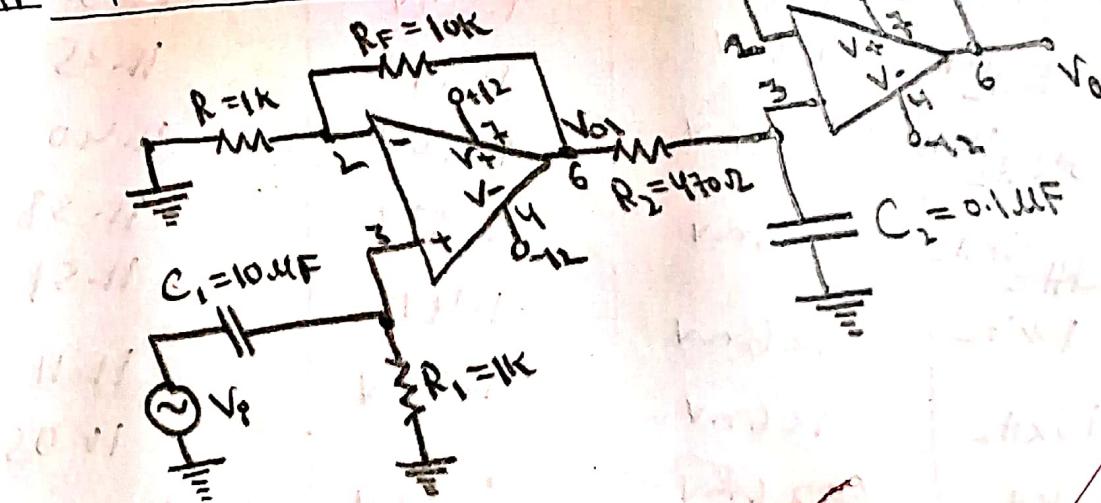


Fig. 3: Active Band Pass filter

### Observation :-

1. Assemble the circuit as shown in fig. 2. Make sure the power supply ( $\pm 12V$ ) ground is connected to circuit ground.
2. Apply a sinusoidal signal of  $150\text{mV}_p$  at a input to the circuit from a function generator, and vary the input signal frequency ( $f$ ) from  $10\text{Hz}$  to  $30\text{kHz}$ . Observe the output voltage corresponding to the input voltage at different frequencies like  $10\text{Hz}$ ,  $50\text{Hz}$ ,  $100\text{Hz}$ ,  $500\text{Hz}$ ,  $1\text{kHz}$ ,  $5\text{kHz}$ ,  $10\text{kHz}$ ,  $15\text{kHz}$ ,  $17\text{kHz}$ ,  $18\text{kHz}$ ,  $19\text{kHz}$ ,  $20\text{kHz}$ ,  $21\text{kHz}$ ,  $22\text{kHz}$ ,  $23\text{kHz}$ ,  $25\text{kHz}$ ,  $30\text{kHz}$ .
3. Observe the input voltage  $V_i$  and output voltage  $V_o$  together on the oscilloscope.
4. Draw the frequency response curve (Gain in dB vs f).
5. Calculate the pass band frequency range  $f_L \leq f \leq f_H$  and compare with the theoretical value.

### Important Note :-

For observation reading - Determine the appropriate theoretical values and draw the expected waveforms.

$$f_L = \frac{1}{2\pi \times 10^{-3}}$$

$$f_H = 3.388\text{kHz}$$

$$\Rightarrow f_L = 15.82\text{Hz}$$

~~for the~~ So the band frequency range,

$$15.82\text{Hz} \leq f \leq 3.388\text{kHz}$$

## Active low pass filter

a) What is the o/p voltage for DC i/p voltage of 300mV

Sol:  $f_c = \frac{1}{2\pi RC} = \frac{1}{6.28 \times 10^{-7} \times 470} = 3.388 \text{ kHz}$

$$V_o = \left(1 + \frac{10}{1}\right) \left( \frac{1}{\sqrt{1 + \frac{10-1}{3.388 \times 10^3}}} \right)$$

$$\Rightarrow V_o = 1.1V$$

b) Gain in dB.

Sol:  $A_v = 20 \log \frac{V_o}{V_i}$

$$\Rightarrow A_v = 20 \cdot 8.27$$

## Active High pass filter

a) What could be the maximum closed loop gain so that the bandwidth of the op-amp will be at least 20kHz ( $G_B = 1.5 \text{ MHz}$ ).

Sol:

$$f_c = \frac{1}{2\pi RC} = 15.92 \text{ Hz}$$

$$V_o = \frac{1}{\frac{f}{f_c}} \times 150 \times 10^{-3} \times 11 =$$

$$\frac{\frac{150}{15.92}}{\sqrt{1 + \left(\frac{150}{15.92}\right)^2}} \times 0.15 \times 11$$

$$\Rightarrow V_o = 1.57V > V_i$$

$$A_v = 20 \log \frac{V_o}{V_i}$$

$$= 20 \log \frac{1.57}{0.15}$$

$$\Rightarrow A_v = 20.40$$

## Conclusion :-

Active RC filters offer advantages such as adjustable gain, improved selectivity and reduced sensitivity to component variations. Active RC filters require additional power supplies and careful consideration of op-amp specifications. Despite these challenges, active RC filters are invaluable tools in modern electronic design, offering flexibility and precision in signal processing applications.

~~Took care  
26/27/2021~~

### Objective →

Designing of a phase shift oscillator, Wien bridge oscillator and Relaxation oscillator.

### Materials Required →

1. Breadboard

2. Equipment: Multi-Output DC power supply, Function generator, Oscilloscope.

3. Components:

- Op-Amp: One - LM741 (1 no).

- Resistors: Eleven -  $820\Omega$  (2 nos),  $1k\Omega$  (3 nos),  $2k\Omega$  (1 no),  $2.2k\Omega$  (1 no),  $3.3k\Omega$  (1 no),  $4.7k\Omega$  (1 no),  $5.6k\Omega$  (1 no),  $100k\Omega$  (1 no)

- Potentiometer: Two - 0 to  $10k\Omega$  (1 no), 0 to  $100k\Omega$  (1 no)

- Capacitor: Six -  $0.1\mu F$  (3 nos),  $0.002\mu F$  (2 nos),  $0.047\mu F$  (1 no)

### I General Guidelines / Precautions:

1. The Op-amp generally works on split power supply (e.g.  $\pm 12V$ ). Both positive and negative power supplies must be present. Whenever op-amp is powered, the range of power supply is from  $\pm 5V$  to  $\pm 15V$ . Do not forget to connect the common terminal of the power supply to the ground on the bread board.

2. Connecting only one side of power supply or interchanging positive and negative power supplies damages the Op-amp.

3- For connecting power supply, you have to follow the procedure as given below.

- Disconnect the power supply to op-amps.
- Switch on the power supply.
- Set the output voltage as required (e.g.  $\pm 12V$ ).
- Switch off the power supply.
- Connect the power supply to op-amps.
- Switch on the power supply.

4- For any IC, never exceed the input voltage beyond the power supply limits.

5- Keep ground terminals of the oscilloscope probes and function generator output, ground & power supply common connected together throughout the experiment.

6- Make sure that the power lines in the breadboard give them the top and bottom for the power supply must be used and from their you connect to the other parts of the circuit.

7- Switch off the supply to all the equipment before you make any changes in the circuit.

## I Oscillators

Oscillator is an electric circuit which converts dc signal into ac signal. Oscillator is basically a positive feedback amplifier with unity loop gain. If the feedback signal is not positive and gain is less than unity, oscillations dumped out. If the gain is higher than unity the oscillation saturates.

feedback through frequency-selective feedback network to ensure oscillation at  $\omega_0$ . Oscillators can be categorized according to the types of feedback networks used.

- RC oscillators: Phase-shift and Wien bridge oscillators.
- LC oscillators: Colpitt and Hartley oscillators.

## II. I Phase Shift Oscillator

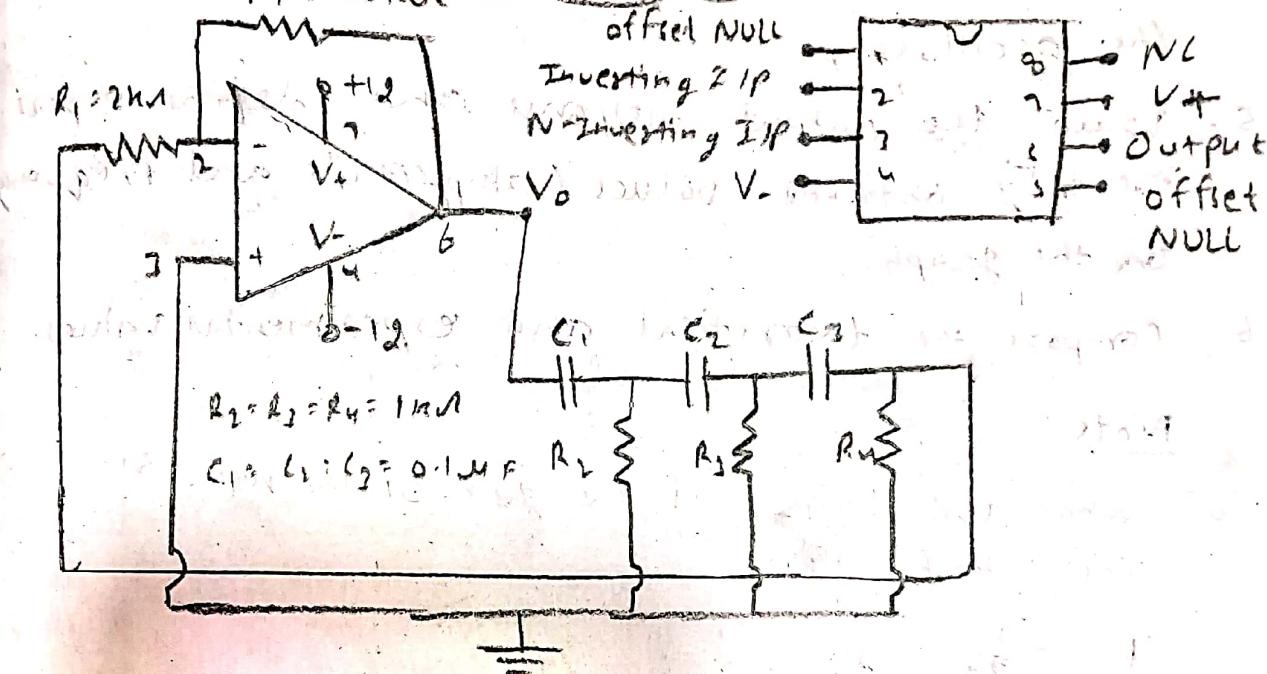


Fig. 1 : Phase Shift Oscillator

### Observations

- 1- Measure the power supply  $\pm 12\text{V}$  from the bread board power lines with respect to ground using multimeter.
- 2- Fig. 2 shows a phase shift oscillator. Connect the circuit and make sure the power supply ( $\pm 12\text{V}$ ) ground is connected to circuit ground and.

3. Initially, set the reference sinusoidal voltage from the function generator according to the theoretical calculations. The output voltage of the phase shift oscillator and the reference from the function generator need to be connected to the oscilloscope.
4. Observe the input voltage  $V_i$  (function generator output) and output voltage  $V_o$  together on the oscilloscope.
5. Draw the output response and define experimentally obtained values (amplitude and frequency) on the graph.
6. Compare the theoretical and experimental values.

Note:

(a) What will happen if the gain of the network is less than  $-1/2g$ .

$$\beta = -\frac{1}{2g}$$

$$\text{feedback gain } |1(\beta)| = \frac{1}{2g}$$

$$\text{for oscillator } |AB| \geq 1 \quad |A| \geq 2g$$

$$\frac{V_o}{V_{in}} = \frac{-R_c}{R_D} = A$$

$$A = \frac{1}{2\pi R C \beta} \times \omega = \frac{1}{R C \beta}$$

$$\frac{V_o}{V_{in}} = \beta \cdot \frac{1}{w^2 R^2 C^2}$$


$$f = \frac{1}{2 \times 3.14 \times 10^3 \times 0.1 \times 10^{-6} \sqrt{6}}$$

$$\beta = -\frac{5}{w^2 R^2 C^2}$$


$$f = 0.65 \text{ kHz}$$

Total phase shift =  $0^\circ$  or  $360^\circ$

Input

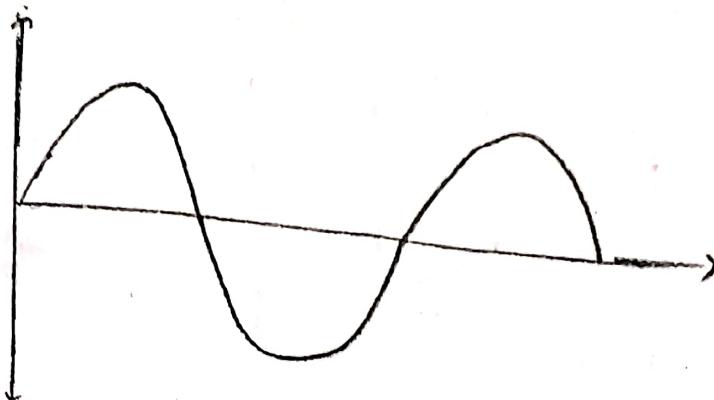

Output

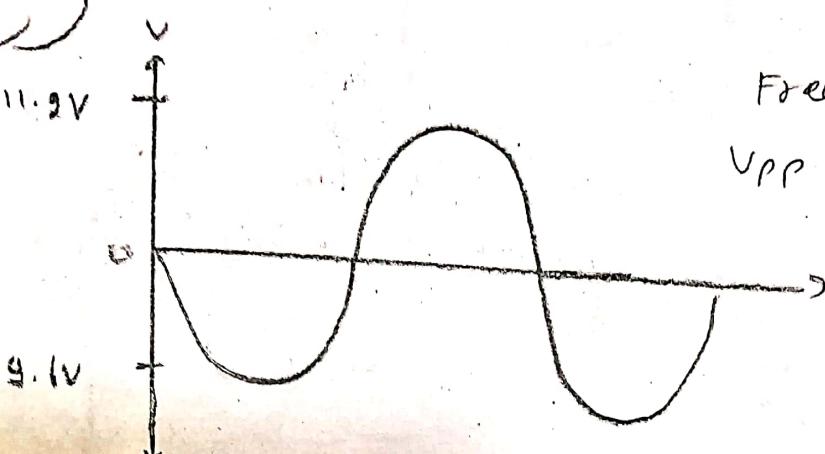

$$\text{Freq} = 1.02 \text{ kHz}$$

$$V_{PP} = 20.9 \text{ V}$$

### RC Phase & Angle

$$X_C = \frac{1}{2\pi f C}, \quad R = R,$$

$$Z = \sqrt{(R^2 + (X_C)^2)}$$

$$\phi = \tan^{-1} \frac{X_C}{R}$$

$$\text{freq} = \frac{1}{2\pi RC} \text{ J2N}$$

$$= \frac{1}{2\pi \times 2 \times 0.1 \times 10^{-6} \times 2 \times 3} \text{ J2N}$$

$$= \frac{10^6 \times 10^{-3}}{4\pi \times 0.1 \times 56}$$

$$= 324 \text{ Hz}$$

All the equations are solved for the output voltage.

## II. II Wien Bridge Oscillator →

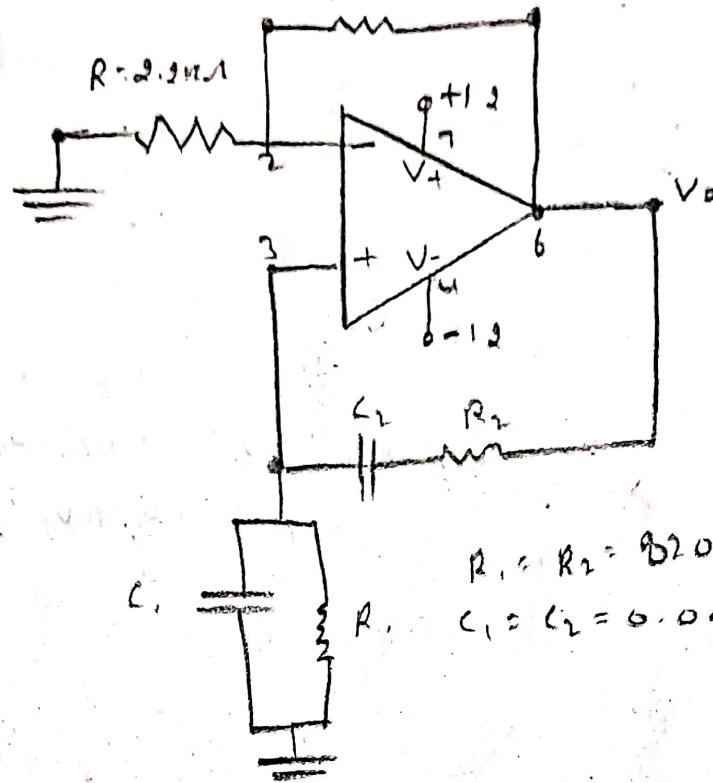


Fig. 2: Wien's Bridge Oscillator

### Observations:-

- 1- Assemble the circuit as shown in Fig. 2. Make sure the power supply ( $\pm 12V$ ) ground is connected to circuit - to - circuit ground.
- 2- Initially, set the reference sinusoidal voltage from the function generator according to the theoretical calculations. The output voltage of the phase shift oscillator and the reference from the function generator need to be connected to the oscilloscope.
- 3- Observe the input voltage  $V_i$  (function generator output) and output voltage  $V_o$  together on the oscilloscope.

Draw the output response obtained values (amplitude and frequency) on the graph.

5. compare the theoretical and experimental values.

Note:

Q. What is the advantage of Wien bridge oscillator compared to phase shift oscillator.

Answer: However, they differ in their circuit topology, operating principle, and frequency stability. In phase shift oscillators, we use 3 capacitors to ensure oscillation. However, we only use 2 capacitors for Wien-bridge and the circuit oscillates fine.

Wien's bridge Oscillator

feedback gain  $|A_f| = \frac{1}{3}$  for oscillator  $\Rightarrow |A_f| \geq 1 \Rightarrow A \geq 3$


$$w = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, f_r = \frac{1}{2\pi \sqrt{R_1 C_1 R_2 C_2}} \quad R_1 = R_2, f_r = \frac{1}{2\pi \sqrt{C_1 C_2}}$$

$$f_r = \frac{1}{2 \times 3.14 \times 810 \times 820 \times 0.002 \times 10^{-6}} = 97.09 \text{ kHz}$$


$$\text{at resonate} \Rightarrow \frac{R_F}{R_i} = \frac{R_2}{R_1} + \frac{C_2}{C_1} = 2$$

$$\frac{V_o}{V_{in}} = 1 + \frac{R_F}{R_i} = A \quad \text{Total Phase shift} = 0^\circ$$
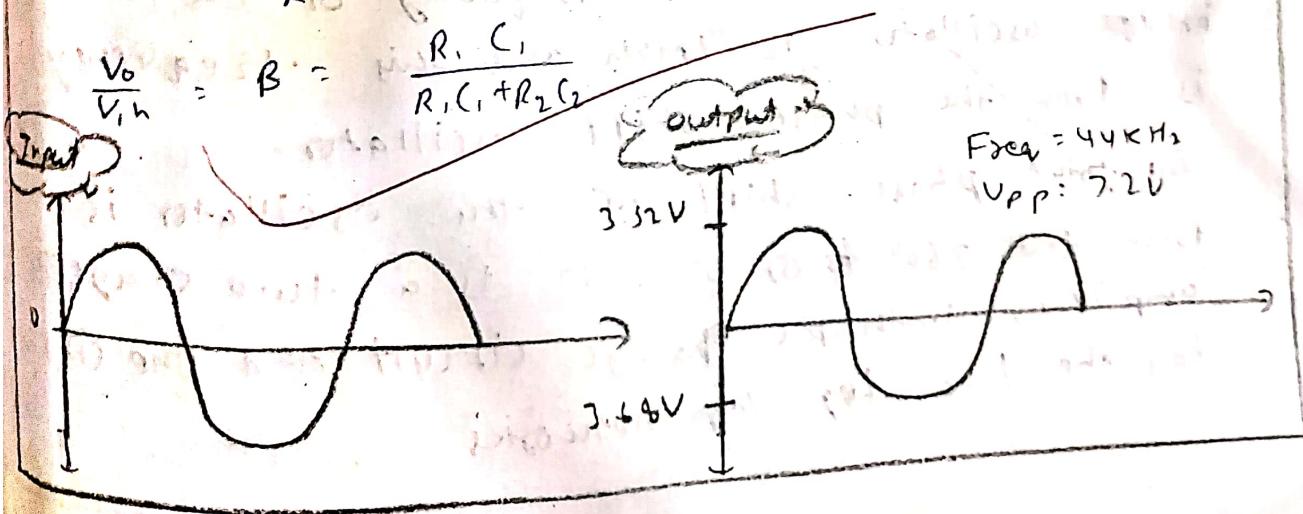
$$\frac{V_o}{V_{in}} = B = \frac{R_1 C_1}{R_1 C_1 + R_2 C_2}$$



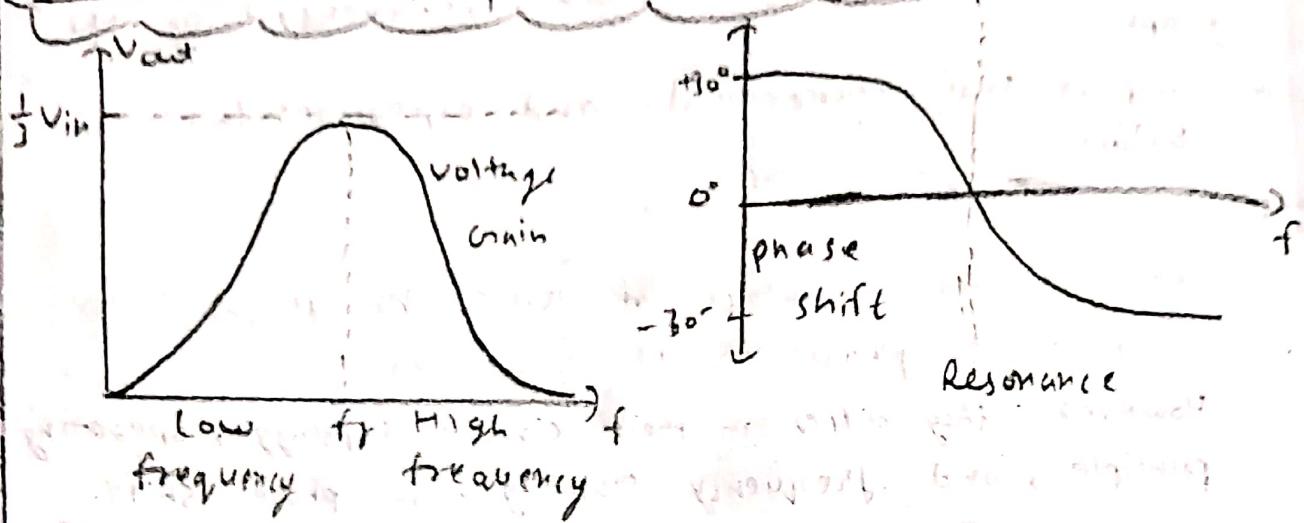Oscillator Output (main and phasor shift)



Wien bridge Oscillator (Frequency:  $\rightarrow$ )

$$f_r = \frac{1}{2\pi R C}$$

$f_r$  = Resonant freq. in Hz

$R$  = Resistance in  $\Omega$

$C$  = Capacitance in  $F$

Series circuit

$$X_C = \frac{1}{2\pi f C}$$

$$Z_s = \sqrt{R^2 + X_C^2}$$

~~Karbach  
 $2\pi f / \text{reson}$~~

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{X_C}$$

$$Z_{out} = \frac{Z_p}{Z_p + Z_s}$$

~~Parallel circuit~~

CONCLUSION

Hence the maximum OIP frequency of the Wien bridge oscillator is  $1 \text{ MHz}$  and this frequency is from the phase shift oscillator.

The total phase shift of the oscillator is from the  $360^\circ$  to  $0^\circ$ : It is a two stage amplifier with RC bridge circuit and the circuit has the lead lag networks.

# Post Lab Experiment 9 (23/01/2011)

Mayank

## Objective :-

Designing of a Astable multivibrator.

## Materials required:-

1. Breadboard

2. Equipment : Multi-output DC power supply, oscilloscope.

3. Components :-

• 555 timer : LM555 (1 no)

• Capacitor : 0.1  $\mu$ F (1 no)

• Resistor : 18 k $\Omega$  (1 no) & 0.001  $\mu$ F (1 no.)

18 k $\Omega$  (1 no.) & 33 k $\Omega$  (1 no.)

## I. General Guidelines / Precautions :-

### i) The op-amp generally works on split power supply (e.g. $\pm 12V$ )

Both positive and negative power supplies must be present whenever op-amp is powered. The range of power supply is from  $\pm 5V$  to  $\pm 15V$ . Don't forget to connect the common terminal of the power supply to the ground on the breadboard.

ii) Connecting only one side of power supply or interchanging positive and negative power supplies damages the op-amps.

iii) For connecting power supply, you have to follow the procedure as given below.

a) Disconnect the power supply to op-amps.

b) Switch on the power supply.

c) Set the output voltage as required (e.g.  $\pm 12V$ ).

d) Switch off the power supply.

e) Connect the power supply to op-amps.

f) Switch on the power supply.

v) For any IC, never exceed the input voltage beyond the limits.

vi) For only IC, never exceed the input voltage beyond keep ground terminals of the oscilloscope probes and function generator output throughout the experiment.

vii) Make sure that the power lies in the breadboard given on the top and bottom for the power supply must be used and from their you connect to other parts of ckt.


viii) Switch off the supply to all the equipments before you make any changes in the ckt.

## II. Astable Multi Vibrator:-

The 555 timer is a highly stable device for generating accurate time delay ranging from micro seconds to hours whereas counter timer can have a maximum timing range of days. These functions are needed in many analog digital or mixed-signal applications.

With the addition of an external capacitor and two external resistors, the 555 timer can be configured to produce a periodic pulsating wave form at the output, without any external trigger pulses. The key difference between the monostable and the astable operation is that the trigger input is connected together with the threshold input so that the timer triggers itself during operation.


Circuit:-

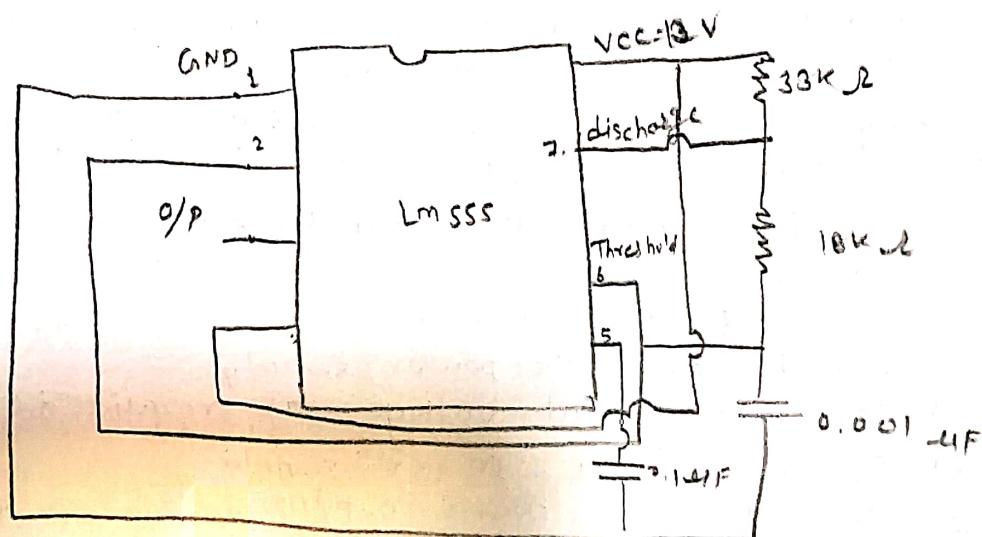

Observations:-

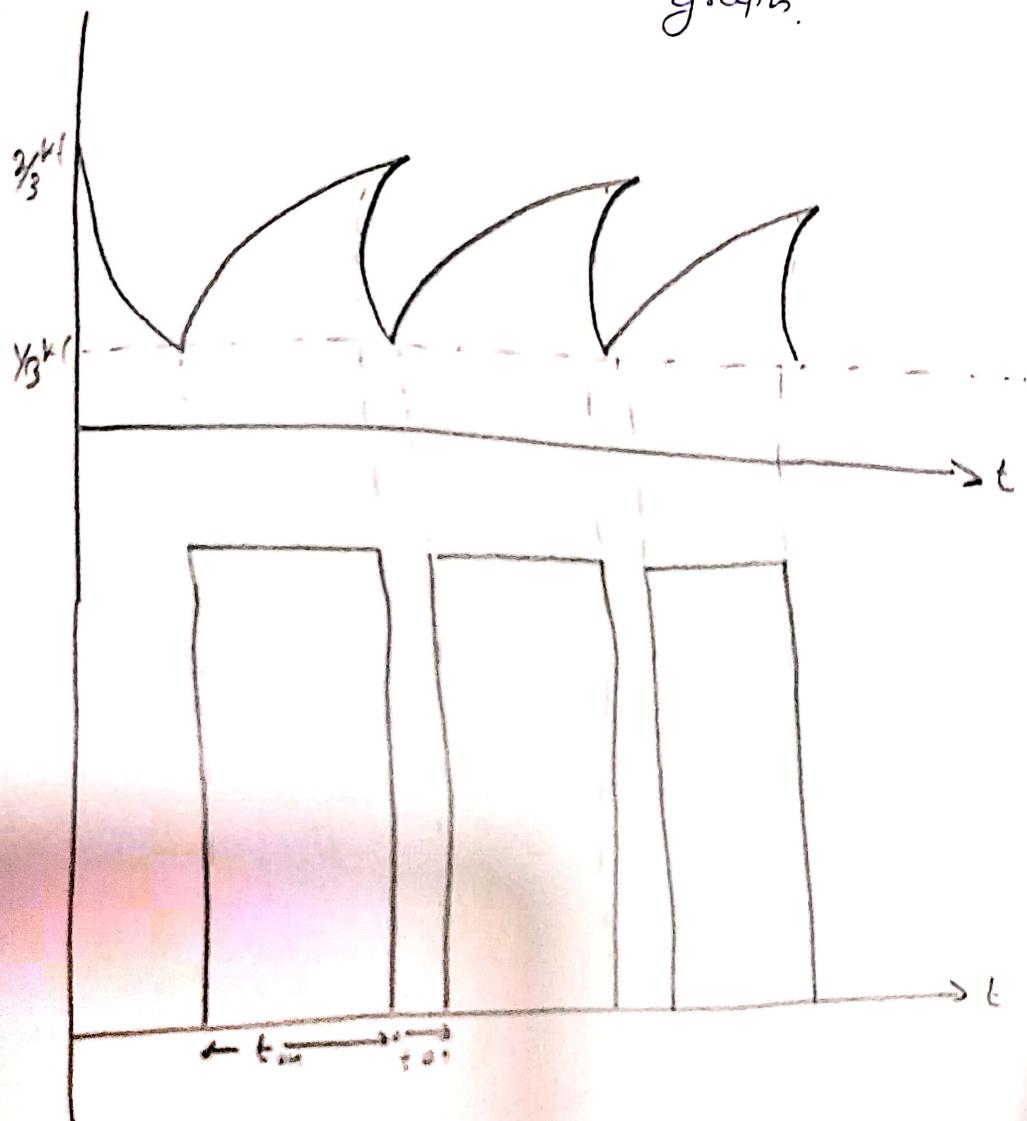1. Assemble the circuit and it is a basic configuration for astable operation.
2. The capacitor 'c' is periodically charged and discharged between the trigger level  $V_L = V_{CC}/3$  and threshold level  $V_H = 2V_{CC}/3$ .
3. Astable circuit produce periodic output pulses with frequency  $f_p = 20kHz (\pm 2)$ .
4. Observe the O/P waveform and define the total time period ( $T_p$ ), on time ( $T_H$ ) or charging time, off time ( $T_L$ ) or discharging time, off time ( $T_L$ ) and duty cycle ( $D$ ).

Draw the capacitor response voltage value on the graph.



Readings :-

$$\text{Duty Cycle} = 99.1\%$$

$$\text{Time period} = 41.8 \mu\text{s}$$

$$f = 23.9 \text{ kHz}$$

$$V_{pp} = 10 \text{ V}$$



Compose the theoretical and experimental values.

Note:-

(a) What will be value  $R_A$  to get 75% duty cycle

$$\Rightarrow \frac{3}{4} = \frac{0.693(R_1 + R_2)C}{0.693(R_1 + 2R_2)C}$$
$$\frac{3}{4} = \frac{R_1 + R_2}{R_1 + 2R_2}$$

$$3R_1 + 6R_2 = 4R_1 + 4R_2$$

$$2R_2 = R_1$$

$$\therefore R_A = 2R_B$$

$$T_{ON} = 0.693(R_1 + R_2)C$$

$$T_{off} = \frac{0.693 \times R_2 \times C}{0.693 \times R_2 \times C} = 1.247 \times 10^{-5} \text{ sec}$$

$$T_{total} = 0.693(R_1 + 2R_2)C$$
$$= 4.781 \times 10^{-5} \text{ sec}$$

$$f = \frac{1}{T} = 20.913 \text{ Hz}$$
$$= 20.913 \text{ kHz}$$

Conclusion:-

In this experiment we designed and implemented the Astable multi window vibrator and checked it V<sub>PP</sub>, V<sub>max</sub>, frequency and reading to satisfy everything.