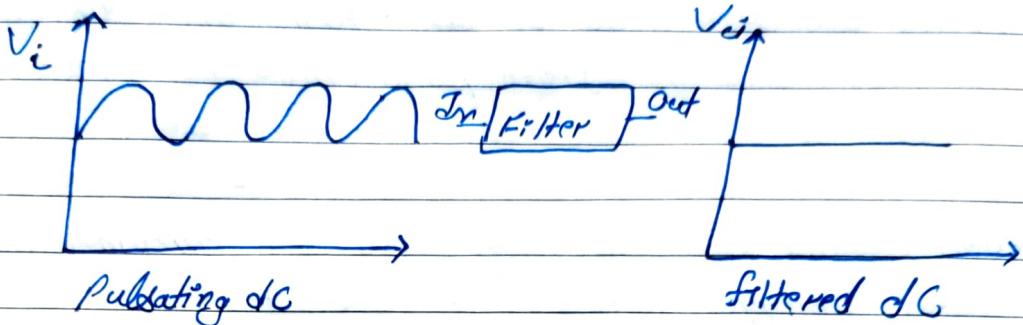




- # Transformer may be used for isolation even if not required for stepping up or down the input ac.

- Filters:**

To minimise the ripple content.





- Shunt Capacitor filter \rightarrow

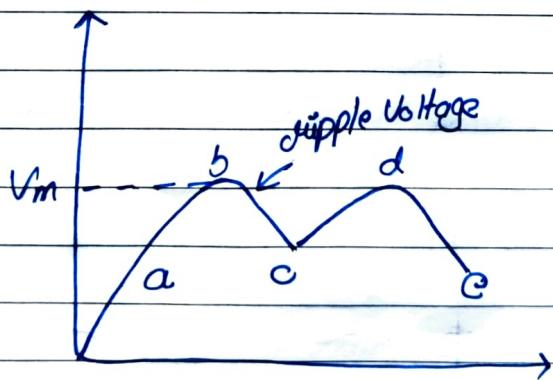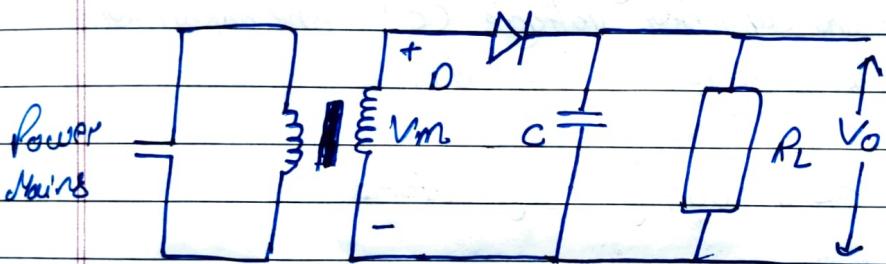

- When the true half cycle of the AC input is applied the diode is in forward bias and hence it'll conduct. So this allows the capacitor to quickly charge upto V_m , i.e., upto (b).

- cii After we fully charge, the capacitor holds the charge till the input ac supply to the rectifier goes negative.
 - iii During the -ve half cycle the capacitor attempts to discharge. However, it can't discharge through diode being reverse bias as off. Hence still gets discharge from load resistor from point (b) to (c) and its voltage decreases somewhat.
 - iv Even during the -ve half cycle the capacitor maintains large voltage across load resistor.
- 5 During the next +ve half cycle when the rectifier voltage exceeds the capacitor voltage (c), the capacitor is again quickly charged to V_m (d).
- Zener diode as a voltage regulator:

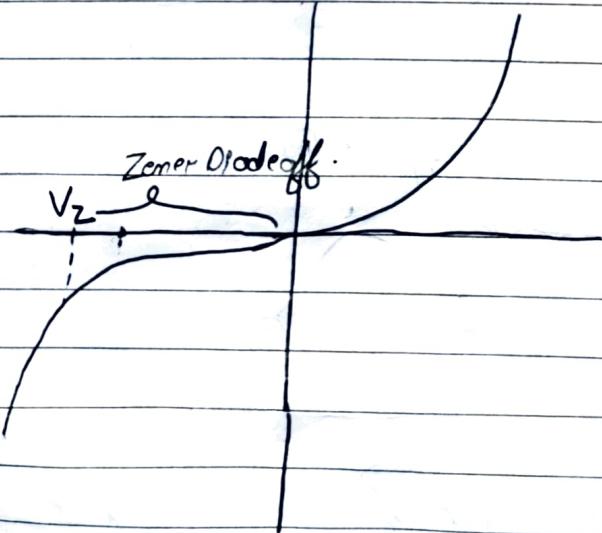

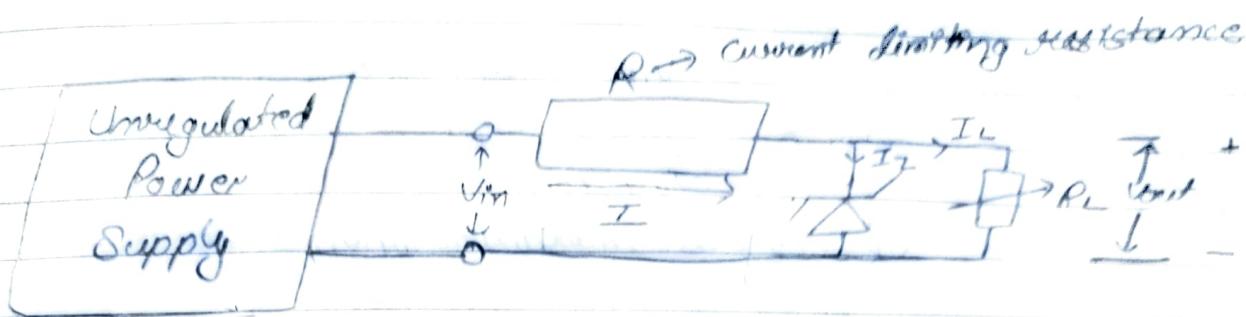

$$I = I_Z + I_L$$

Voltage Regulator is used to keep constancy in the dc voltage

Case I: Suppose R_s is kept fixed but supply voltage V_{in} is slightly increased.

- i The increase in current I will be absorbed by zener diode without affecting I_L .
- ii The increase in V_{in} will be dropped across R thereby keeping V_{out} constant.
- iii On the other hand, if the supply voltage decrease the diode takes a smaller current and voltage drop across R is reduced, thus again keeping V_{out} constant.
- iv When V_{in} changes I and IR drop changes in such a way as to keep $V_{out} = V_Z$ constant.

Case II: V_{in} is fixed but I_L is changed.

- i When I_L increases, diode current I_Z decreases thereby keeping I and IR drop constant. In this way V_{out} remains unaffected.
- ii When I_L decreases, diode current I_Z increases thereby keeping I and IR drop constant. In this way V_{out} remains unaffected.

$$V_{out} = V_{in} - IR$$

$$= V_{in} - (I_L + I_Z)R$$

$$R = \frac{V_{in} - V_{out}}{I_L + I_Z}$$

If I_Z is maximum then $I_L = 0$

$$\text{So } R = \frac{V_{in} - V_{out}}{I_Z(\text{max})}$$

Half Wave Rectifier:

$$\text{Ripple factor} = 1$$

$$2\sqrt{3}fRC$$

Full wave Rectifier:

$$\text{Ripple factor} = \frac{1}{4\sqrt{3}fR_L C}$$

In a centre tap full wave rectifier the load resistance $R_L = 1k\Omega$. Each diode has forward bias resistance of 10^{-2} . The voltage across half the secondary winding is $220 \text{ & } 314 \text{ volt}$. Find

- i Peak value of current

- ii DC average value of current

- iii RMS value of current.

- iv Ripple factor

- v Rectification efficiency.

$$\text{iii} \quad V = 220 \text{ Volts} / 100\pi f$$

$$2\pi f = 100\pi$$

$$f = 50 \text{ Hz}$$

$$R_L = 1000 \Omega$$


$$\text{Im} = \frac{220}{1016} = 0.217 \text{ A}$$

$$\text{iii} \quad \frac{2\text{Im}}{\pi} = \frac{2 \times 0.217}{3.14} \approx 0.138 \text{ A}$$

$$\text{iii} \quad \frac{0.217}{\sqrt{2}} = 0.158$$

$$\text{iv} \quad \underline{0.482} \quad R = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{dc}}}\right)^2 - 1} \\ = 0.478$$
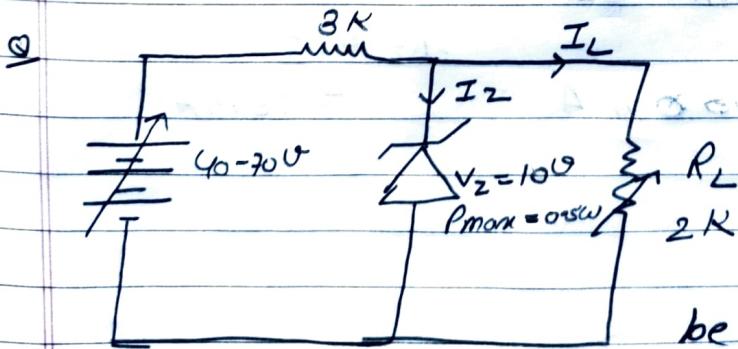
$$\text{v} \quad \eta = \frac{P_{\text{dc}}}{P_{\text{ac}}} = \frac{(I_{\text{dc}})^2 R_L}{I_{\text{rms}} \times (R_L + R_d)} \\ \approx 81.2 \%$$



Calculate the battery current I , I_2 and I_L in the circuit.
How will these values be affected if source voltage increases to 70V.

Neglect zener resistance.

$$P_{max} = I_2 \cdot V_2$$

tp

~~$$20V = I_2 \times 10$$~~

$$IR = 30V$$

~~$$0.05A = I_2$$~~

$$\frac{80 \times 10^{-3}}{3} = I$$

~~$$5 \times 10^{-2} A = I_2$$~~

~~$$\text{so } I = 408$$~~

$$10mA = I$$

~~$$8 \times 10^{-3}$$~~

~~$$I = 8 \times 10^{-3} A$$~~

$$i_L = \frac{10}{2000}$$

$$= 5mA$$

~~$$V_{RL} = 30V$$~~

~~$$\text{so } V = IR$$~~

~~$$\frac{30V}{2 \times 10^3} = I_L$$~~

$$i_2 = I - i_L$$

$$= 5mA$$

~~$$10 \times 10^{-3} = I_2$$~~

~~$$I_2 + i_L = I \text{ so } V_{in} = 30V$$~~

$$IR = 60$$

$$= \frac{60 \times 10^{-3}}{3}$$

~~$$\text{When } V_{in} = 40V$$~~

~~$$V_2 = 10V$$~~

~~$$30V = IR$$~~

$$= 20mA$$

~~$$30 = I \times 3 \times 10^{-3}$$~~

~~$$10 \times 10^{-3} = I$$~~

~~$$10mA = I$$~~

~~$$9.5mA = I_L$$~~

$$i_L = \frac{10}{2000} = 5mA$$

$$i_2 = I - i_L$$

$$= 15mA$$



~~$$I_2 = 5mA$$~~

• Clippers and Clampers:


portion of input signal is clipped off

lift up or lift down the input signal to a different DC circuit level.

Clipper circuit:

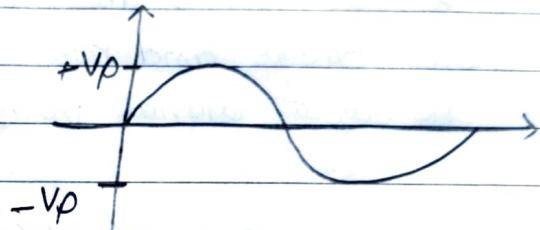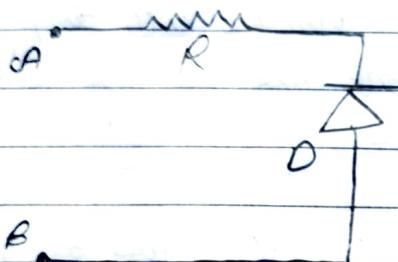


Input Sine Wave Signal

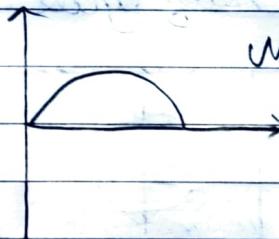

Negative Clipper

When the +ve half cycle of the signal is applied on the clipper A is ~~the~~ cut B the diode ~~is~~ D is reverse biased. Hence it acts as an open circuit.

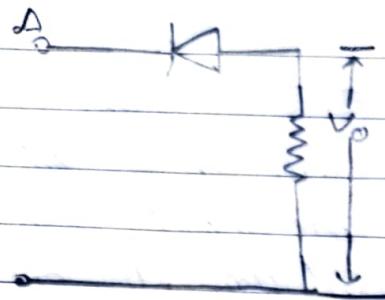During the -ve half cycle D is forward biased, hence it acts a closed ~~switch~~ switch.





Positive Clipping






During the +ve half cycle of signal D acts as an open switch, hence, all the applied voltage will drop across the diode and none across the resistor. So there's no output signal voltage.

During the -ve half cycle D is in f.B. so all the voltage is across R.

Clipping of both half cycles:

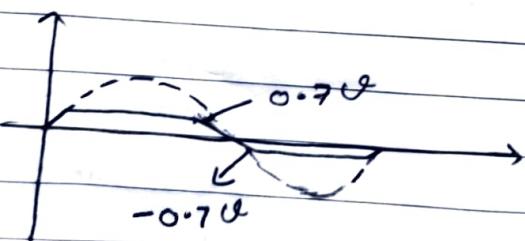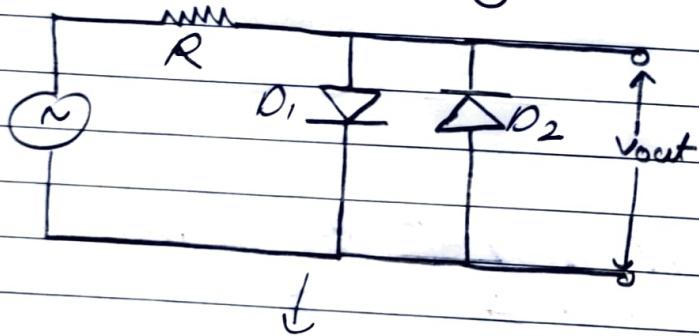


Bias diode Clipping Circuits:

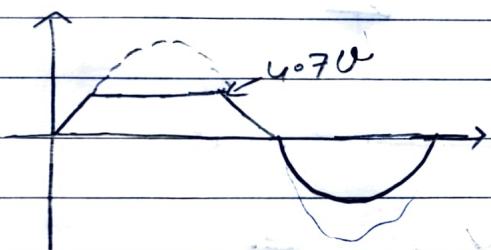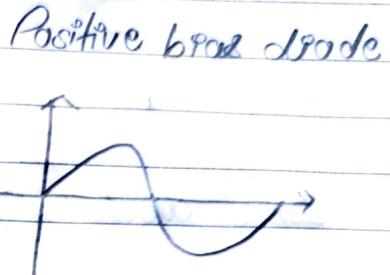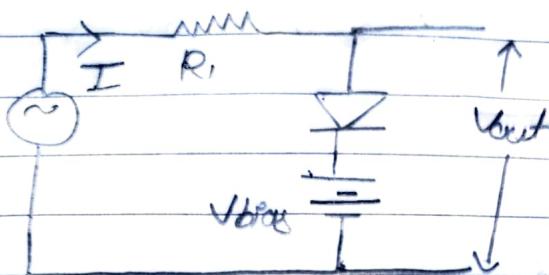



$$V_{bias} + V_{diode} \approx V_{AC}$$

Negative bias diode


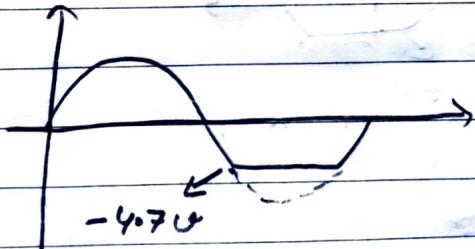


Q find o/p wave form .

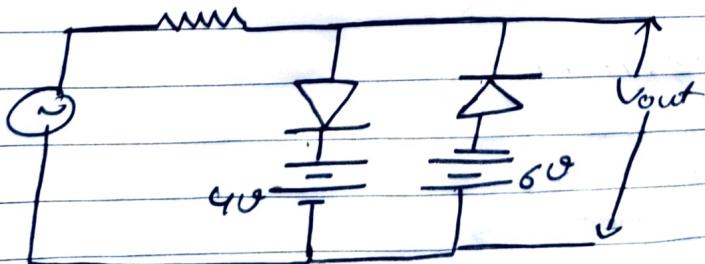

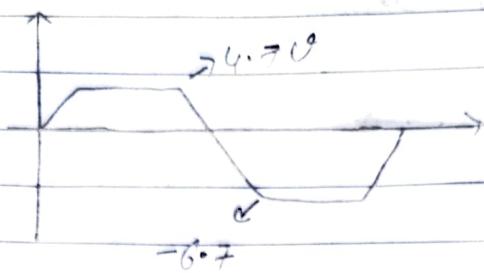

- Zener diode Clipping:

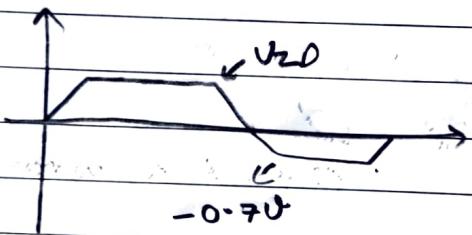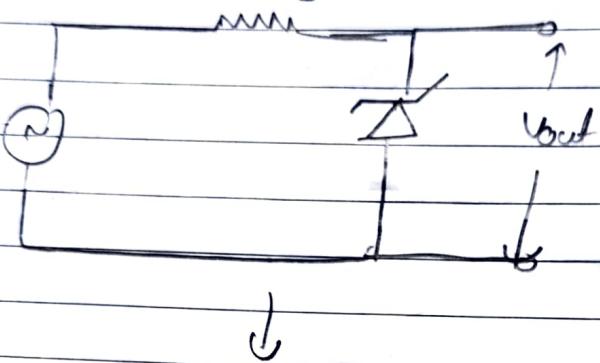



- Clampers:

time constant $\rightarrow \tau = CR$

$\tau \gg \frac{T}{2}$, where T = time period of the signal

- 1: Positive Clamper Circuit:

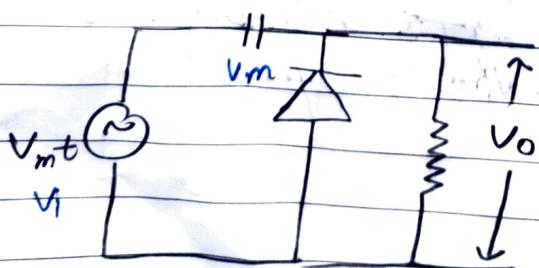

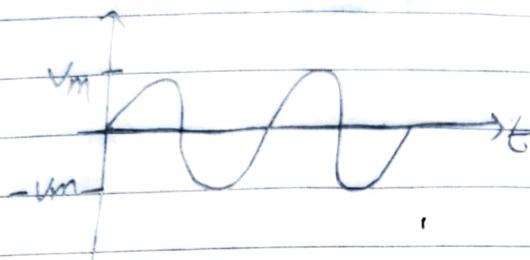

-ve half cycle:




Diode \rightarrow F.B.

Capacitor \rightarrow fully charge do +ve Vm.

+ve half cycle:

Diode \rightarrow R.B.
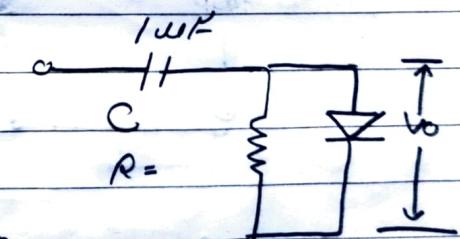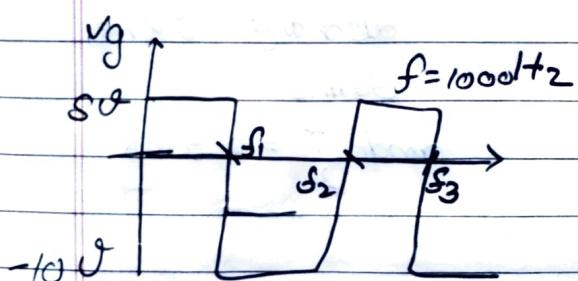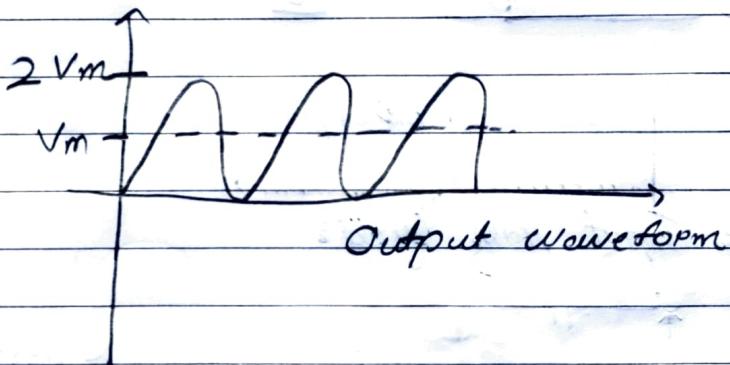
$$\text{O/p} \rightarrow V_i + V_m = 2V_m$$



The input signal of fig. (a) is applied to clammer circuit in (b). Draw the o/p waveform of o/p voltage V_o .


Time period of signal = $\frac{1}{f} = 1\text{ms}$

$$\frac{I}{2} = 0.5\text{ms}$$

$$T = 10\text{ms}$$


$$T \gg \frac{I}{2}$$

Positive Input Half-Cycle:

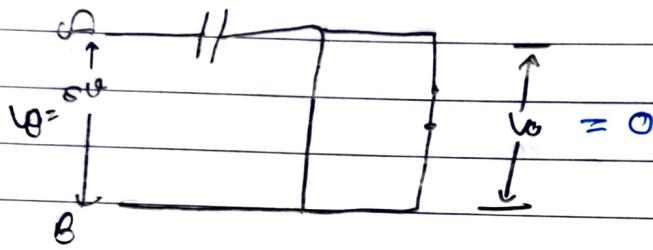


$+50V$ will be applied on A for 0.5ms

Negative Input Half-Cycle:

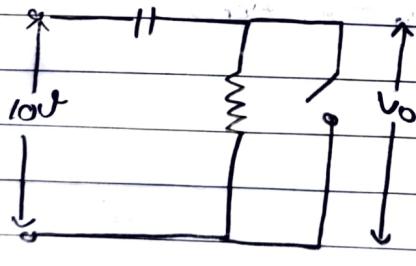


C needs to discharge at 5ms , i.e., 5ms .
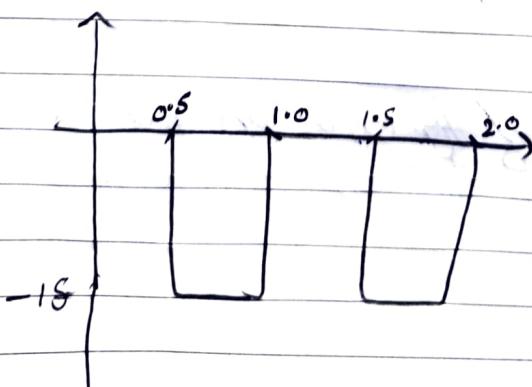
$$\text{and } \frac{I}{2} = 0.5\text{ms}$$



• Operational Amplifier (Op Amp):

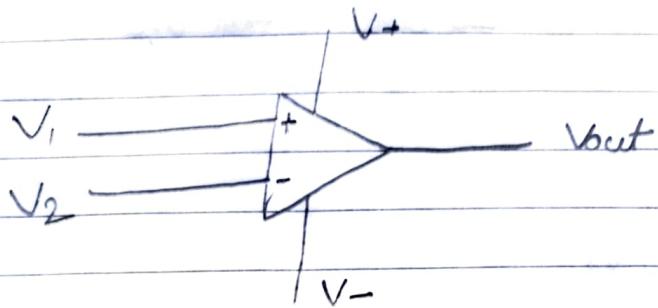



⇒ Two types:


- i Non-Inverting
- ii Inverting

$$V_{out} = A(V_1 - V_2)$$

↓


Chain

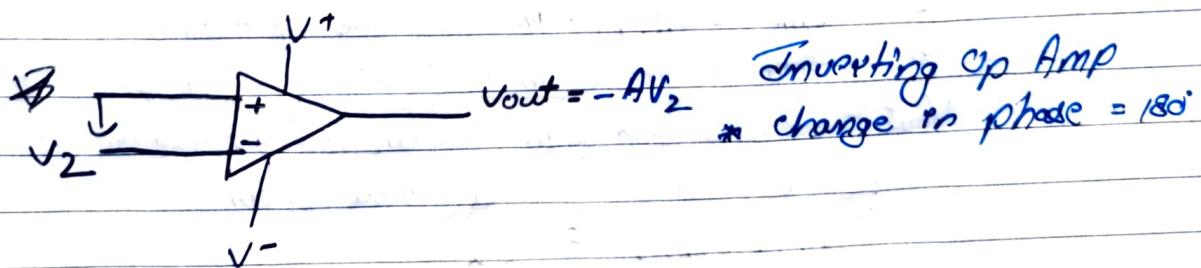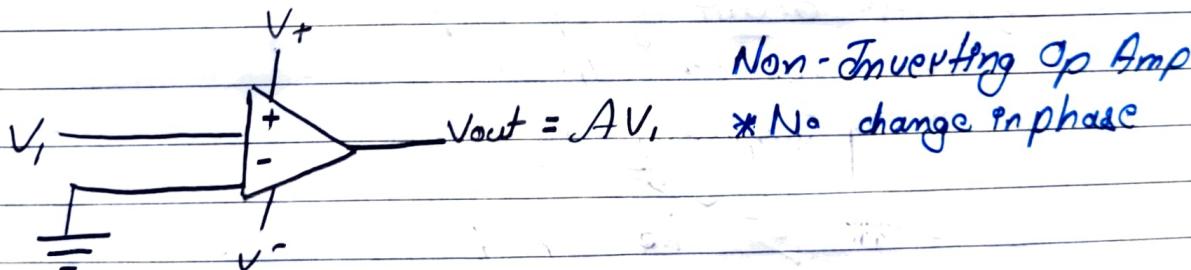

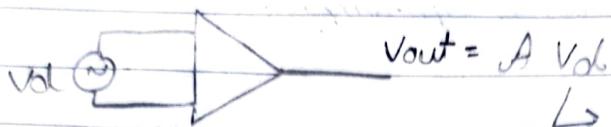


\hookrightarrow differential op-amp

$$A \approx 10^3 - 10^6$$

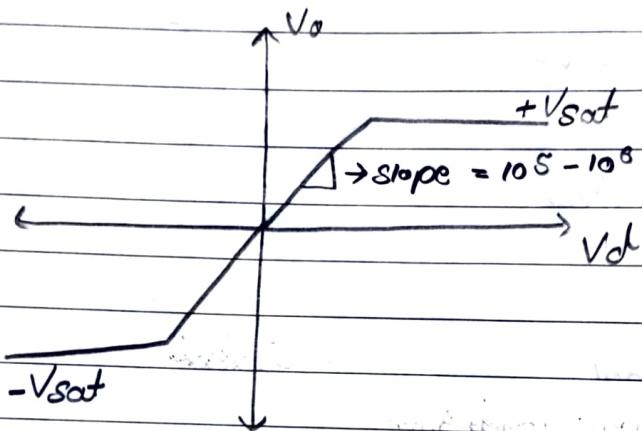

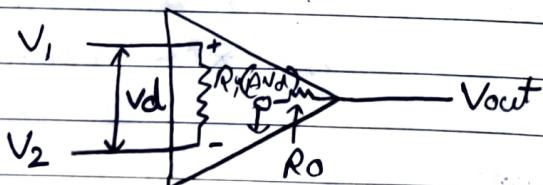\Rightarrow Equivalent circuit of Op-Amp:



R_i = input impedance of the op-amp

R_o = output impedance of the op-amp

$V_{out} =$ open loop gain multiplied by the difference
b/w the input signals V_1 and V_2 .

- Characteristics of an Ideal Op-Amp:
- 1. $R_i = \infty$, so that the input voltage applied b/w the input terminals will be directly applied to the op-amp.

2. $R_o = 0$,

3. Bandwidth = ∞ .

4. $A = \infty$

⇒

1. Infinite Input Impedance

Ideal

$$R_i = \infty$$

Practical

$$M\Omega$$

2. Zero o/p Impedance

$$R_o = 0$$

$$\sim 2$$


3. Infinite open loop gain

$$A = \infty$$

$$10^5 - 10^6$$

4. $V_{out} = 0$ when $V_{in} = 0$

$$mV$$

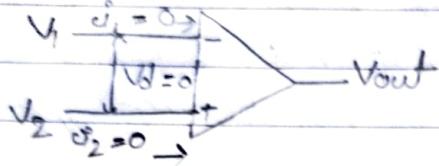

$$i_1 = i_2 = 0 \Rightarrow R_i \text{ is } \infty$$

- \Rightarrow Op-Amp draws no current at both the input terminals
i.e. $i_1 = i_2 = 0$
- \Rightarrow As the gain is infinite the Voltage b/w the inverting and non-inverting terminals ~~is~~ i.e. differential input voltage i.e. $V_d = (V_1 - V_2)$ is essentially zero, for the finite o/p voltage V_o .

• Feedback in Ideal op-amp:


\Rightarrow -ve feedback:

\rightarrow 2 basic feedback connection used.

Realistic \underline{i} The current drawn by the o/p terminals is negligible.
Assumptions \underline{ii} The differential o/p Voltage b/w non-inverting & inverting input terminal is zero.

\underline{iii} The differential o/p Voltage b/w non-inverting & inverting input terminal is zero.

\Rightarrow The Inverting Amplifier:

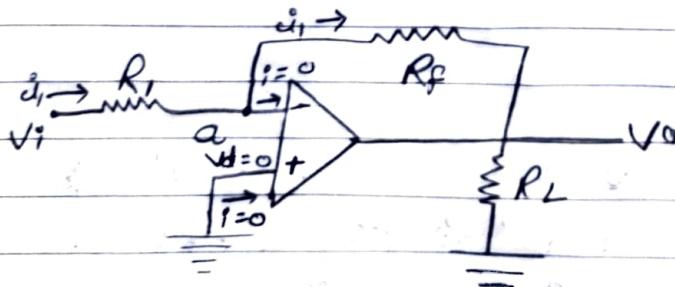

(a) Inverting Amplifier

$$\dot{i}_1 = \frac{V_i}{R_i}$$

$$V_o = -\dot{i}_1 R_f = -\frac{V_i}{R_i} R_f$$

Gain of the inverting amplifier (Closed loop gain):

$$A_{CL} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

The nodal eqn. at the node 'o' is

$$\frac{V_o - V_i}{R_i} + \frac{V_o - V_n}{R_f} = 0$$

V_o is the Voltage at node 'o'.

'o' is grounded, so $V_o = 0$

$$\frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

- Q Design an amplifier with the gain of -10 and input resistance $10\text{ k}\Omega$.

Ans $-10 = -\frac{R_f}{R_i}$

$$R_i = 100\text{ k}\Omega$$

- Q $R_i = 10\text{ k}\Omega$, $R_f = 100\text{ k}\Omega$, $V_i = 1\text{ V}$. A load of $25\text{k}\Omega$ is connected to the output terminal. Calculate \dot{i}_1 , V_o , \dot{i}_L and the total current i_o on o/p.

Ans $\dot{i}_1 = \frac{V_i}{R_i} = 10^{-4}\text{ A}$

~~$$\dot{i}_L = \frac{V_o}{R_L} = \frac{V_o}{25\text{k}\Omega} = \frac{10}{25 \times 10^3} = 4 \times 10^{-4}$$~~

$$V_o = -\frac{R_f}{R_i} \times V_i = -10\text{ V}$$

$$i_L = \frac{10}{25 \times 10^3}$$

$$= \frac{1 \times 10^{-2}}{25}$$

$$= 4 \times 10^{-4}$$

$$= 0.4 \text{ mA}$$

$$i_T = (0.4 + 0.1) \text{ mA}$$

$$= 0.5 \text{ mA}$$

• Practical Inverting Amplifier:

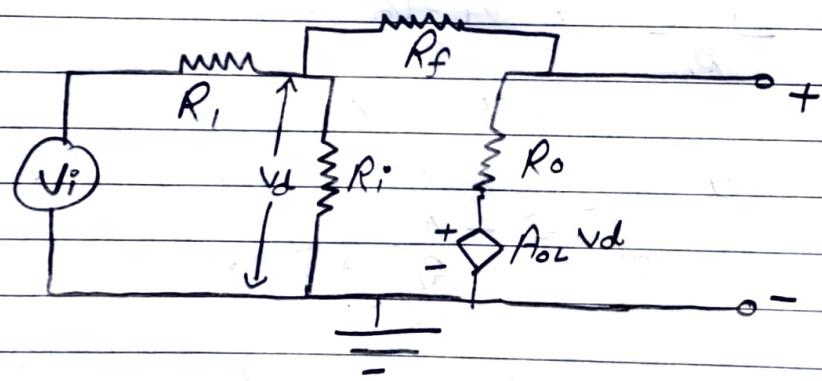


Fig : Equivalent circuit of a practical op-amp inverting amplifier

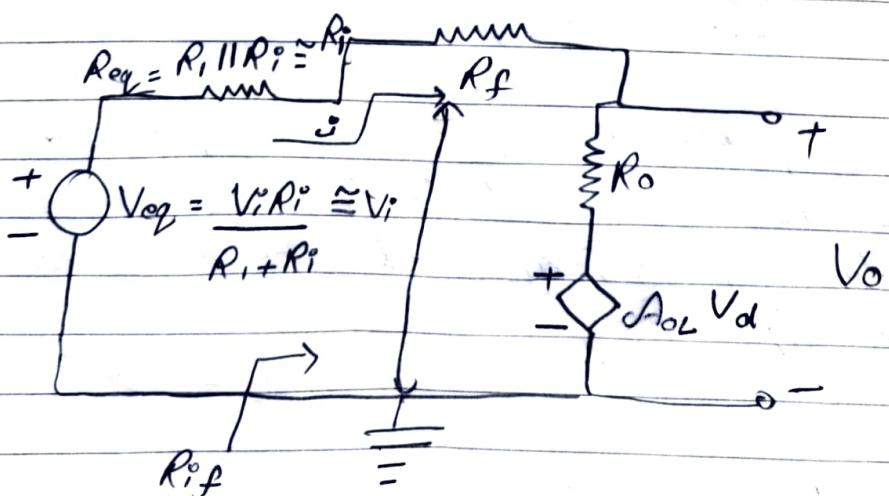


Fig: Simplified circuit by using Thevenin's Equivalent

from the o/p loop:

$$V_o = -jR_o + A_{OL} V_d - \textcircled{1}$$

\downarrow
open loop gain

Also

$$V_d + jR_f + V_o = 0 - \textcircled{2}$$

Putting the value of V_d from $\textcircled{1}$ to $\textcircled{2}$ and simplify eqn.

$$\begin{aligned} V_o - jR_o - A_{OL} V_d \\ \underline{A_{OL} V_o + jR_f A_{OL} + A_{OL} V_d} \end{aligned}$$

$$V_o (1 + A_{OL}) + j(CR_f A_{OL} - R_o) = 0$$

$$V_o = \frac{(R_o - R_f A_{OL}) j}{1 + A_{OL}} - \textcircled{3}$$

$$\frac{V_o - jR_o}{A_{OL}} = V_d$$

$$V_o - jR_o + j \cdot$$

Also, the RVL loop eqn.

$$V_i = j(CR_1 + R_f) + V_o - \textcircled{4}$$

Put the value of j from $\textcircled{3}$ into $\textcircled{4}$ and solve for closed loop gain,

$$A_{CL} = \frac{V_o}{V_i}$$

$$i = \frac{V_o (1 + A_{OL})}{R_o - A_{OL} R_f}$$

$$V_i^o = \frac{V_o (1 + A_{OL} (R_f + R_o)) + V_o}{R_o - A_{OL} R_f}$$

$$V_i^o = V_o \left[\frac{1 + A_{OL} + R_o - A_{OL} R_f}{R_o - A_{OL} R_f} \right]$$

$$\frac{V_o}{V_i^o} = \frac{R_o - A_{OL} R_f}{1 + A_{OL} + R_o - A_{OL} R_f}$$

$$\frac{V_o}{V_i^o} = \frac{R_o - A_{OL} R_f}{1 + A_{OL} (1 - R_f) + R_o}$$

$$V_i^o = V_o \left[\frac{R_f + R_o + A_{OL} (R_f + R_o) + R_o - A_{OL} R_f}{R_o - A_{OL} R_f} \right]$$

$$\begin{aligned} \frac{V_o}{V_i^o} &= \frac{R_o - A_{OL} R_f}{R_f + R_o + R_o + R_f A_{OL}} \\ &= \frac{R_o - A_{OL} R_f}{R_f (1 + A_{OL}) + R_o + R_f} \end{aligned}$$

If $A_{OL} \gg 1$, $A_{OL} R_f \gg R_o + R_f$ and neglecting R_o ,

$$A_{OL} = \frac{V_o}{V_i^o} = -\frac{R_f}{R_f}$$

\Rightarrow Input resistance, R_{if}

$$R_{if} = \frac{V_d}{i}$$


Writing the loop eqn. and solving for R_{if} .

$$V_d + i(R_f + R_o) + A_{ol}V_d = 0$$

$$V_d(1 + A_{ol}) = -i(R_f + R_o)$$

$$R_{if} = \frac{V_d}{i} = \frac{(R_f + R_o)}{1 + A_{ol}}$$

\Rightarrow Output impedance, R_{of}

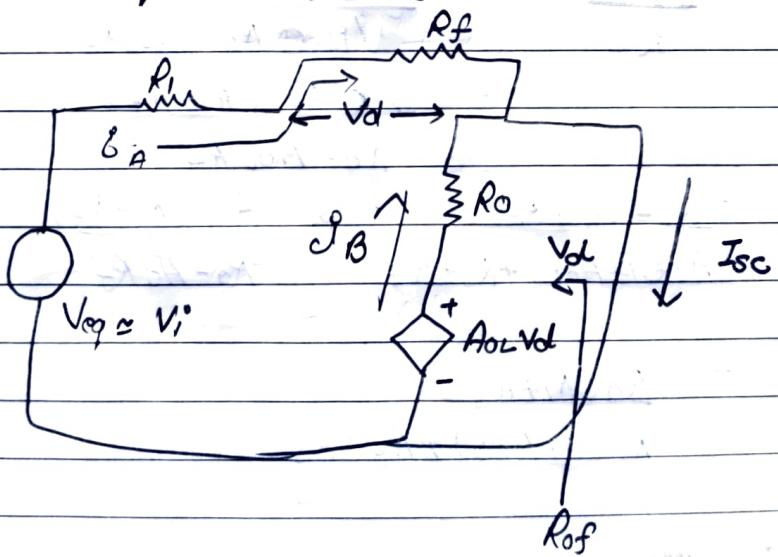

$$i_A = \frac{V_i}{R_i + R_f} \quad \text{--- (1)}$$

$$i_B = \frac{A_{ol}V_d}{R_o} \quad \text{--- (2)}$$

$$V_d = -i_A R_f$$

$$i_B = -\frac{A_{ol}i_A R_f}{R_o}$$

$$\begin{aligned}
 i_{SC} &= i_A + i_B \\
 &= A_o \cdot i_A - A_{oL} \frac{i_A R_f}{R_o} \\
 &= i_A \left(1 - A_{oL} \frac{R_f}{R_o} \right) \\
 &= \frac{V_i}{(R_i + R_f)} \frac{(R_o - A_{oL} R_f)}{R_o}
 \end{aligned}$$

$$A_{oL} = \frac{V_{oc}}{V_i}$$

$$A_{oL} V_i = V_{oc}$$

$$\begin{aligned}
 R_f &= \frac{V_{oc}}{i_{SC}} = \frac{A_{oL} \cdot V_i R_o (R_i + R_f)}{V_i (R_o - A_{oL} R_f)} \\
 &= \frac{A_{oL} R_o (R_i + R_f)}{R_o - A_{oL} R_f} \\
 &= \frac{(R_o - A_{oL} R_f)}{R_i (1 + A_{oL}) + R_o + R_f} \times \frac{R_o (R_i + R_f)}{R_o - A_{oL} R_f}
 \end{aligned}$$

$$R_f = \frac{R_o (R_i + R_f)}{R_i (1 + A_{oL}) + R_o + R_f}$$

If can be written as.

$$\begin{aligned}
 R_f &= \frac{R_o (R_i + R_f)}{R_o + R_i + R_f} \\
 &\quad \frac{1 + \frac{R_i A_{oL}}{A_{oL} + R_i + R_f}}{A_{oL} + R_i + R_f}
 \end{aligned}$$

• The Non-Inverting Amplifier:

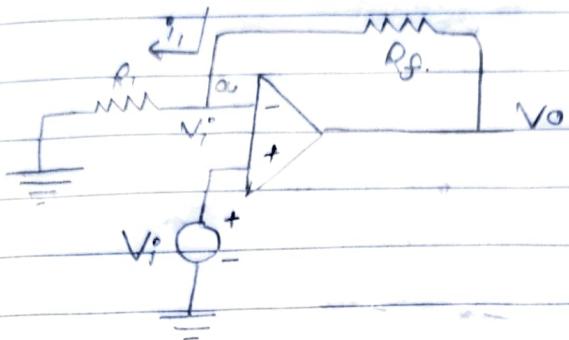


Fig. Non-Inverting Amplifier

Two assumptions:

- i Input current = 0
- ii $V_{OL} = 0$

$$V_i = \frac{V_o}{R_f + R_1} \cdot R_1$$

$$\frac{V_o}{V_i} = \frac{R_f + R_1}{R_1}$$

$$A_{CL} = 1 + \frac{R_f}{R_1}$$

• Practical Non-Inverting Amplifier:

- Practical Non-inverting Amplifier:

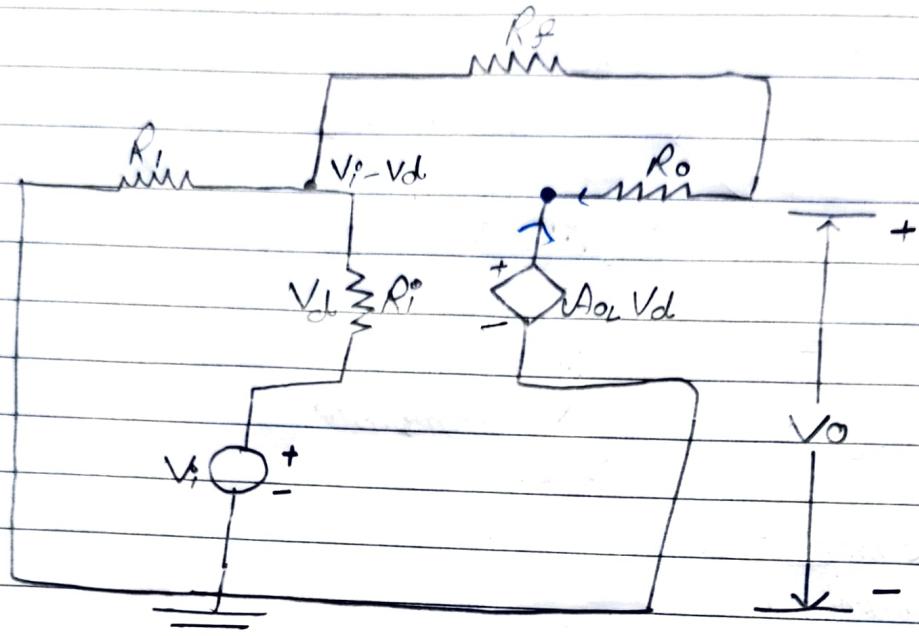


Fig. Equivalent circuit of non-inverting amplifier.

$$\cancel{V_i + V_d = \partial R_1}$$

$$\frac{V_i - V_d}{R_1} + \frac{V_d}{R_i} + \frac{V_i - V_d - V_o}{R_f} = 0$$

$$(V_i - V_d)Y_i + V_d Y_i^o + (V_i^o - V_d - V_o)Y_f = 0$$

\rightarrow Admittance

δe

$$- (Y_i + Y_i^o + Y_f) V_d + (Y_i + Y_f) V_i^o = Y_f V_o \quad \textcircled{1}$$

$$(Y_i + Y_i^o) V_i^o - Y_f V_o = V_d (Y_i + Y_f - Y_i^o)$$

$$\Rightarrow V_i Y_i = (V_d Y_i + V_d Y_f) + V_o Y_f - V_d Y_f - \\ V_o Y_f = 0.$$

$$\Rightarrow V_d [Y_i - Y_f - Y_f]$$

$$\Rightarrow -V_d [Y_i + Y_f + Y_f] + V_o [Y_f + Y_f] - V_o Y_f$$

At output node: KCL

$$Y_f (V_i^o - V_d - V_o) + (A_{OL} V_d - V_o) Y_o = 0$$

$$= V_o (Y_f + Y_o) + Y_f V_i^o + V_d (C - Y_f + A_{OL} Y_o) = 0 \quad - (2)$$

$$- V_o (Y_f + Y_o) + Y_f V_i^o = V_d (A_{OL} Y_o + Y_f)$$

$$(Y_f + Y_o - Y_i) (-V_o (Y_f + Y_o) + Y_f V_i^o) = (Y_f + Y_f) V_i^o - Y_f V_o$$

$$(Y_f + Y_o - Y_i) (-V_o Y_f - Y_o V_o + Y_f V_i^o) = Y_f V_i^o + Y_f V_i^o - Y_f V_o$$

$$- V_o Y_f Y_i - Y_o V_o Y_i + Y_f V_i^o Y_i - V_o Y_f^2 - Y_o V_o Y_f + \\ Y_f^2 V_i^o + Y_i V_o Y_f + Y_i Y_o V_o - Y_f V_i^o Y_i - Y_i V_i^o - Y_f V_i^o \\ + Y_f V_o = 0$$

$$V_o (C - Y_f Y_i - Y_o Y_f - Y_f^2 - Y_o Y_f + Y_i Y_f + Y_o Y_i^o \\ + Y_f) + V_i^o (C Y_f Y_i + Y_f^2 - Y_f Y_i^o - Y_i \\ - Y_f) = 0$$

$$\frac{V_o}{V_i^o} = Y_f Y_i + Y_o Y_i$$